



DesignNews

Field-Programmable Gate Array (FPGA) Primer

Day 2: Verilog 101

Sponsored by



Webinar Logistics

- Turn on your system sound to hear the streaming presentation.
- If you have technical problems, click “Help” or submit a question asking for assistance.
- Participate in ‘Attendee Chat’ by maximizing the chat widget in your dock.




Fred Eady



Visit 'Lecturer Profile' in your console for more details.

AGENDA


 
- The Hook Up
- Vivado Projects
 - *gates*
 - *sw_to_led*
 - *seven_seg_A*
 - *debounce_A*



 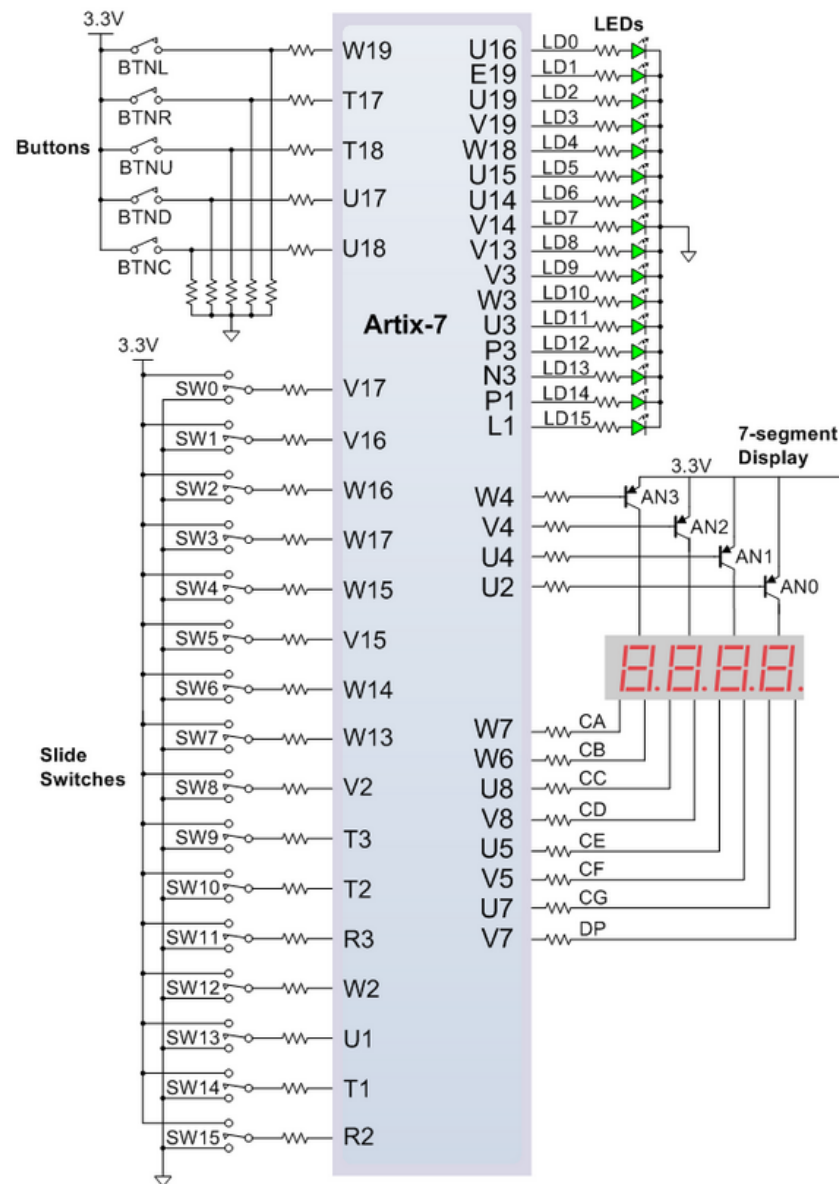  
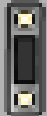

Buttons, Switches and LEDs




JTAG (Joint Test Action Group)




Programming Mode Jumper

JP1	
	SPI Flash
	JTAG
	USB


Programming Mode

 



The Other Side

 

32Mbit Non-Volatile Serial Flash

 

Flow

 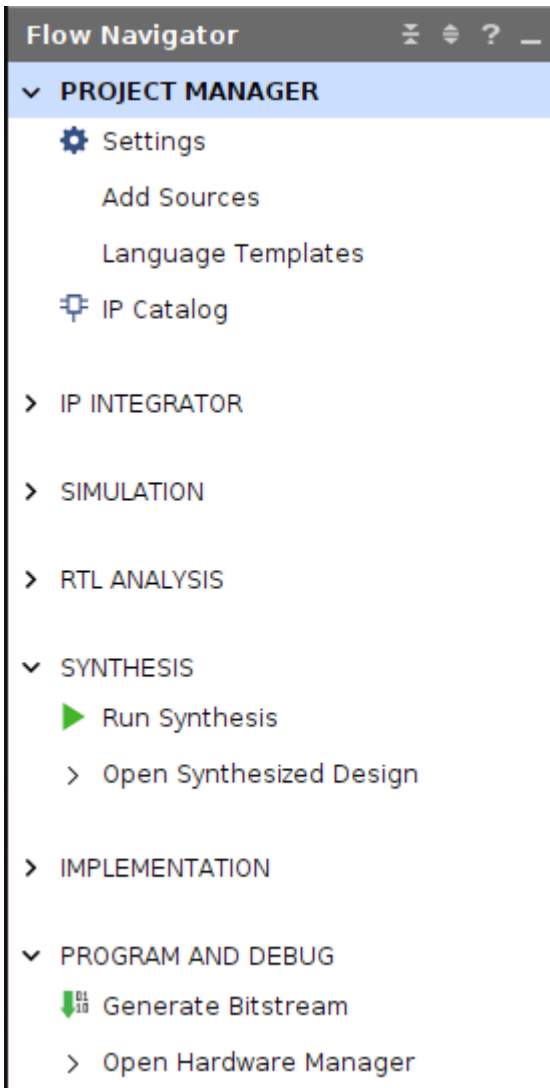

Gate Modules

Top Module

```

22 module gates_top
23 (
24     input [15:0] sw,
25     output [15:0] led,
26     output [3:0] an
27 );


```

GATE Instantiations

```

30 andGate gateAND      48 norGate gateNOR
31 (                    49 (
32     .a(sw[0]),        50     .a(sw[6]),
33     .b(sw[1]),        51     .b(sw[7]),
34     .y(led[0])        52     .y(led[3])
35 );                    53 );
36 nandGate gateNAND    54 exorGate gateEXOR
37 (                    55 (
38     .a(sw[4]),        56     .a(sw[8]),
39     .b(sw[5]),        57     .b(sw[9]),
40     .y(led[2])        58     .y(led[4])
41 );                    59 );
42 orGate gateOR        60 exnorGate gateEXNOR
43 (                    61 (
44     .a(sw[2]),        62     .a(sw[10]),
45     .b(sw[3]),        63     .b(sw[11]),
46     .y(led[1])        64     .y(led[5])
47 );                    65 );

```

 

GATE Modules

```

22 module andGate(      49 module norGate(
23     input a,          50     input a,
24     input b,          51     input b,
25     output y          52     output y
26 );                  53     );
27     //assign y = a & b; 54     assign y = ~(a | b);
28     and(y,a,b);      55     //nor(y,a,b);
29 endmodule            56 endmodule
30                    57
31 module nandGate(     58 module exorGate(
32     input a,          59     input a,
33     input b,          60     input b,
34     output y          61     output y
35 );                  62     );
36     assign y = ~(a & b); 63     //assign y = a ^ b;
37     //nand(y,a,b);   64     xor(y,a,b);
38 endmodule            65 endmodule
39                    66
40 module orGate(       67 module exnorGate(
41     input a,          68     input a,
42     input b,          69     input b,
43     output y          70     output y
44 );                  71     );
45     //assign y = a | b; 72     assign y = ~(a ^ b);
46     or(y,a,b);       73     //xnor(y,a,b);
47 endmodule            74 endmodule

```


AND Gate - Basys-3-Master.xdc

```

22 module gates_top
23 (
24     input [15:0] sw,
25     output [15:0] led,
26     output [3:0] an
27 );
28
29 //anode segments are active low
30 //turn off 7-segment anodes
31 assign an = 4'b1111;
32
33 andGate gateAND
34 (
35     .a(sw[0]),
36     .b(sw[1]),
37     .y(led[0])
38 );

```

```

22 module andGate(
23     input a,
24     input b,
25     output y
26 );
27     //assign y = a & b;
28     and(y,a,b);
29 endmodule

```

```

11 ## Switches
12 set_property -dict { PACKAGE_PIN V17 IOSTANDARD LVCMOS33 } [get_ports {sw[0]}]
13 set_property -dict { PACKAGE_PIN V16 IOSTANDARD LVCMOS33 } [get_ports {sw[1]}]
14 set_property -dict { PACKAGE_PIN W16 IOSTANDARD LVCMOS33 } [get_ports {sw[2]}]
15 set_property -dict { PACKAGE_PIN W17 IOSTANDARD LVCMOS33 } [get_ports {sw[3]}]
16 set_property -dict { PACKAGE_PIN W15 IOSTANDARD LVCMOS33 } [get_ports {sw[4]}]
17 set_property -dict { PACKAGE_PIN V15 IOSTANDARD LVCMOS33 } [get_ports {sw[5]}]
18 set_property -dict { PACKAGE_PIN W14 IOSTANDARD LVCMOS33 } [get_ports {sw[6]}]
19 set_property -dict { PACKAGE_PIN W13 IOSTANDARD LVCMOS33 } [get_ports {sw[7]}]
20 set_property -dict { PACKAGE_PIN V2 IOSTANDARD LVCMOS33 } [get_ports {sw[8]}]
21 set_property -dict { PACKAGE_PIN T3 IOSTANDARD LVCMOS33 } [get_ports {sw[9]}]
22 set_property -dict { PACKAGE_PIN T2 IOSTANDARD LVCMOS33 } [get_ports {sw[10]}]
23 set_property -dict { PACKAGE_PIN R3 IOSTANDARD LVCMOS33 } [get_ports {sw[11]}]
24 set_property -dict { PACKAGE_PIN W2 IOSTANDARD LVCMOS33 } [get_ports {sw[12]}]
25 set_property -dict { PACKAGE_PIN U1 IOSTANDARD LVCMOS33 } [get_ports {sw[13]}]
26 set_property -dict { PACKAGE_PIN T1 IOSTANDARD LVCMOS33 } [get_ports {sw[14]}]
27 set_property -dict { PACKAGE_PIN R2 IOSTANDARD LVCMOS33 } [get_ports {sw[15]}]
28
29
30 ## LEDs
31 set_property -dict { PACKAGE_PIN U16 IOSTANDARD LVCMOS33 } [get_ports {led[0]}]
32 set_property -dict { PACKAGE_PIN E19 IOSTANDARD LVCMOS33 } [get_ports {led[1]}]
33 set_property -dict { PACKAGE_PIN U19 IOSTANDARD LVCMOS33 } [get_ports {led[2]}]
34 set_property -dict { PACKAGE_PIN V19 IOSTANDARD LVCMOS33 } [get_ports {led[3]}]
35 set_property -dict { PACKAGE_PIN W18 IOSTANDARD LVCMOS33 } [get_ports {led[4]}]
36 set_property -dict { PACKAGE_PIN U15 IOSTANDARD LVCMOS33 } [get_ports {led[5]}]
37 set_property -dict { PACKAGE_PIN U14 IOSTANDARD LVCMOS33 } [get_ports {led[6]}]
38 set_property -dict { PACKAGE_PIN V14 IOSTANDARD LVCMOS33 } [get_ports {led[7]}]
39 set_property -dict { PACKAGE_PIN V13 IOSTANDARD LVCMOS33 } [get_ports {led[8]}]
40 set_property -dict { PACKAGE_PIN V3 IOSTANDARD LVCMOS33 } [get_ports {led[9]}]
41 set_property -dict { PACKAGE_PIN W3 IOSTANDARD LVCMOS33 } [get_ports {led[10]}]
42 set_property -dict { PACKAGE_PIN U3 IOSTANDARD LVCMOS33 } [get_ports {led[11]}]
43 set_property -dict { PACKAGE_PIN P3 IOSTANDARD LVCMOS33 } [get_ports {led[12]}]
44 set_property -dict { PACKAGE_PIN N3 IOSTANDARD LVCMOS33 } [get_ports {led[13]}]
45 set_property -dict { PACKAGE_PIN P1 IOSTANDARD LVCMOS33 } [get_ports {led[14]}]
46 set_property -dict { PACKAGE_PIN L1 IOSTANDARD LVCMOS33 } [get_ports {led[15]}]

```


AND Gate – Generated Schematic

```


22 module gates_top
23 (
24     input [15:0] sw,
25     output [15:0] led,
26     output [3:0] an
27 );
28
29 //anode segments are active low
30 //turn off 7-segment anodes
31 assign an = 4'b1111;
32
33 andGate gateAND
34 (
35     .a(sw[0]),
36     .b(sw[1]),
37     .y(led[0])
38 );

```

```

22 module andGate(
23     input a,
24     input b,
25     output y
26 );
27 //assign y = a & b;
28     and(y,a,b);
29 endmodule

```

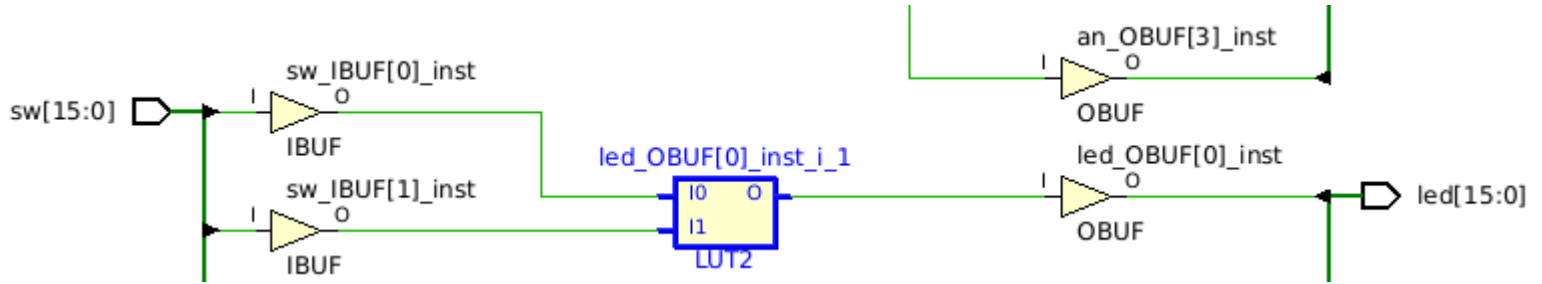

Cell Properties

led_OBUF[0]_inst_i_1

I1	I0	O=I0 & I1
0	0	0
0	1	0
1	0	0
1	1	1

Edit LUT Equation...

Power Nets Cell Pins **Truth Table**

AND Gate – Simulation View

```

22 module gates_top
23 (
24     input [15:0] sw,
25     output [15:0] led,
26     output [3:0] an
27 );
28
29 //anode segments are active low
30 //turn off 7-segment anodes
31 assign an = 4'b1111;
32
33 andGate gateAND
34 (
35     .a(sw[0]),
36     .b(sw[1]),
37     .y(led[0])
38 );

```

```

22 module andGate(
23     input a,
24     input b,
25     output y
26 );
27     //assign y = a & b;
28     and(y,a,b);
29 endmodule

```




Switch x ON = LED x ON

```

23 module sw_to_led_top(
24     input [15:0] sw,
25     output [15:0] led
26 );
27
28 // always @*
29 // begin
30 //     led[0] <= sw[0];
31 //     led[1] <= sw[1];
32 //     led[2] <= sw[2];
33 // end
34
35 sw_to_led hextoled(
36     .hex_in(sw),
37     .led_out(led)
38 );
39 endmodule
  
```

```

 
23 module sw_to_led_top(
24     input [15:0] sw,
25     output reg [15:0] led
26 );
27
28 always @*
29 begin
30     led[0] <= sw[0];
31     led[1] <= sw[1];
32     led[2] <= sw[2];
33 end
34
35 // sw_to_led hextoled(
36 //     .hex_in(sw),
37 //     .led_out(led)
38 // );
39 endmodule
  
```



```

23 module sw_to_led(
24     input [15:0] hex_in,
25     output reg [15:0] led_out
26 );
27
28 // activate on any input change
29 always @*
30 begin
31     case(hex_in)
32         16'h0: led_out <= 16'b0000000000000000; // LED OFF
33         16'h1: led_out <= 16'b0000000000000001; // LED 0
34         16'h2: led_out <= 16'b0000000000000010; // LED 1
35         16'h4: led_out <= 16'b0000000000000100; // LED 2
36         16'h8: led_out <= 16'b0000000000001000; // LED 3
37         16'h10: led_out <= 16'b0000000000010000; // LED 4
38         16'h20: led_out <= 16'b000000000100000; // LED 5
39         16'h40: led_out <= 16'b000000001000000; // LED 6
40         16'h80: led_out <= 16'b000000010000000; // LED 7
41         16'h100: led_out <= 16'b000000010000000; // LED 8
42         16'h200: led_out <= 16'b000000100000000; // LED 9
43         16'h400: led_out <= 16'b000001000000000; // LED 10
44         16'h800: led_out <= 16'b000010000000000; // LED 11
45         16'h1000: led_out <= 16'b000100000000000; // LED 12
46         16'h2000: led_out <= 16'b001000000000000; // LED 13
47         16'h4000: led_out <= 16'b010000000000000; // LED 14
48         16'h8000: led_out <= 16'b100000000000000; // LED 15
49         default: led_out <= 16'b000000000000000; // LED OFF
50     endcase
51 end
52 endmodule
  
```


Seven-Segment Display Pin Assignments

 

```

50 set_property -dict { PACKAGE_PIN W7 IOSTANDARD LVCMOS33 } [get_ports {seg[0]}] A
51 set_property -dict { PACKAGE_PIN W6 IOSTANDARD LVCMOS33 } [get_ports {seg[1]}] B
52 set_property -dict { PACKAGE_PIN U8 IOSTANDARD LVCMOS33 } [get_ports {seg[2]}] C
53 set_property -dict { PACKAGE_PIN V8 IOSTANDARD LVCMOS33 } [get_ports {seg[3]}] D
54 set_property -dict { PACKAGE_PIN U5 IOSTANDARD LVCMOS33 } [get_ports {seg[4]}] E
55 set_property -dict { PACKAGE_PIN V5 IOSTANDARD LVCMOS33 } [get_ports {seg[5]}] F
56 set_property -dict { PACKAGE_PIN U7 IOSTANDARD LVCMOS33 } [get_ports {seg[6]}] G
57
58 #set_property -dict { PACKAGE_PIN V7 IOSTANDARD LVCMOS33 } [get_ports dp]
59
60 set_property -dict { PACKAGE_PIN U2 IOSTANDARD LVCMOS33 } [get_ports {an[0]}]
61 set_property -dict { PACKAGE_PIN U4 IOSTANDARD LVCMOS33 } [get_ports {an[1]}]
62 set_property -dict { PACKAGE_PIN V4 IOSTANDARD LVCMOS33 } [get_ports {an[2]}]
63 set_property -dict { PACKAGE_PIN W4 IOSTANDARD LVCMOS33 } [get_ports {an[3]}]
    
```

```

23 // seven-segment digit display driver
24
25 module sseg_display (
26     input [3:0] hex_in,
27     output reg [6:0] seg_out
28 );
29
30 // activate on any input change
31 always @*
32 begin
33     case(hex_in)
34         4'h0: seg_out <= 7'b1000000; // digit 0
35         4'h1: seg_out <= 7'b1111001; // digit 1
36         4'h2: seg_out <= 7'b0100100; // digit 2
37         4'h3: seg_out <= 7'b0110000; // digit 3
38         4'h4: seg_out <= 7'b0011001; // digit 4
39         4'h5: seg_out <= 7'b0010010; // digit 5
40         4'h6: seg_out <= 7'b0000010; // digit 6
41         4'h7: seg_out <= 7'b1111000; // digit 7
42         4'h8: seg_out <= 7'b0000000; // digit 8
43         4'h9: seg_out <= 7'b0010000; // digit 9
44         4'ha: seg_out <= 7'b0001000; // digit A
45         4'hb: seg_out <= 7'b0000011; // digit B
46         4'hc: seg_out <= 7'b1000110; // digit C
47         4'hd: seg_out <= 7'b0100001; // digit D
48         4'he: seg_out <= 7'b0000110; // digit E
49         4'hf: seg_out <= 7'b0001110; // digit F
50         default: seg_out <= 7'b1111111; // digit OFF
51     endcase
    
```


Hex-to-Seven-Segment

```

22 module sseg_top(
23     input [3:0] sw,
24     output [6:0] seg,
25     output [3:0] an
26 );
27
28 // an is active low, turn on an[0], others off
29 assign an = 4'b1110;
30
31 // connect our input to the display
32 sseg_display display(
33     .hex_in(sw),
34     .seg_out(seg)
35 );
36
37 endmodule
  
```


 Top Module


 Hex-to-Segment

```


12 set_property -dict { PACKAGE_PIN V17 IOSTANDARD LVCMOS33 } [get_ports {sw[0]}]
13 set_property -dict { PACKAGE_PIN V16 IOSTANDARD LVCMOS33 } [get_ports {sw[1]}]
14 set_property -dict { PACKAGE_PIN W16 IOSTANDARD LVCMOS33 } [get_ports {sw[2]}]
15 set_property -dict { PACKAGE_PIN W17 IOSTANDARD LVCMOS33 } [get_ports {sw[3]}]
16
49 ##7 Segment Display
50 set_property -dict { PACKAGE_PIN W7 IOSTANDARD LVCMOS33 } [get_ports {seg[0]}]
51 set_property -dict { PACKAGE_PIN W6 IOSTANDARD LVCMOS33 } [get_ports {seg[1]}]
52 set_property -dict { PACKAGE_PIN U8 IOSTANDARD LVCMOS33 } [get_ports {seg[2]}]
53 set_property -dict { PACKAGE_PIN V8 IOSTANDARD LVCMOS33 } [get_ports {seg[3]}]
54 set_property -dict { PACKAGE_PIN U5 IOSTANDARD LVCMOS33 } [get_ports {seg[4]}]
55 set_property -dict { PACKAGE_PIN V5 IOSTANDARD LVCMOS33 } [get_ports {seg[5]}]
56 set_property -dict { PACKAGE_PIN U7 IOSTANDARD LVCMOS33 } [get_ports {seg[6]}]
57
58 #set_property -dict { PACKAGE_PIN V7 IOSTANDARD LVCMOS33 } [get_ports dp]
59
60 set_property -dict { PACKAGE_PIN U2 IOSTANDARD LVCMOS33 } [get_ports {an[0]}]
61 set_property -dict { PACKAGE_PIN U4 IOSTANDARD LVCMOS33 } [get_ports {an[1]}]
62 set_property -dict { PACKAGE_PIN V4 IOSTANDARD LVCMOS33 } [get_ports {an[2]}]
63 set_property -dict { PACKAGE_PIN W4 IOSTANDARD LVCMOS33 } [get_ports {an[3]}]
  
```


 Xilinx Design
Constraint File

```

23 // seven-segment digit display driver
24
25 module sseg_display (
26     input [3:0] hex_in,
27     output reg [6:0] seg_out
28 );
29
30 // activate on any input change
31 always @*
32 begin
33     case(hex_in)
34         4'h0: seg_out <= 7'b1000000; // digit 0
35         4'h1: seg_out <= 7'b1111001; // digit 1
36         4'h2: seg_out <= 7'b0100100; // digit 2
37         4'h3: seg_out <= 7'b0110000; // digit 3
38         4'h4: seg_out <= 7'b0011001; // digit 4
39         4'h5: seg_out <= 7'b0010010; // digit 5
40         4'h6: seg_out <= 7'b0000010; // digit 6
41         4'h7: seg_out <= 7'b1111000; // digit 7
42         4'h8: seg_out <= 7'b0000000; // digit 8
43         4'h9: seg_out <= 7'b0010000; // digit 9
44         4'ha: seg_out <= 7'b0001000; // digit A
45         4'hb: seg_out <= 7'b0000011; // digit B
46         4'hc: seg_out <= 7'b1000110; // digit C
47         4'hd: seg_out <= 7'b0100001; // digit D
48         4'he: seg_out <= 7'b0000110; // digit E
49         4'hf: seg_out <= 7'b0001110; // digit F
50         default: seg_out <= 7'b1111111; // digit OFF
51     endcase
  
```


Hex-to-Seven-Segment

 

```


25 module sseg_display (
26     input [3:0] hex_in,
27     output reg [6:0] seg_out
28 );
29
30 // activate on any input change
31 always @*
32 begin
33     case(hex_in)
34         4'h0: seg_out <= 7'b100000; // digit 0
35         4'h1: seg_out <= 7'b1111001; // digit 1
36         4'h2: seg_out <= 7'b0100100; // digit 2
37         4'h3: seg_out <= 7'b0110000; // digit 3
38         4'h4: seg_out <= 7'b0011001; // digit 4
39         4'h5: seg_out <= 7'b0010010; // digit 5
40         4'h6: seg_out <= 7'b0000010; // digit 6
41         4'h7: seg_out <= 7'b1111000; // digit 7
42         4'h8: seg_out <= 7'b0000000; // digit 8
43         4'h9: seg_out <= 7'b0010000; // digit 9
44         4'ha: seg_out <= 7'b0001000; // digit A
45         4'hb: seg_out <= 7'b0000011; // digit B
46         4'hc: seg_out <= 7'b1000110; // digit C
47         4'hd: seg_out <= 7'b0100001; // digit D
48         4'he: seg_out <= 7'b0000110; // digit E
49         4'hf: seg_out <= 7'b0001110; // digit F
50         default: seg_out <= 7'b1111111; // digit OFF
51     endcase
52 end
53 endmodule

```


Debouncing Pushbuttons


```

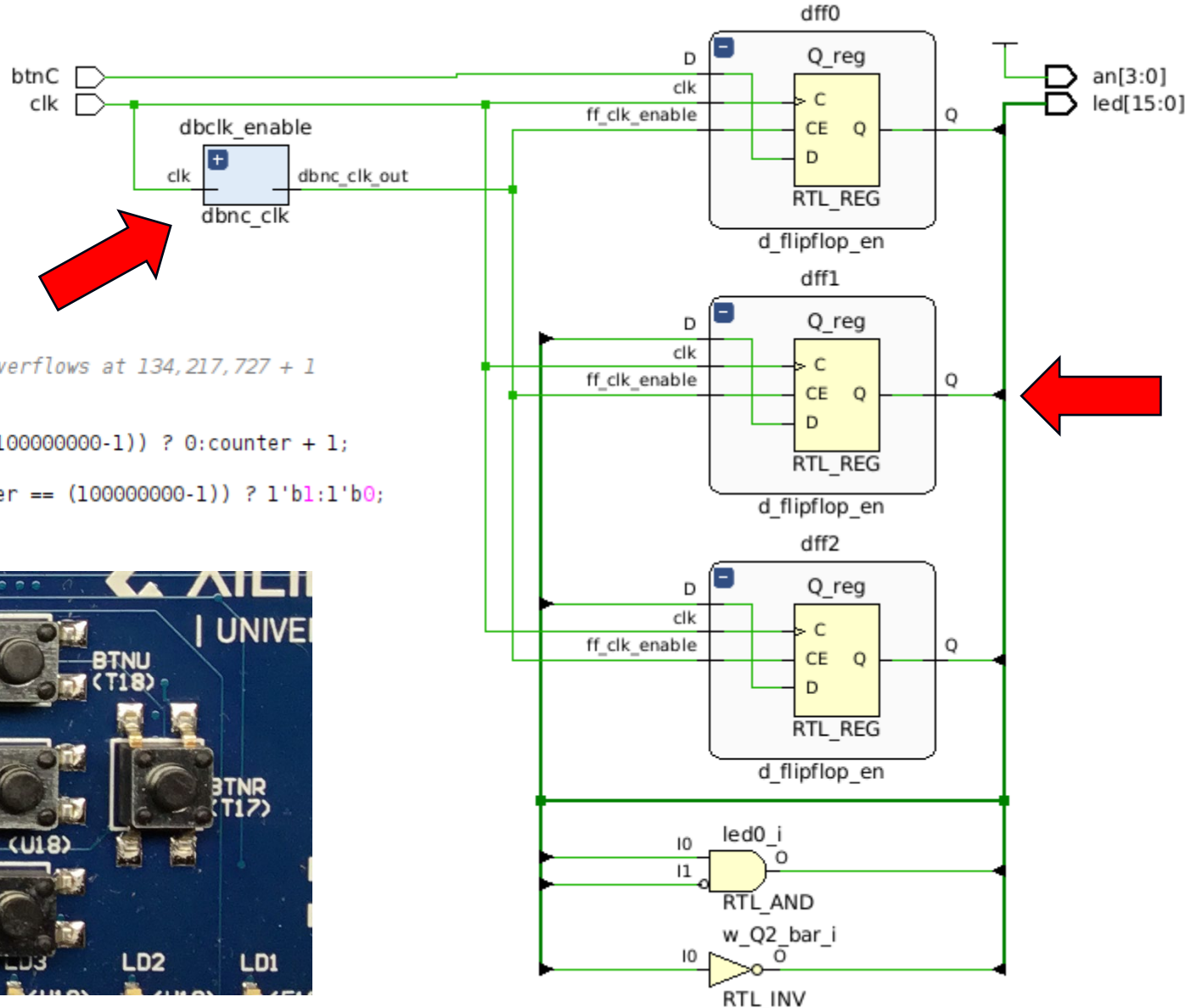23 module dbnc_clk(
24     input clk,
25     output dbnc_clk_out
26 );
27     reg [26:0] counter = 0; //overflows at 134,217,727 + 1
28     always @ (posedge clk)
29     begin
30         counter <= (counter >= (100000000-1)) ? 0:counter + 1;
31     end
32     assign dbnc_clk_out = (counter == (100000000-1)) ? 1'b1:1'b0;
33 endmodule
    
```



```

 23 module d_flipflop_en(
24     input clk,
25     input ff_clk_enable,
26     input D,
27     output reg Q=0
28 );
29     always @ (posedge clk)
30     begin
31         if(ff_clk_enable == 1)
32             Q <= D;
33     end
34 endmodule
    
```




Debouncing Pushbuttons

```

23 module debounce_top(
24     input clk,
25     input btnC,
26     output [15:0] led,
27     output [3:0] an
28 );
29 //turn off 7-segment anodes
30 assign an = 4'b1111;
31
32 wire w_clk_enable;
33 wire w_Q0,w_Q1,w_Q2,w_Q2_bar;
34
35 dbnc_clk dbclk_enable(
36     .clk(clk),
37     .dbnc_clk_out(w_clk_enable)
38 );
39 d_flipflop_en dff0(
40     .clk(clk),
41     .ff_clk_enable(w_clk_enable),
42     .D(btnC),
43     .Q(w_Q0)
44 );
45 d_flipflop_en dff1(
46     .clk(clk),
47     .ff_clk_enable(w_clk_enable),
48     .D(w_Q0),
49     .Q(w_Q1)
50 );
51 d_flipflop_en dff2(
52     .clk(clk),
53     .ff_clk_enable(w_clk_enable),
54     .D(w_Q1),
55     .Q(w_Q2)
56 );

```

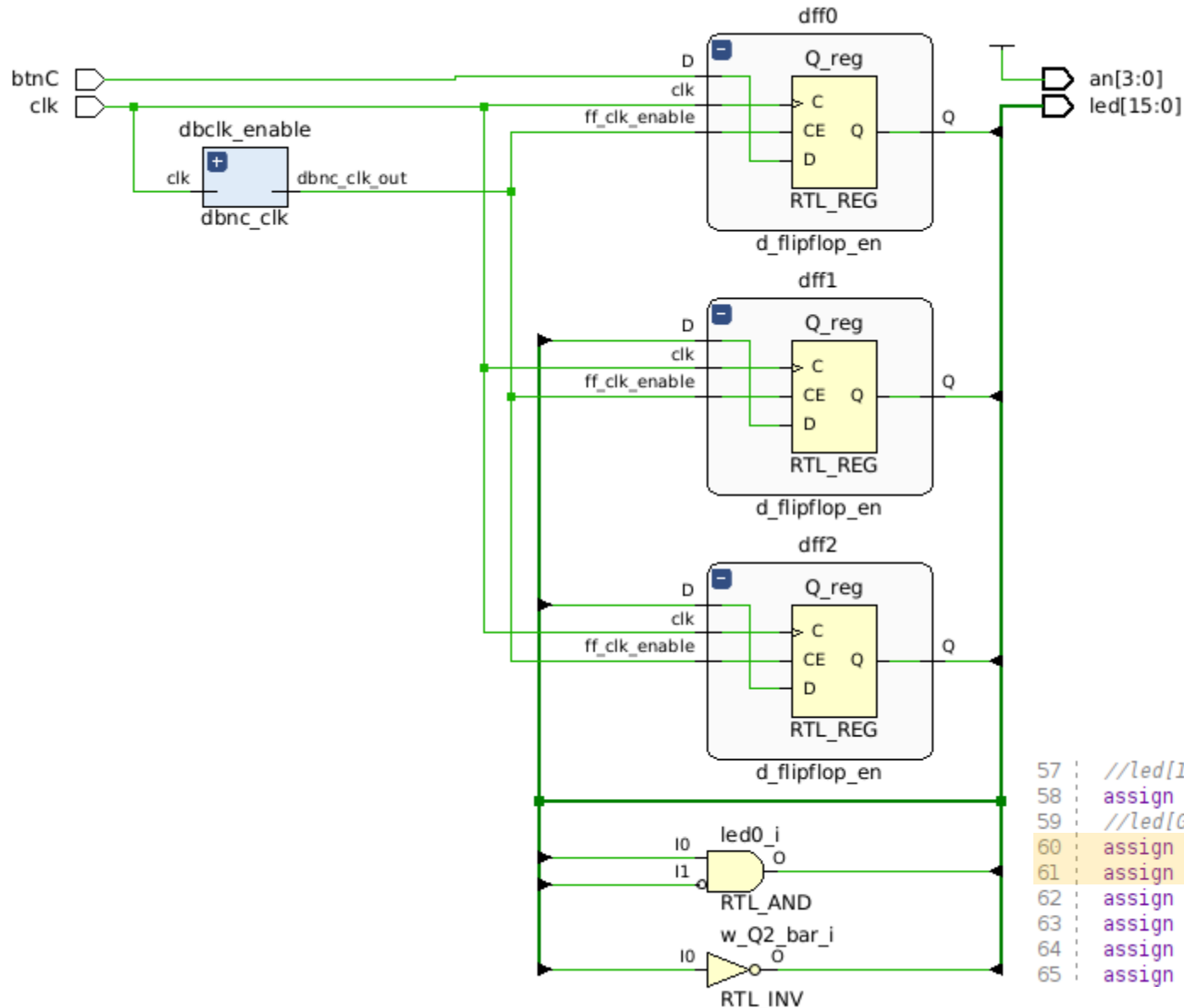

```

57 //led[1] on as long as btnC is depressed
58 assign led[1] = w_Q2;
59 //led[0] on for 1 second
60 assign w_Q2_bar = ~w_Q2;
61 assign led[0] = w_Q1 & w_Q2_bar;
62 assign led[15] = w_Q0;
63 assign led[14] = w_Q1;
64 assign led[13] = w_Q2;
65 assign led[12] = w_Q2_bar;


```


MORE TO COME..

Thank you for attending!!!

Please consider the resources below:

 - xilinx.com
- digilent.com
- [Basys 3 Reference Manual](#)





DesignNews

Thank You

Sponsored by

