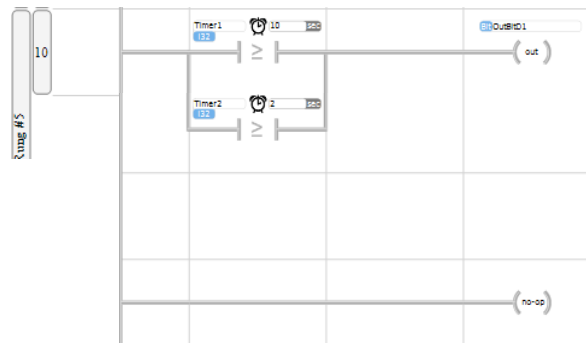


# Programmable Logic Controllers: Hands On Introduction to Industrial Controls

## Class 2: PLC Bit Instruction Basics

March 28, 2017 – Don Wilcher



# PLC Bit Instruction Basics

## Topics

- PLC Bit Instructions
- Introduction to Basic Logic Gates
- Setting up the Velocio “vBuilder” software (Ladder Logic)
- Hands-On Project: Bit Instruction – Logic Based Controllers

# PLC Bit Instructions

Bit Instructions can be divided into two broad categories:


- Input
- Output

Input Instruction is a contact.


Output Instruction is a coil.

# PLC Bit Instructions...

Input Instruction is a contact.

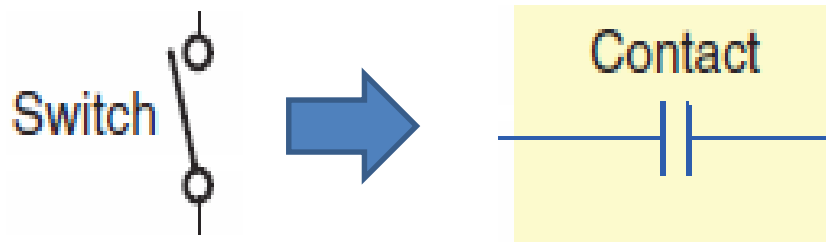

Output Instruction is a coil.

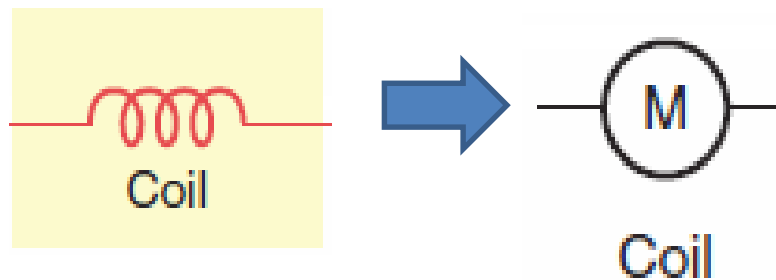

# PLC Bit Instructions...

Contacts and Coils used in an Electrical Control Circuit.

Switch open and coil **de-energized**

Switch closed and coil **energized**

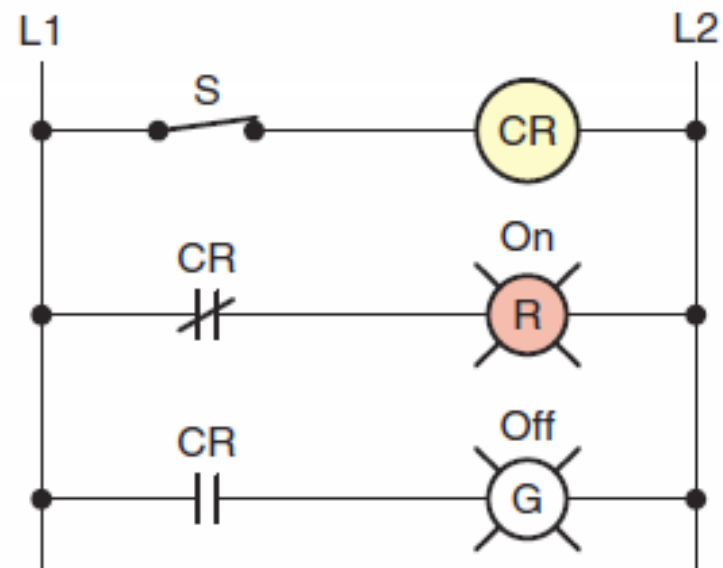
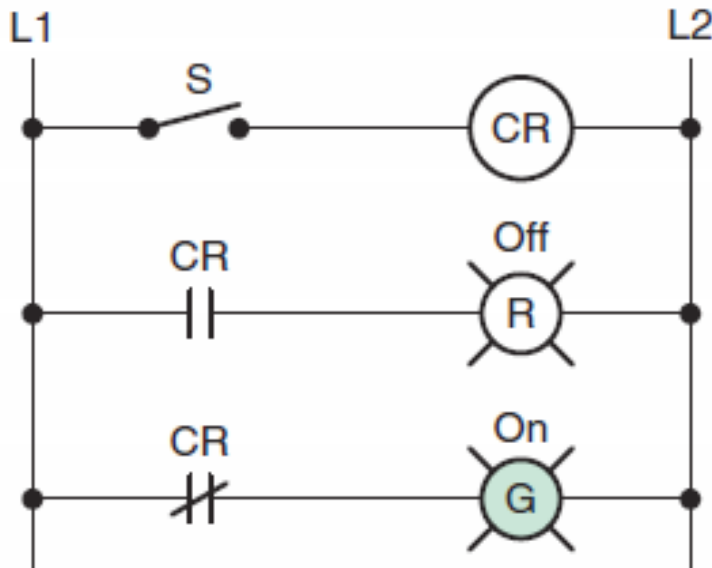


Image Source: Programmable Logic Controllers, 4<sup>th</sup> Ed., McGraw Hill, 2011

# Question 1

**Input Instruction is coil and Output Instruction is contact.**

- a) True**
- b) False**

# PLC Bit Instructions...

When programming PLCs, the following bit instructions are used.

- **Examine If Closed (XIC)**
- **Examine If Open (XIO)**
- **Output Energize (OTE)**

Examine If Closed or ***Examine ON*** instruction is associated with a physical input being set to binary logic **1** with a voltage being present

# PLC Bit Instructions...

- **Examine If Closed (XIC)**  
Examine If Closed or *Examine ON* instruction is associated with a physical input being set to binary logic **1** with a voltage being present
- **Examine If Open (XIO)**  
Examine If Open or *Examine OFF* instruction is associated with a physical input being set to binary logic **0** with a no voltage being present.
- **Output Energize (OTE)**  
Output Energize instruction is associated with a physical output being set to binary logic **1** with a voltage being present.



# PLC Bit Instructions...

- **Examine If Closed (XIC) Bit Instruction**



- **Examine If Open (XIO) Bit Instruction**




- **Output Energize (OTE) Bit Instruction**



Image Source: Programmable Logic Controllers, 4<sup>th</sup> Ed., McGraw Hill, 2011

# PLC Bit Instructions...

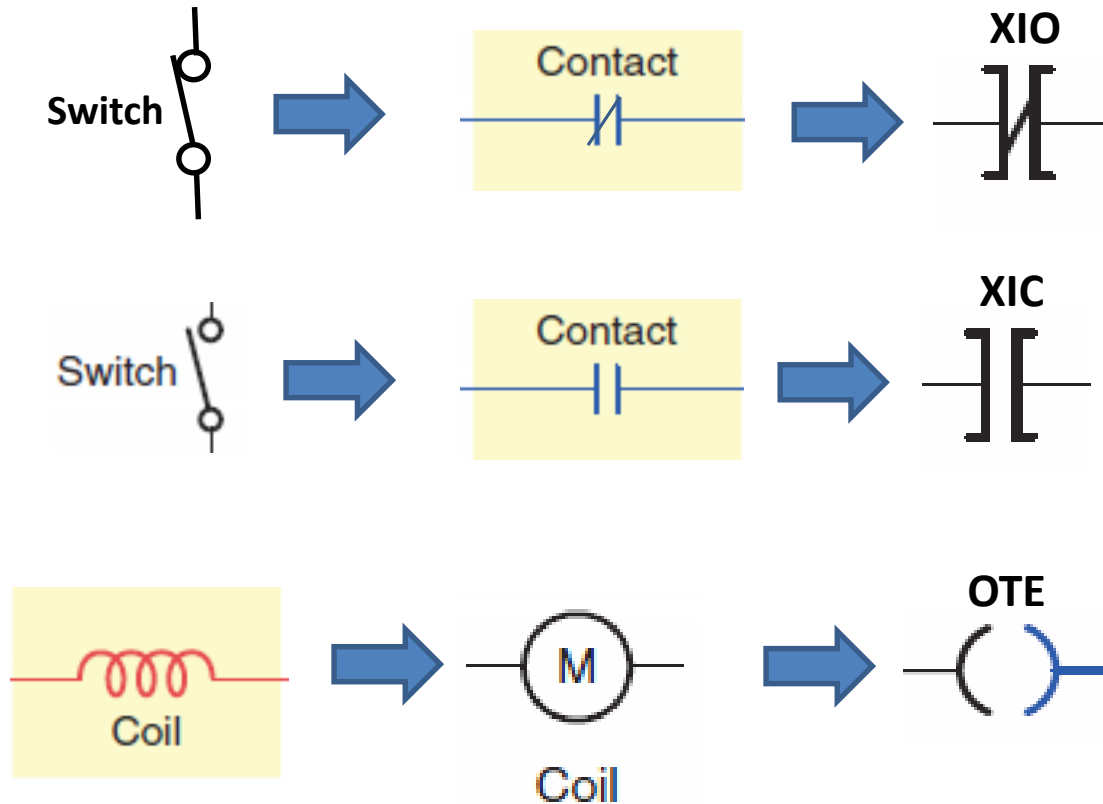

**Relationship between Electronic, Industrial Control Symbols and PLC Bit Instructions**

# PLC Bit Instructions...

## PLC Bit Instructions are arranged in

- A series of logical rungs.
- The logical rungs operate based on the physical input and output binary values.
- The logical rungs are called a Ladder Logic Program.


## Question 2

**A Photoswitch wired to a PLC would use what type of Bit Instruction.**


- a) XIO**
- b) XIC**
- c) a & b**
- d) OTE**
- e) None of the above**

# PLC Bit Instructions...
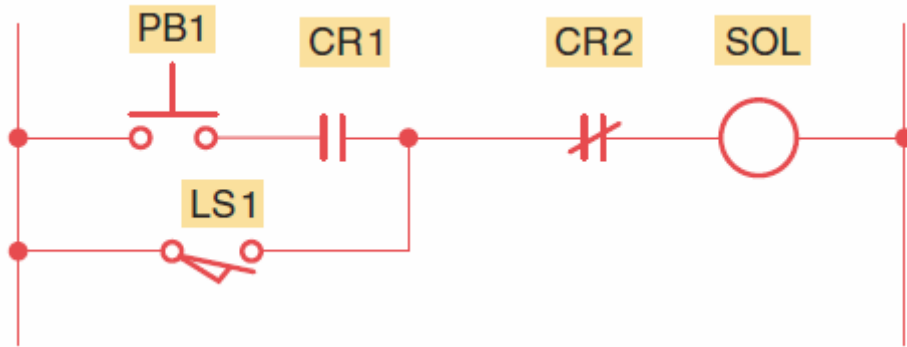
## Comparison of Hardwired Relay Control Circuit with Ladder Logic Program



Hardwired **relay control circuit**

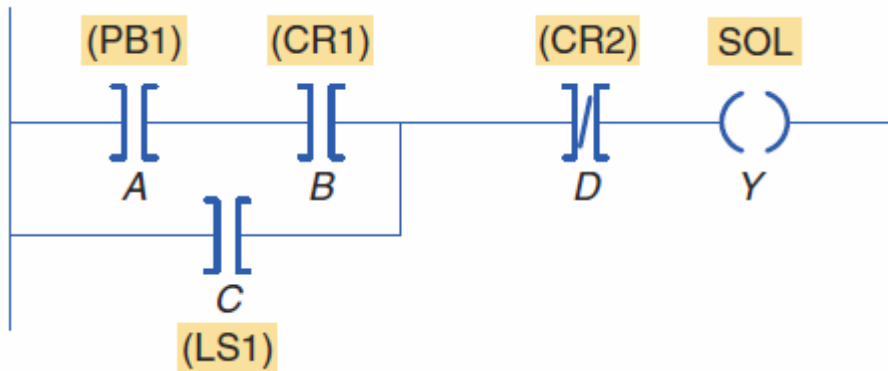

Equivalent **ladder diagram program**

Image Source: Programmable Logic Controllers, 4<sup>th</sup> Ed., McGraw Hill, 2011

# PLC Bit Instructions...

***Ladder Logic*** language is the most commonly used PLC programming language and is designed to mimic hardwired relay logic.

Source: Programmable Logic Controllers, 4<sup>th</sup> Ed., McGraw Hill, 2011

## Question 3

On slide 13, CR2 represents what type of bit instruction.

- a) XIO
- b) XIC
- c) a & b
- d) OTE
- e) None of the above

# Introduction to Basic Logic Gates


***A logic gate* is a circuit with several inputs but only one output that is activated by particular combinations of input conditions.**

Source: Programmable Logic Controllers, 4<sup>th</sup> Ed., McGraw Hill, 2011



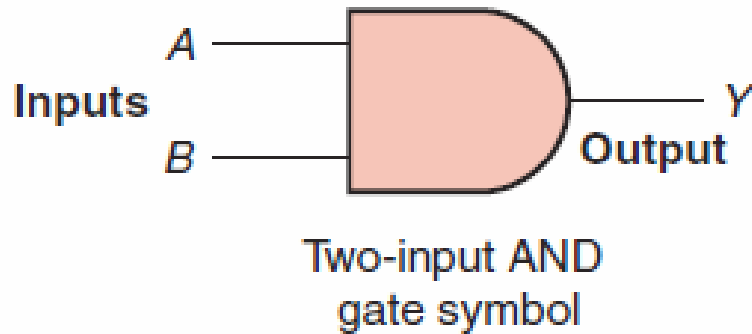
# Introduction to Basic Logic Gates...

An **AND gate** is a device with two or more inputs and one output.



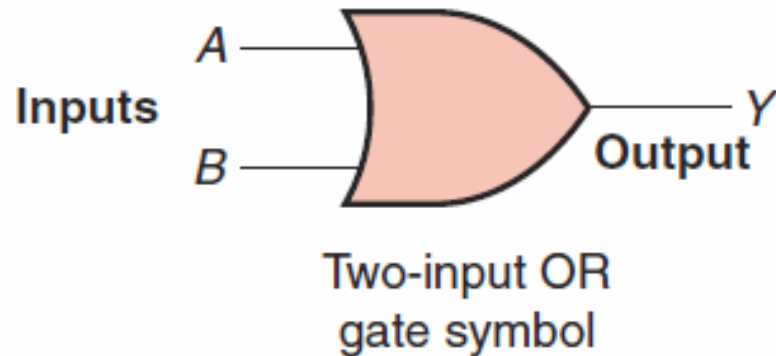
An **OR gate** can have any number of inputs but only one output.



Source: Programmable Logic Controllers, 4<sup>th</sup> Ed., McGraw Hill, 2011
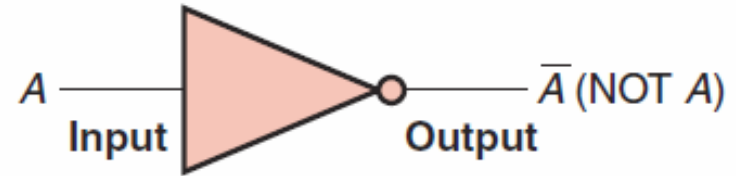
# Introduction to Basic Logic Gates...

The **NOT** function can have **only one** input.




Source: Programmable Logic Controllers, 4<sup>th</sup> Ed., McGraw Hill, 2011

# Introduction to Basic Logic Gates...


## Practical Examples of Logic Gates:

### Logical AND

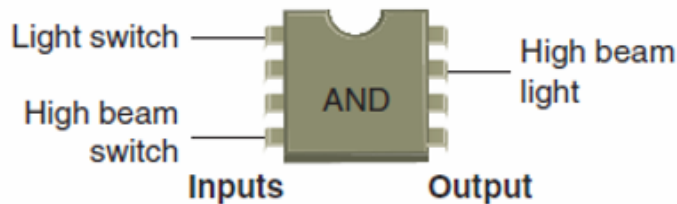

The **high beam light** can be turned on only when the **light switch AND** the **high beam switch** are closed.

### Logical OR

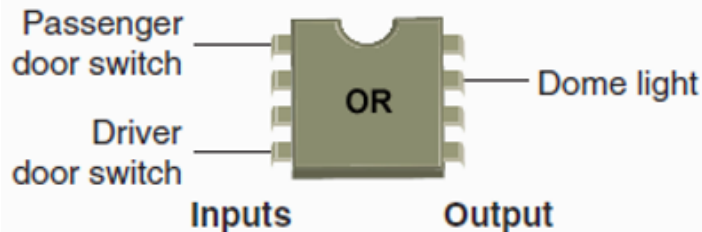

The **dome light** will be turned on whenever the **passenger door switch OR** the **driver door switch** is activated.

# Question 4

**Provide a practical example of device or system that performs the NOT Function.**


# Setting Up the Velocio "vBuilder" Software (Ladder Logic)



Reference


<http://velocio.net/vbuilder/>
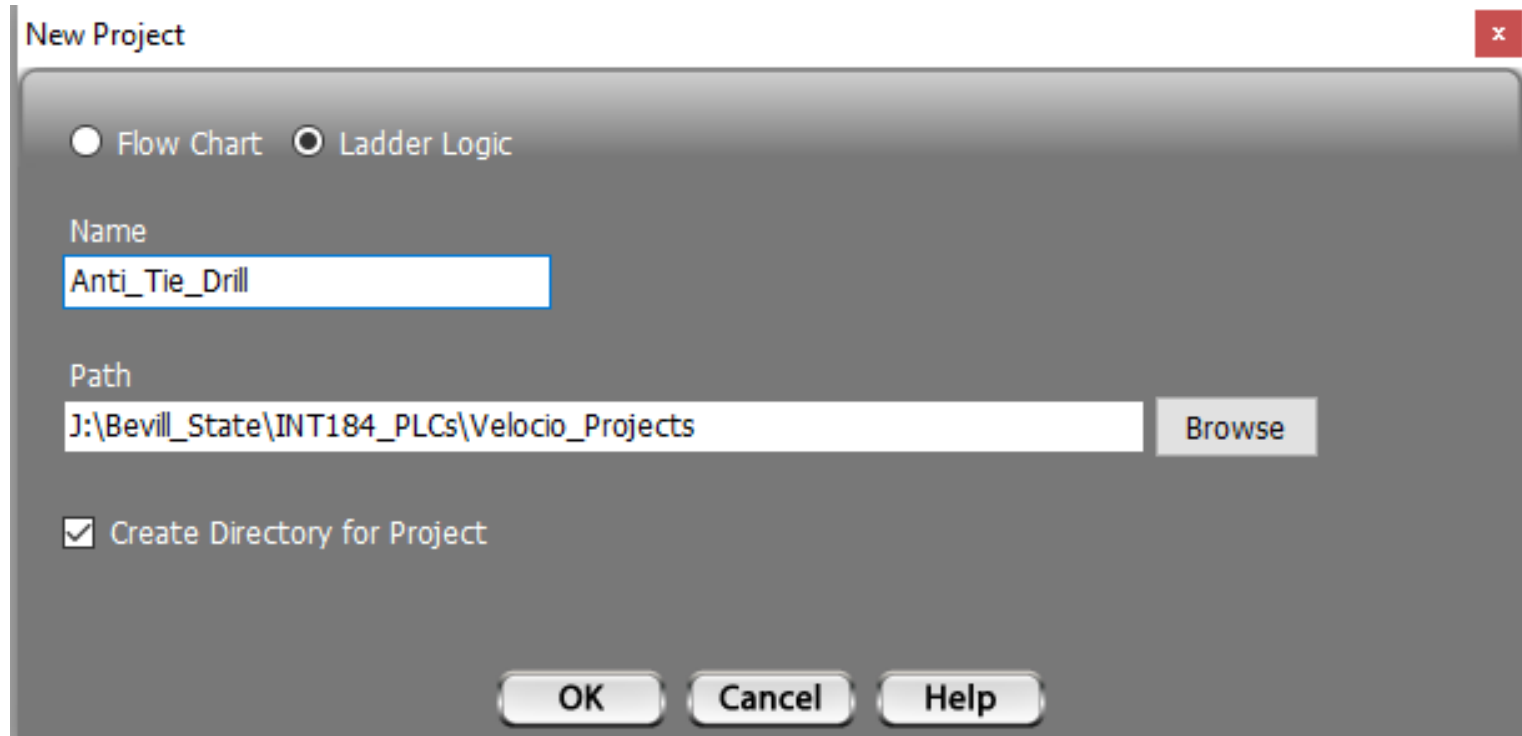
# Setting Up the Velocio "vBuilder" Software...




**Creating the Ladder Logic program for a Anti-Tie Down Controller.**
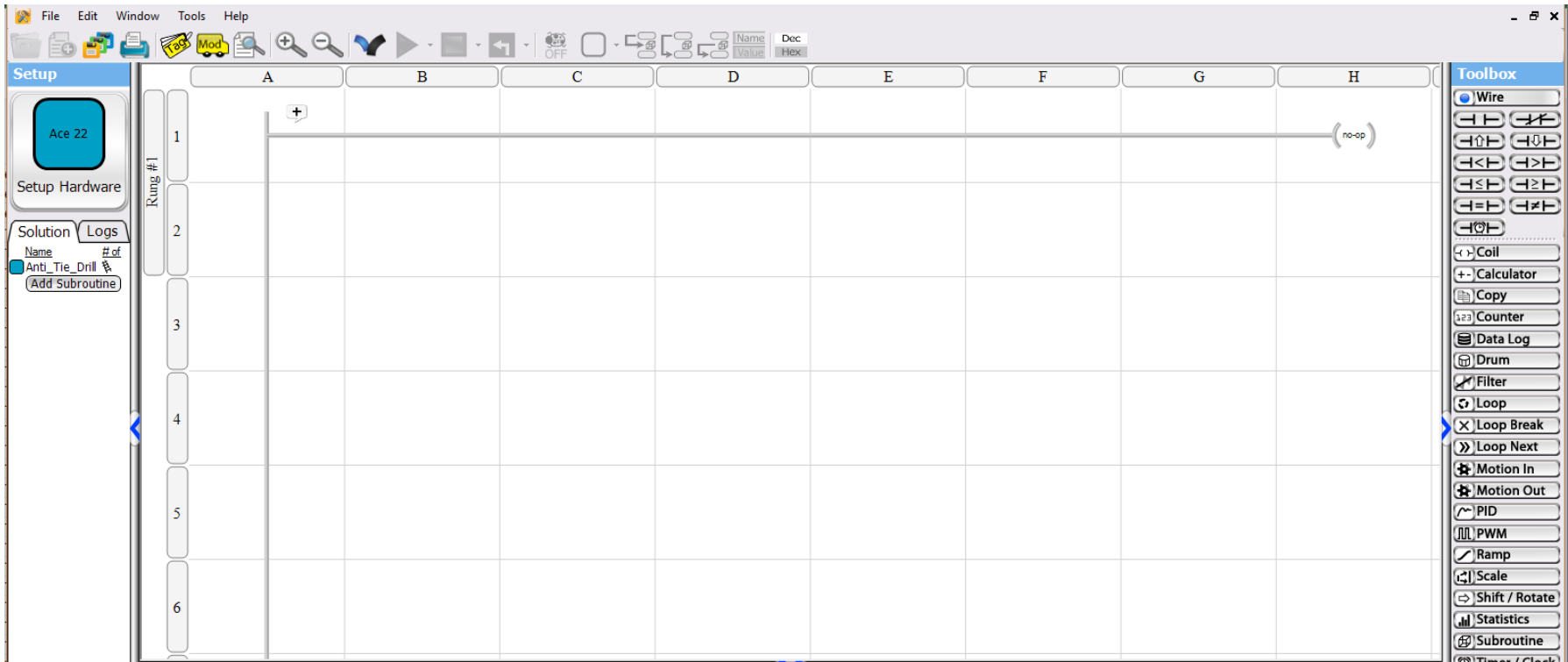
# Setting Up the Velocio "vBuilder" Software...



The Ace 22 PLC Hardware setup is complete.
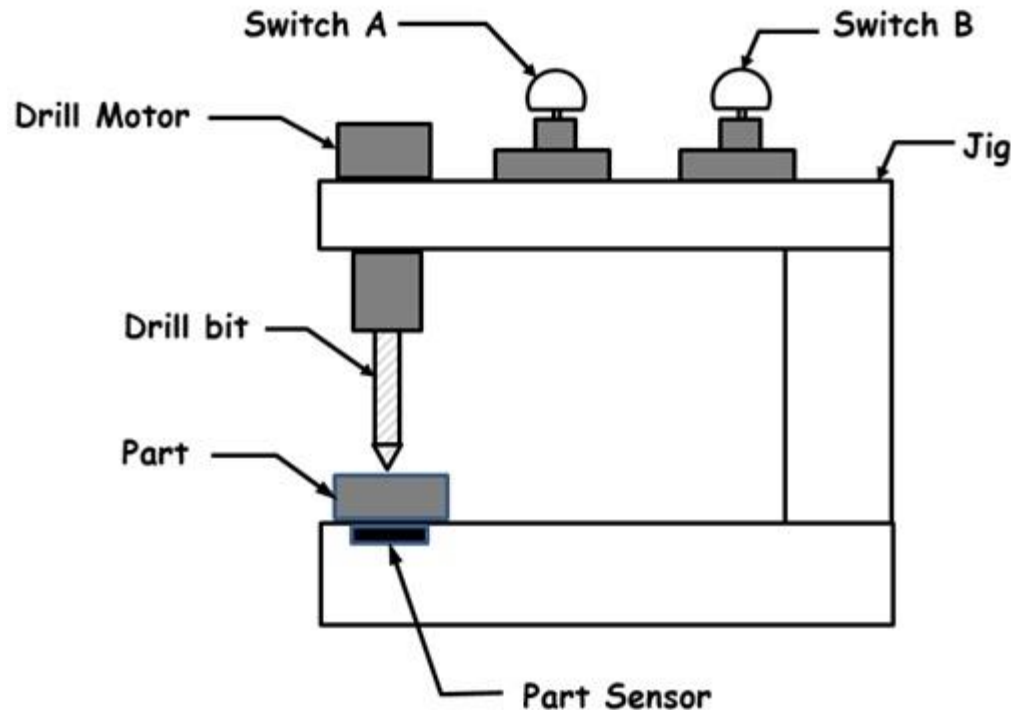
# Developing a PLC Ladder Logic Program for a Small Drill



Small Drill Press with Anti-Tie Down Controls




# Developing a PLC Ladder Logic Program for a Small Drill...

Input / Output	Name	Signal	Debounce (ms.)	Used	Modbus
<b>Input bit</b>	PART_SENSOR	B1	0	<input type="checkbox"/>	<input type="checkbox"/>
Input i16	SWITCH_A	B2	0	<input type="checkbox"/>	<input type="checkbox"/>
Input Float	SWITCH_B	B3	0	<input type="checkbox"/>	<input type="checkbox"/>
Output bit	InBitB4	B4	0	<input type="checkbox"/>	<input type="checkbox"/>
Output ui16	InBitB5	B5	0	<input type="checkbox"/>	<input type="checkbox"/>
Register	InBitB6	B6	0	<input type="checkbox"/>	<input type="checkbox"/>
bit	InBitC1	C1	0	<input type="checkbox"/>	<input type="checkbox"/>
ui8	InBitC2	C2	0	<input type="checkbox"/>	<input type="checkbox"/>
i16	InBitC3	C3	0	<input type="checkbox"/>	<input type="checkbox"/>
ui16	InBitC4	C4	0	<input type="checkbox"/>	<input type="checkbox"/>
i32	InBitC5	C5	0	<input type="checkbox"/>	<input type="checkbox"/>
Float	InBitC6	C6	0	<input type="checkbox"/>	<input type="checkbox"/>


**Creating Tags PART\_SENSOR, SWITCH\_A, AND SWITCH\_B**
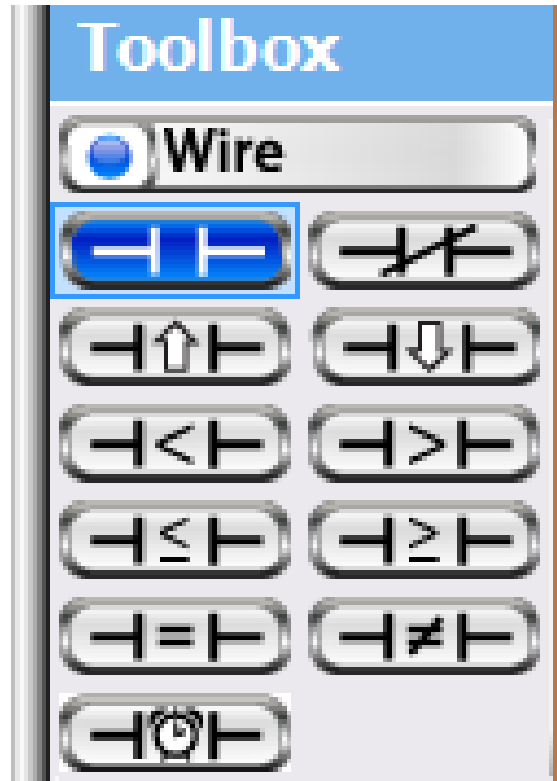
# Developing a PLC Ladder Logic Program for a Small Drill...




Three Normally Open Contacts (XIC) will be used in the program.
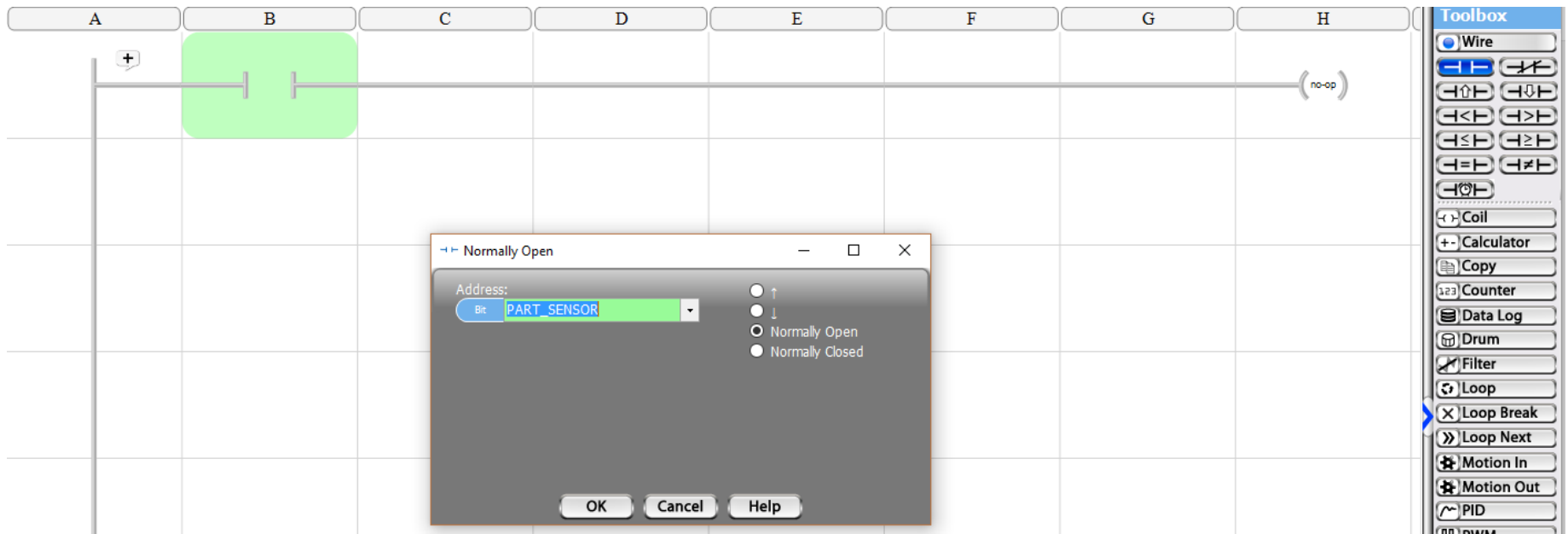
# Developing a PLC Ladder Logic Program for a Small Drill...




Select the PART\_SENSOR Tag for the bit instruction.
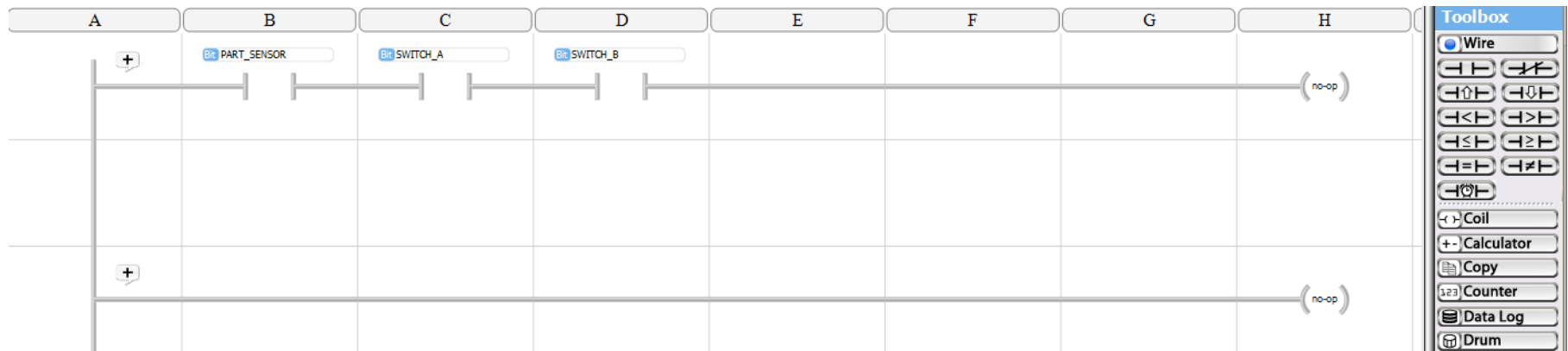
# Developing a PLC Ladder Logic Program for a Small Drill...




**Select the remaining XIC bit instructions with their appropriate Tags and place them on the ladder logic rung.**
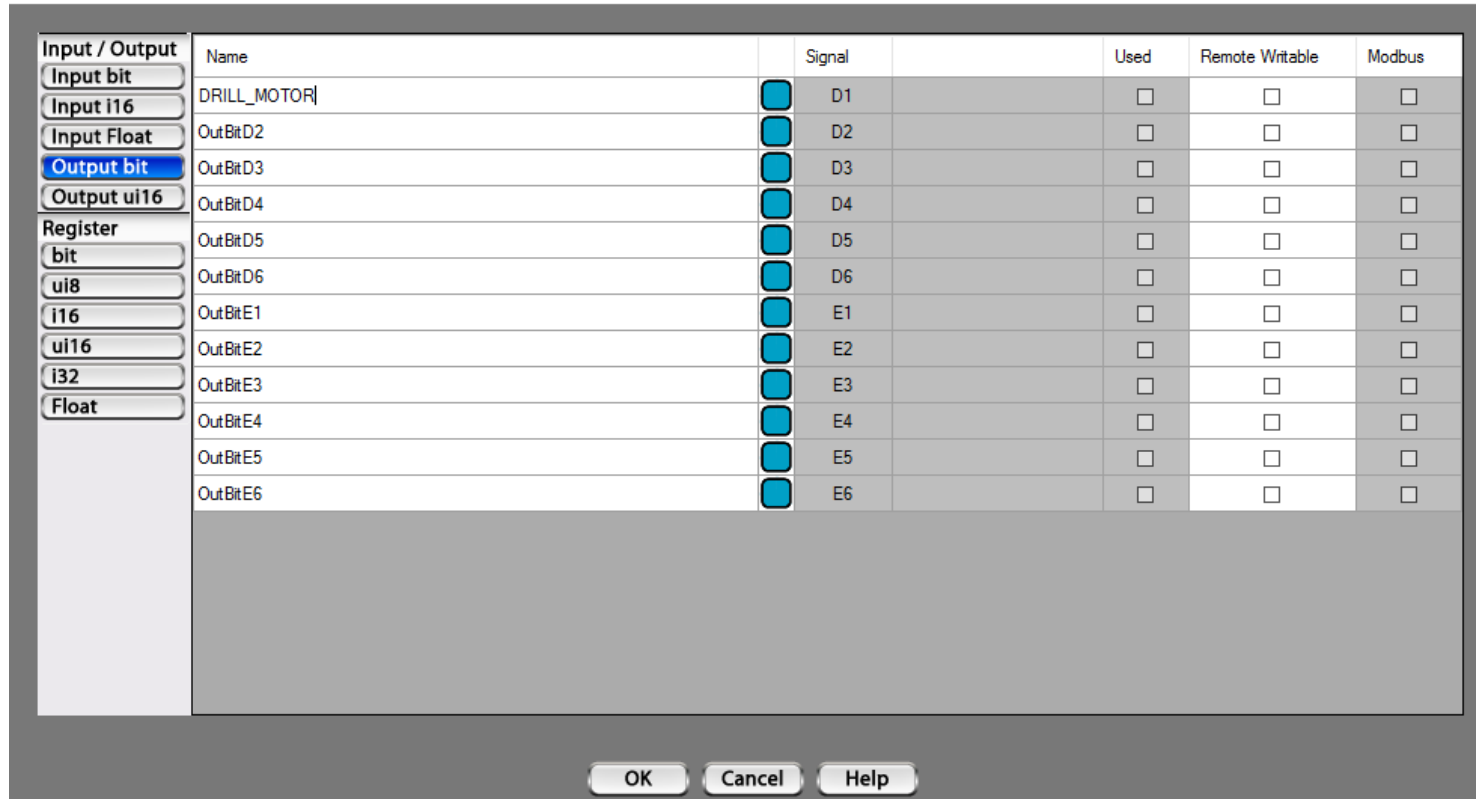
# Developing a PLC Ladder Logic Program for a Small Drill...




## Creating Tag DRILL\_MOTOR
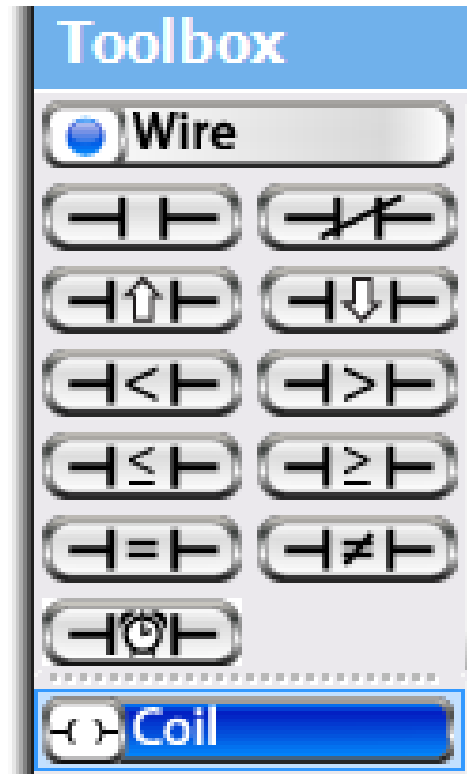
# Developing a PLC Ladder Logic Program for a Small Drill...




One coil (OTE) will be used in the program.
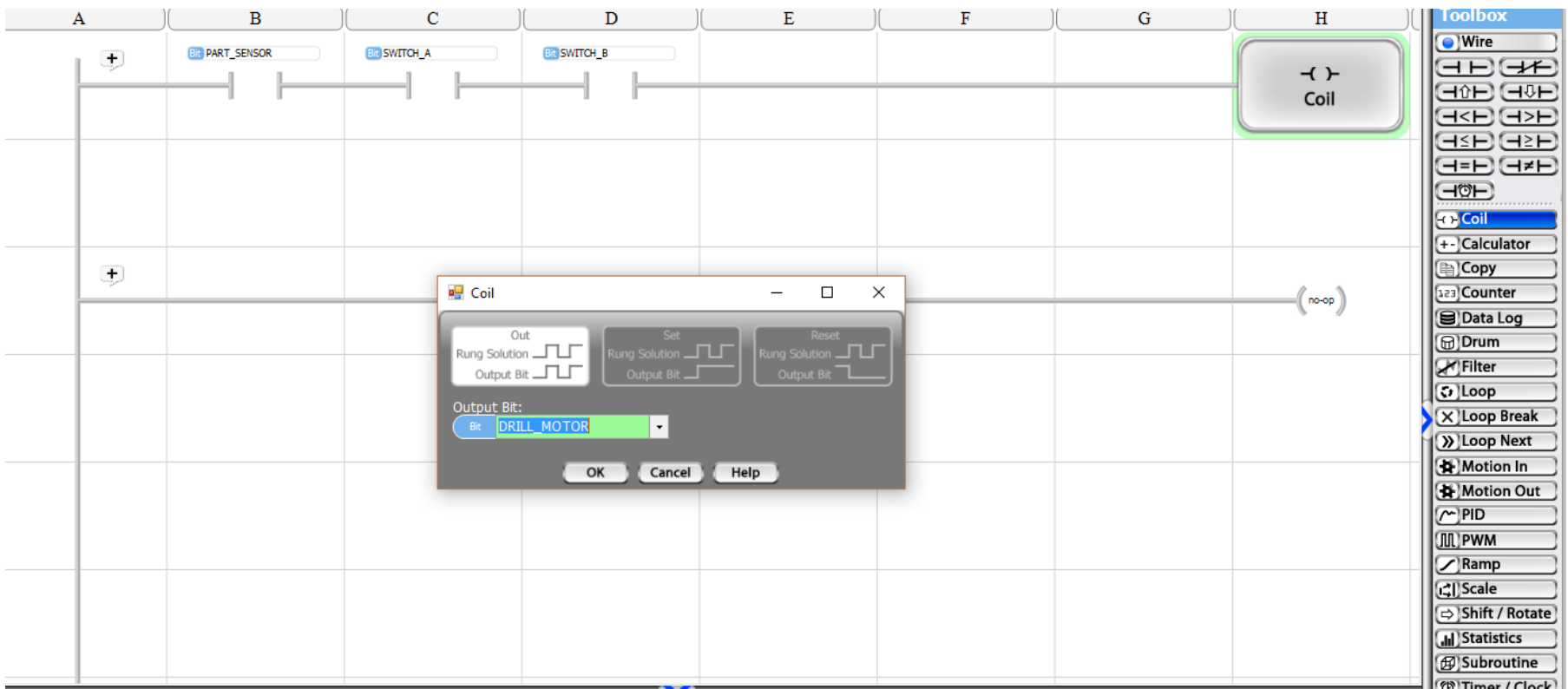
# Developing a PLC Ladder Logic Program for a Small Drill...



Select the DRILL\_MOTOR Tag for the OTE bit instruction.
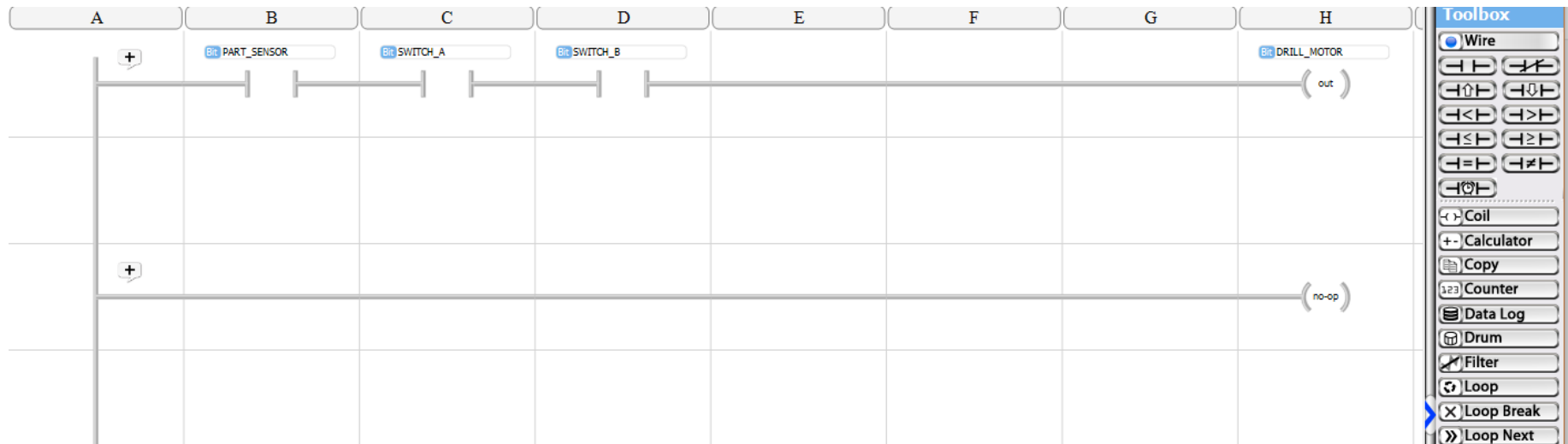
# Developing a PLC Ladder Logic Program for a Small Drill...




The Anti Tie Down Controller PLC Ladder Logic is completed.




# Question 5

**What basic logic function will be performed by the Anti Tie down Controller?**
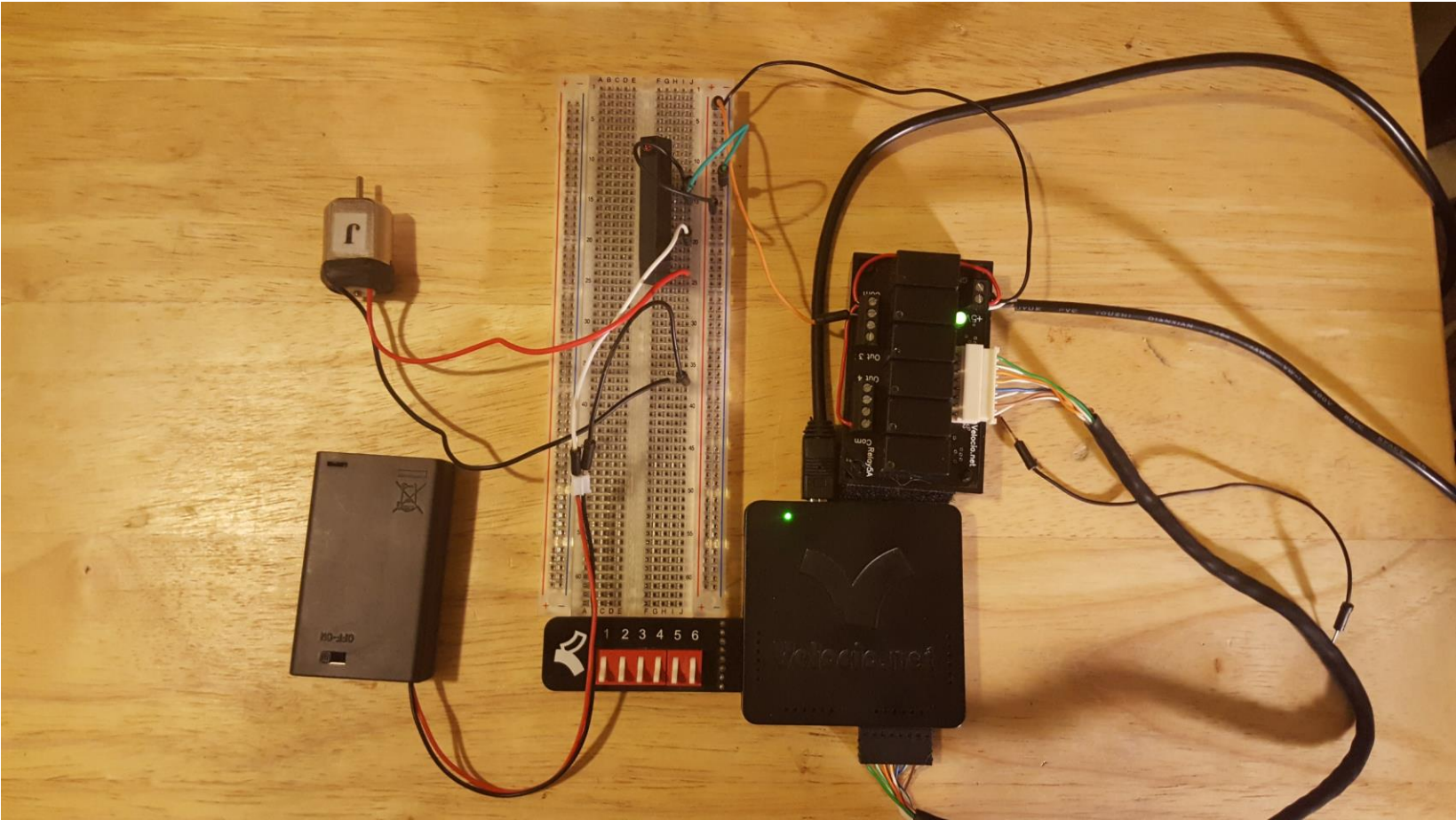
# Hands-On Project: Bit Instruction Based Logic Controller


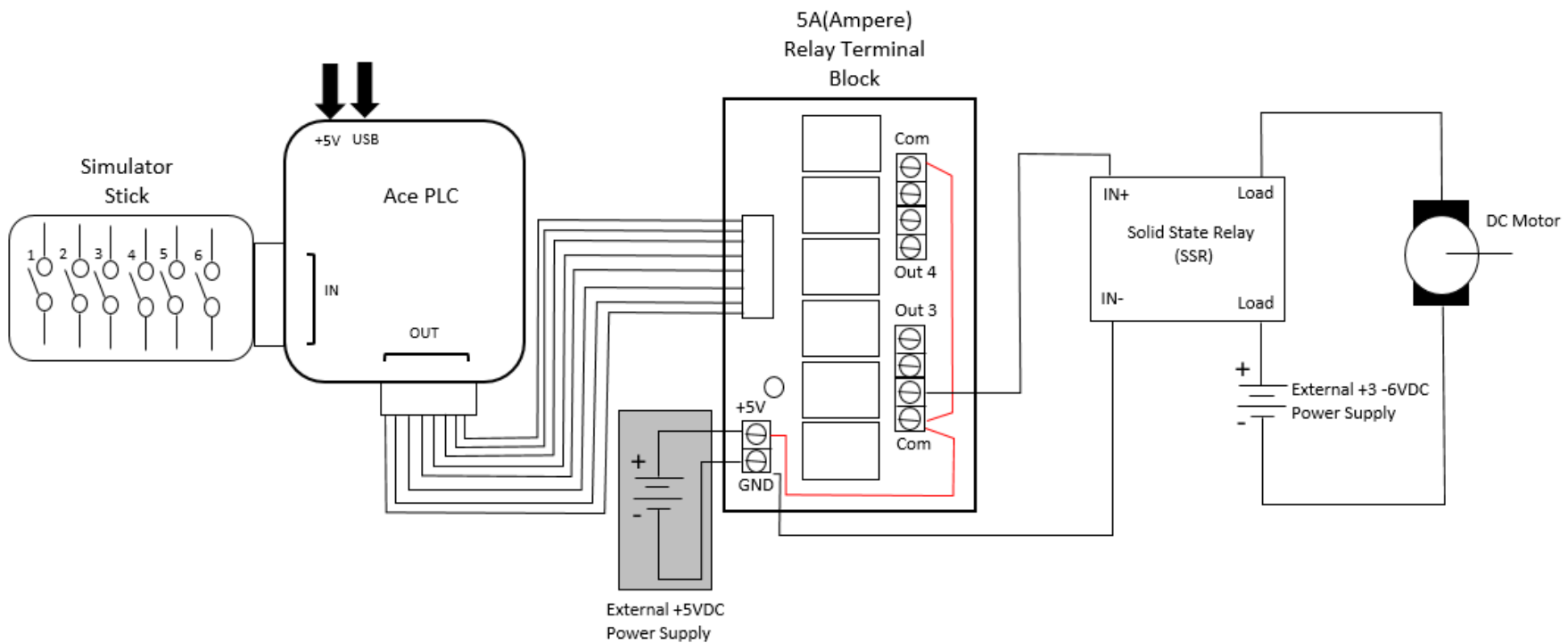
# Hands-On Project: Bit Instruction Based Logic Controller



Electrical Wiring Diagram

# Solid State Relay (SSR)

## FAQs

**SSRs are widely used in industrial control circuits for operating electric heaters, solenoid, motor, and lighting fixtures.**

### **Advantages.**

- small in size.
- fast switching speeds.
- can isolate low voltage/current circuits from high voltage/current electrical loads.

# Solid State Relay (SSR)

## FAQs...

### Disadvantage.

- small leakage that occurs when the SSR is turned off (de-energize). Device stays on (energize)


### SSR Types.

- AC or DC devices (input/output signals).
- Use an internal optical emitter –detector pair for isolating low voltage/current circuits from high voltage/current loads.
- BJTs, SCRs, or Triacs are commonly used as the switching components for output control.

# Solid State Relay (SSR)

## FAQs...
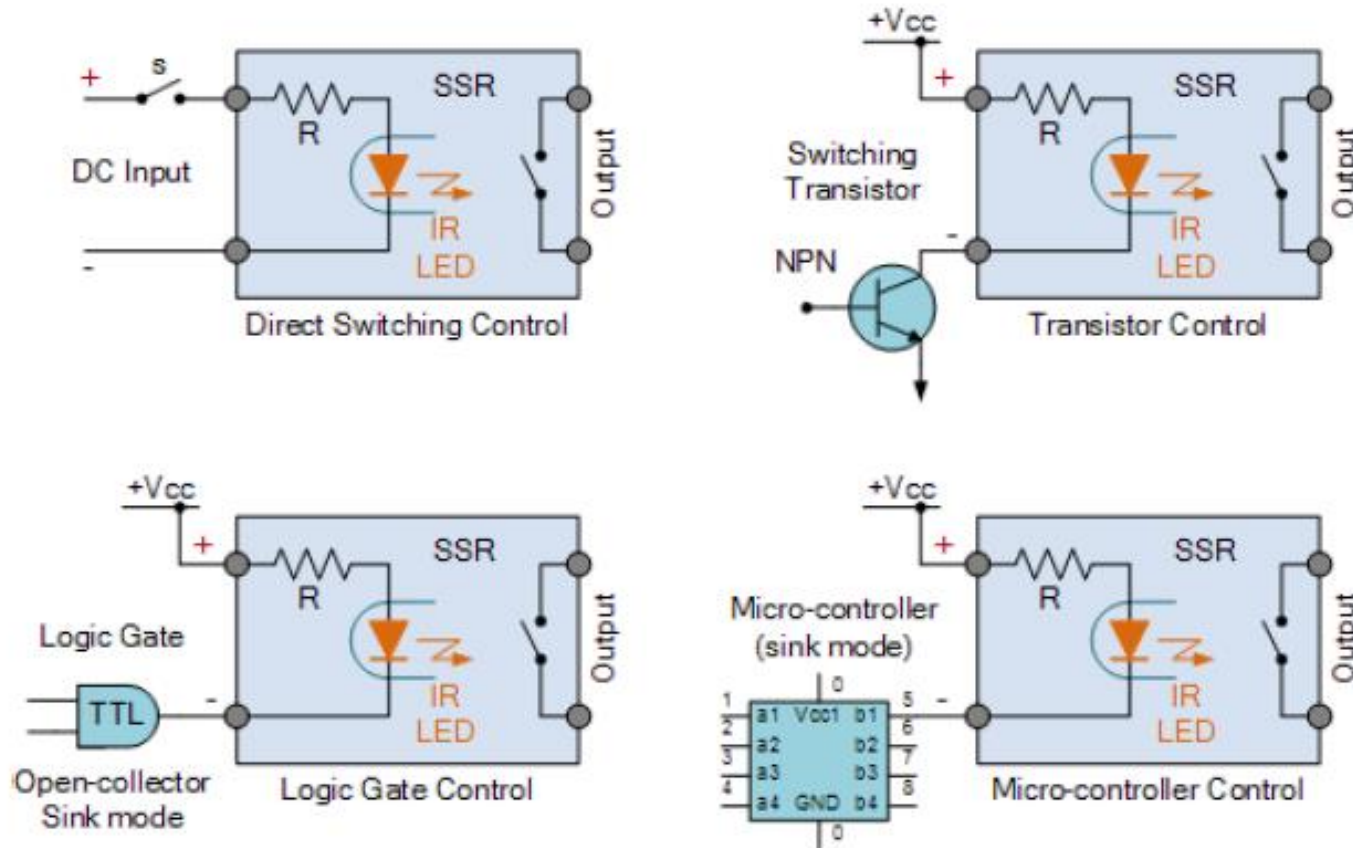
### Solid State Relay DC Input Control Circuits:




<http://www.electronics-tutorials.ws/power/solid-state-relay.html>


# Solid State Relay (SSR) FAQs...

**KSD203AC3 SSR:**

**LED Indicator**

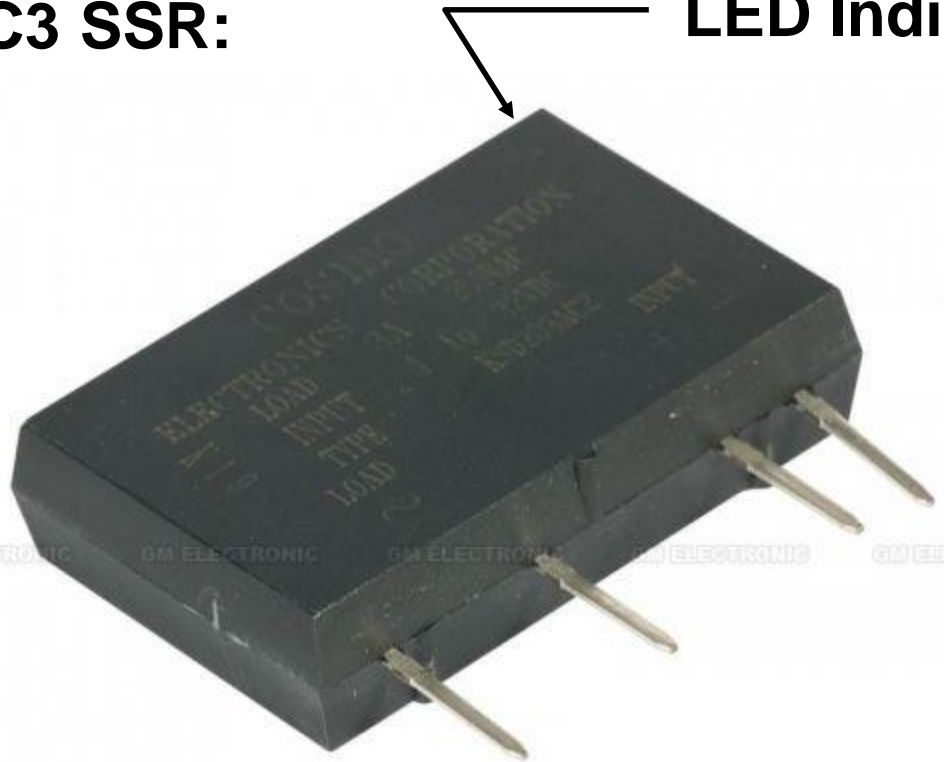

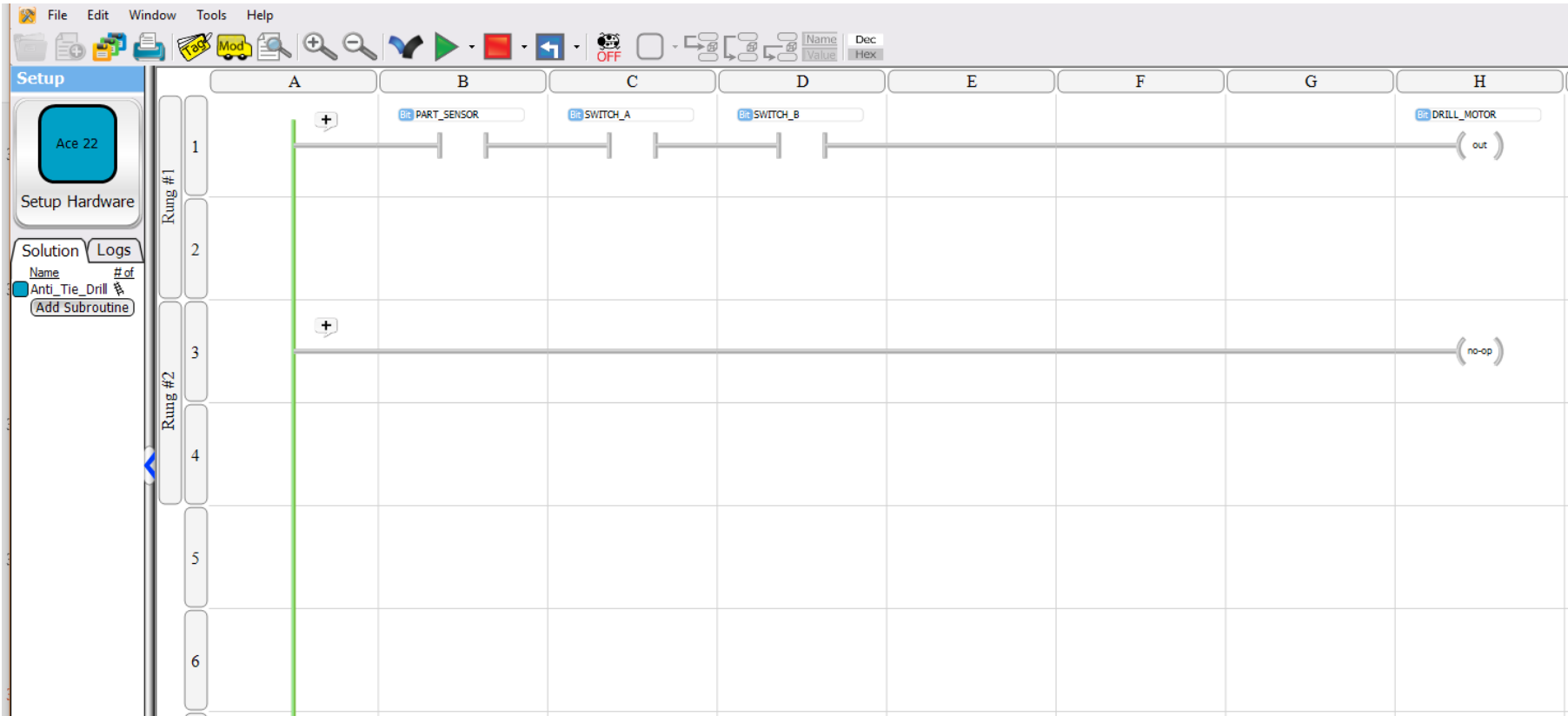
# Running the Anti Tie Down Controller Ladder Logic Program



Click the “Green” run button to operate the Anti Tie Down Controller with the Simulator switch.


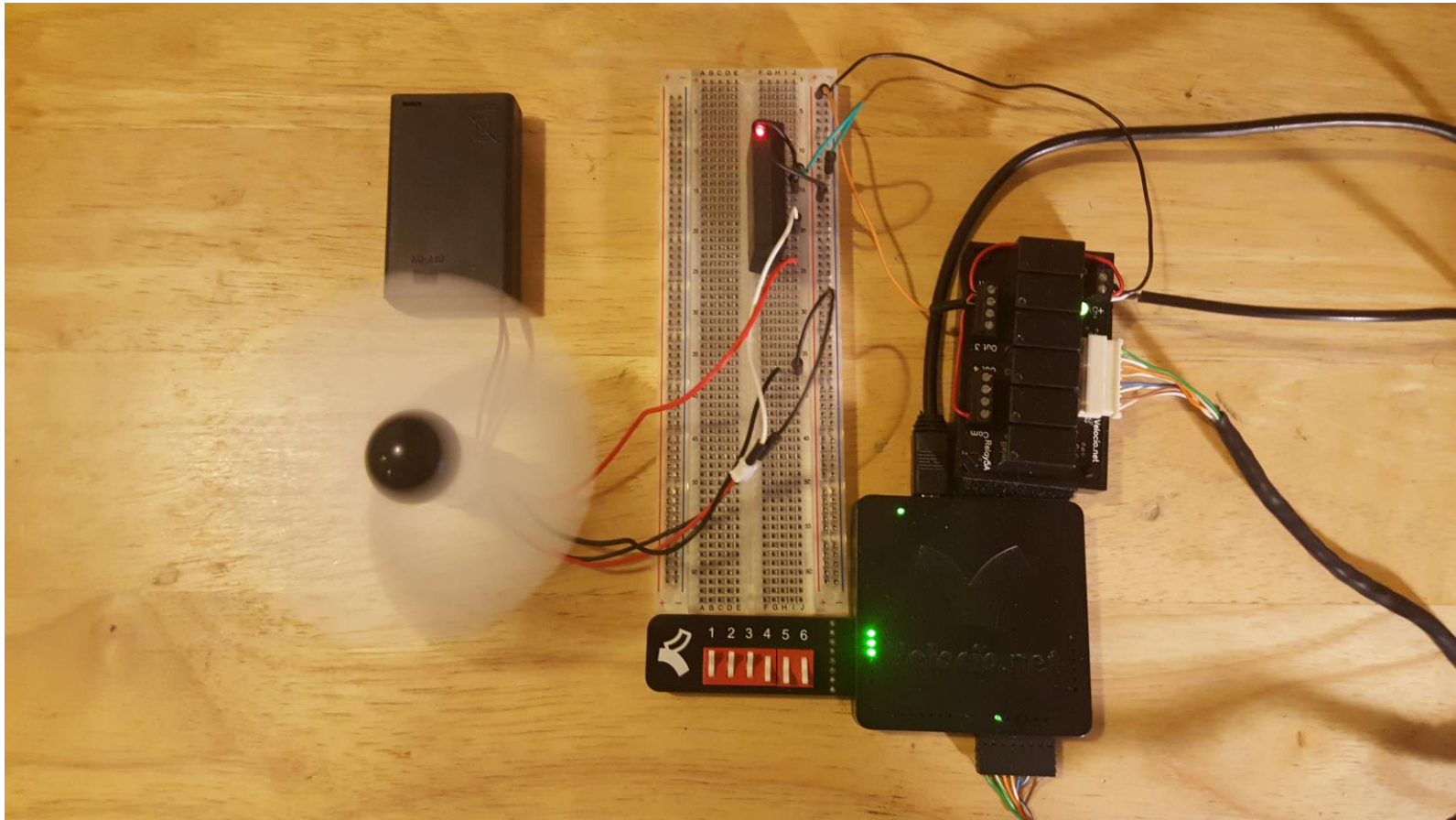
# Running the Anti Tie Down Controller Ladder Logic Program



**Anti-Tie Down Controller in operation!**

# Question 6

**What disadvantage is presented by a SSR?**