
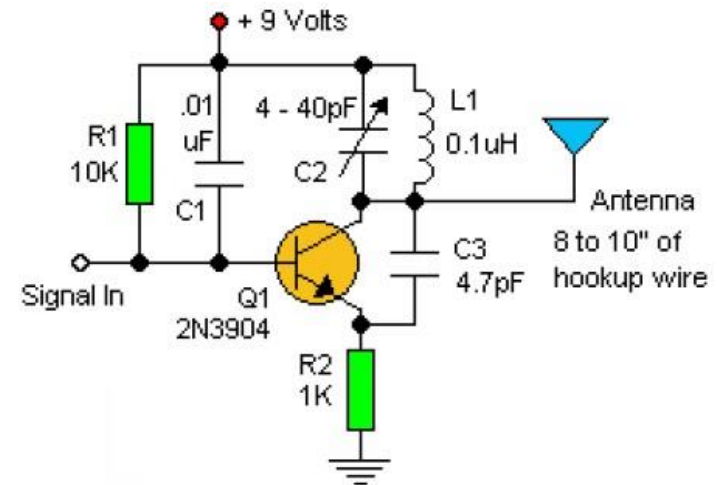
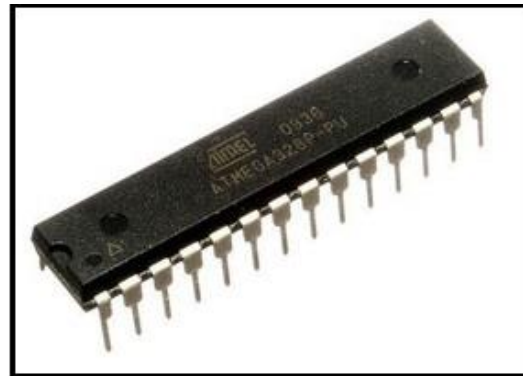



Building Wireless Interfaces for Microcontrollers

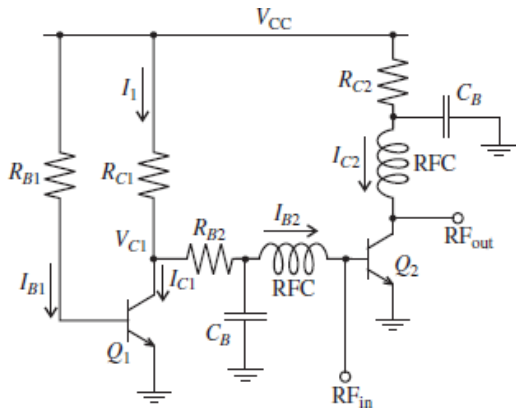Class 1: Traditional RF Circuits for Microcontrollers



May 22, 2017
Don Wilcher

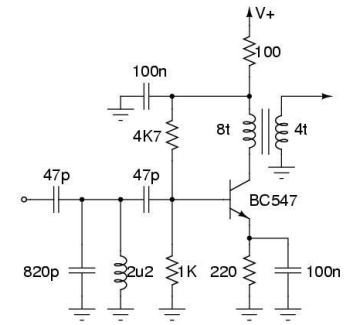Traditional RF Circuits for Microcontrollers





Topics

- What is an RF Amplifier?
- RF Amplifier Circuit Examples
- RF Modules and Examples
- Hands-On Project: A Wireless 7 Segment LED Display Controller



What is an RF Amplifier?

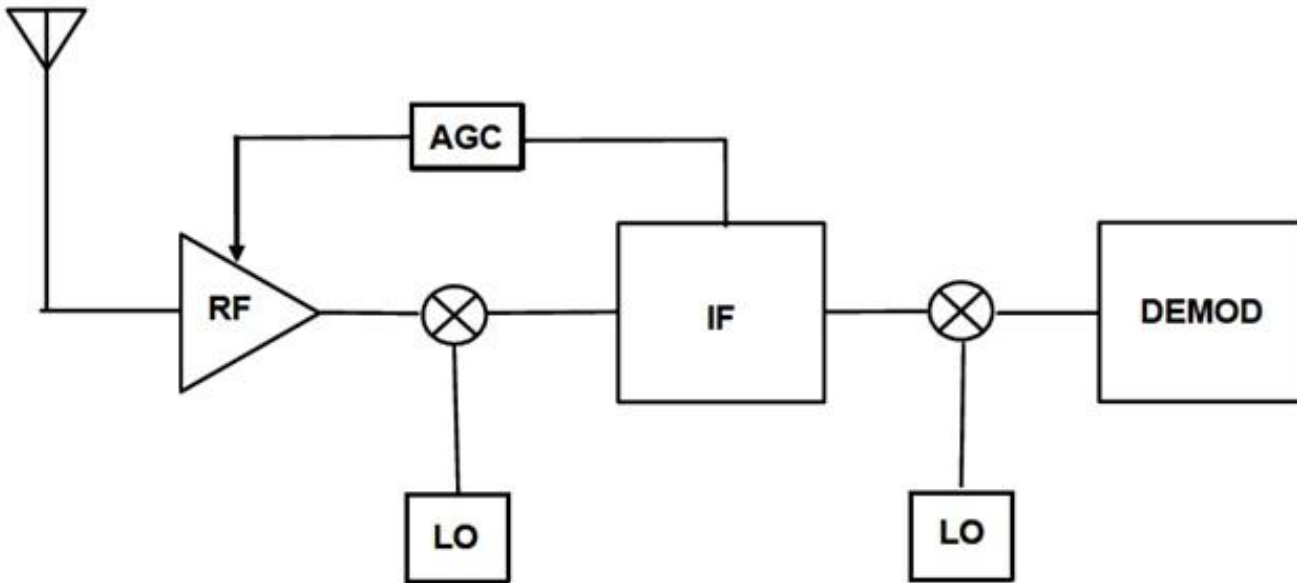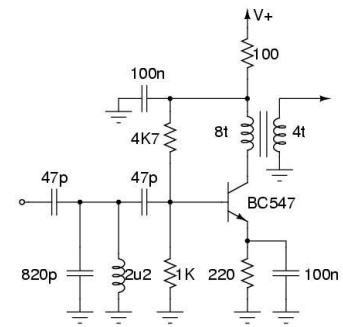- A Tuned Amplifier
- Amplifies High-Frequency Signals
- Used in radio communications



Superheterodyne Receiver Block Diagram

RF Amplifier Circuit Examples

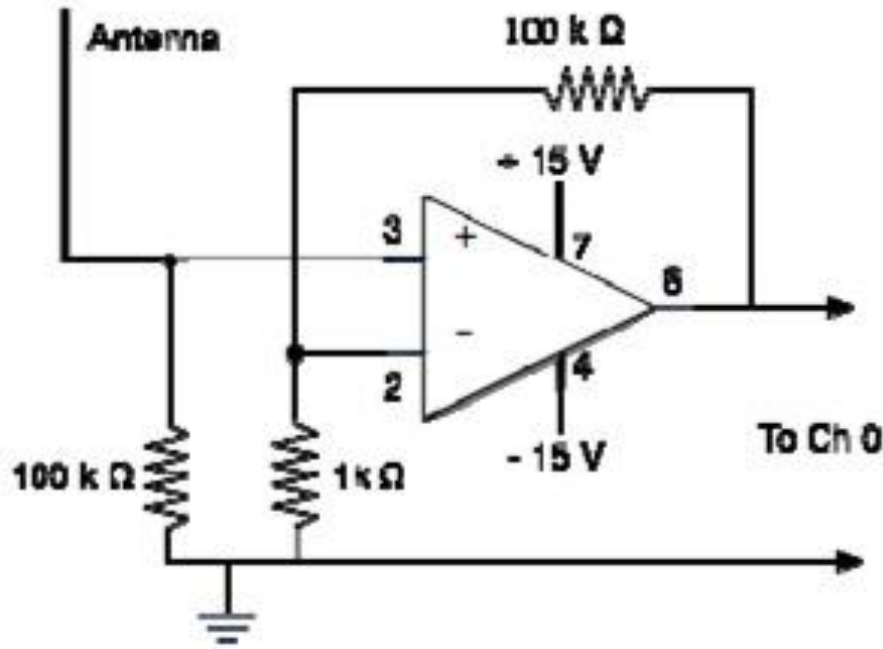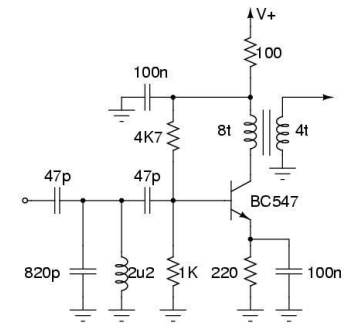

741 Operational Amplifier-RF High Gain Amplifier



Source:

http://download.ni.com/pub/devzone/tut/lab9_wireless_comms.pdf

Question 1

What known radio receiver technology uses an RF Amplifier?

RF Amplifier Circuit Examples...

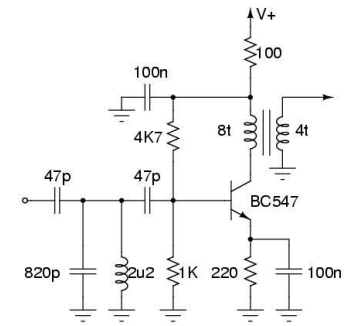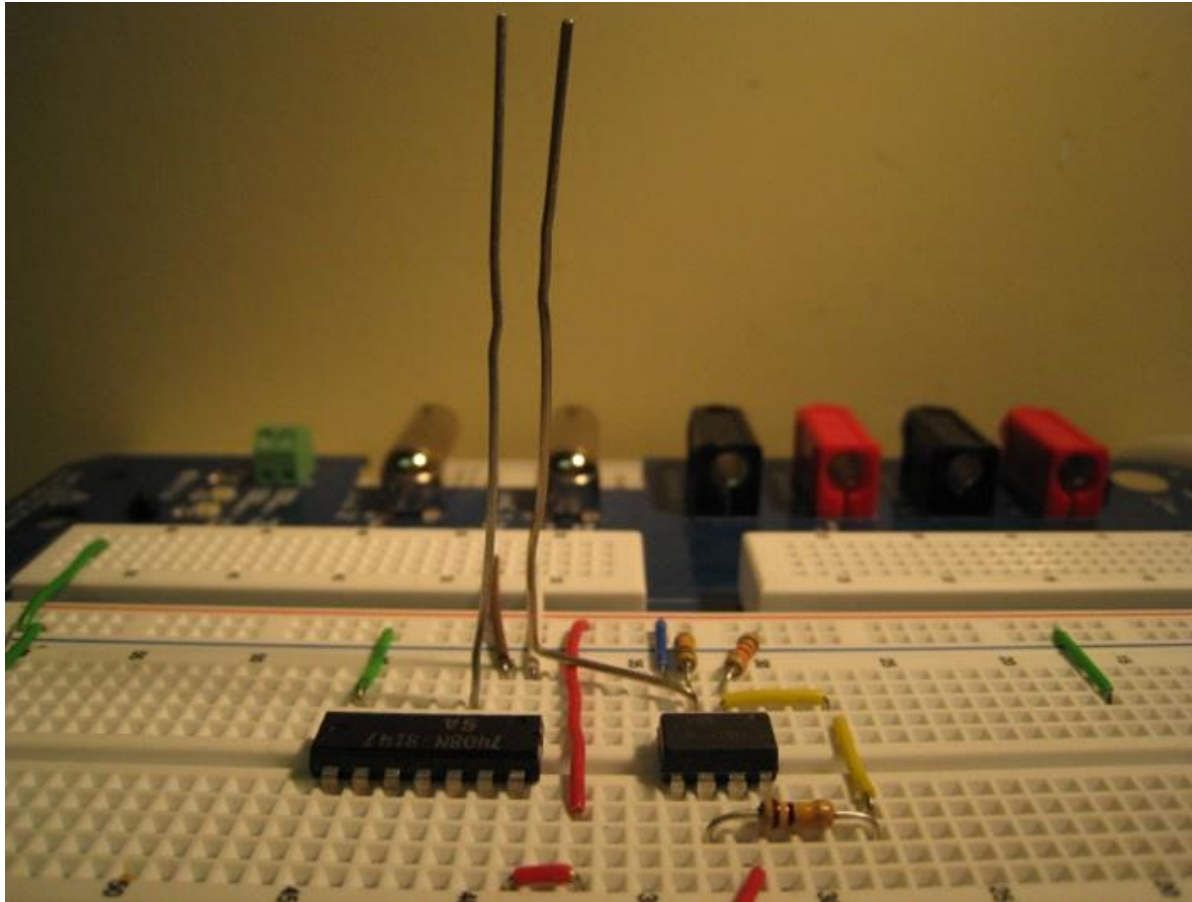


741 Operational Amplifier-RF High Gain Amplifier: Test Circuit Lab Setup


Source:

http://download.ni.com/pub/devzone/tut/lab9_wireless_comms.pdf

RF Amplifier Circuit Examples...

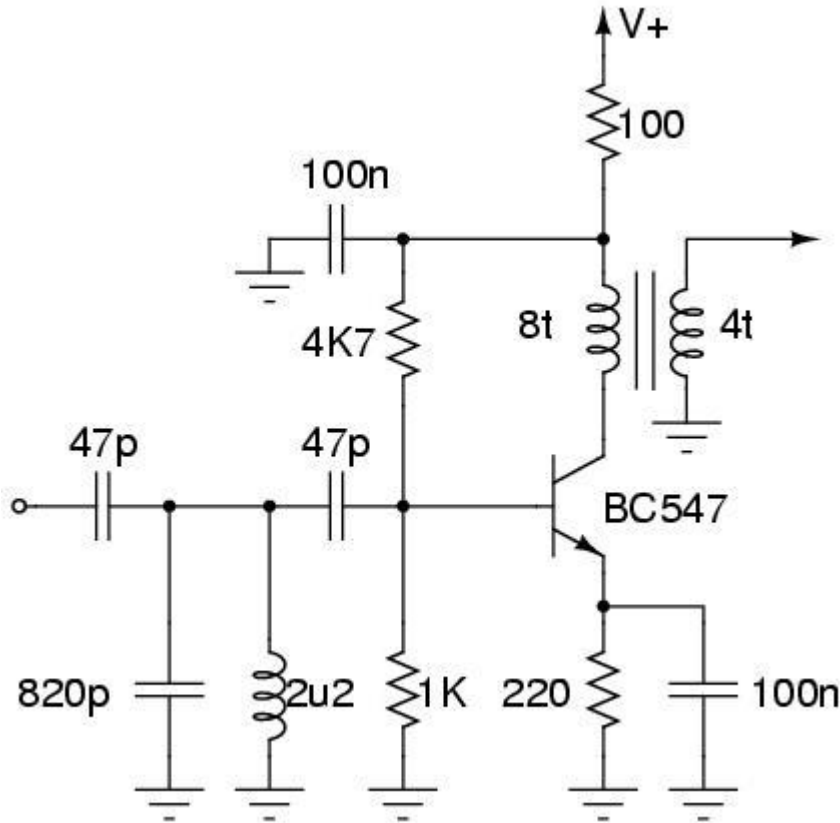

RF Front End Amplifier

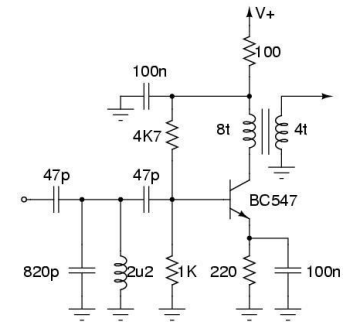

Source:



<http://www.vk2zay.net/article/46>

Question 2

A Tuned Amplifier is a key attribute of a RF Amplifier.

- a) True**
- b) False**

RF Amplifier Circuit Examples...

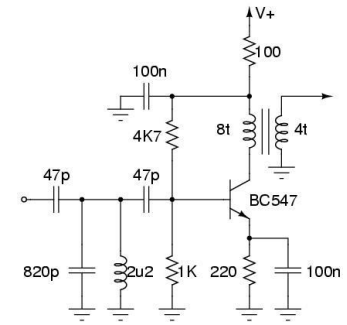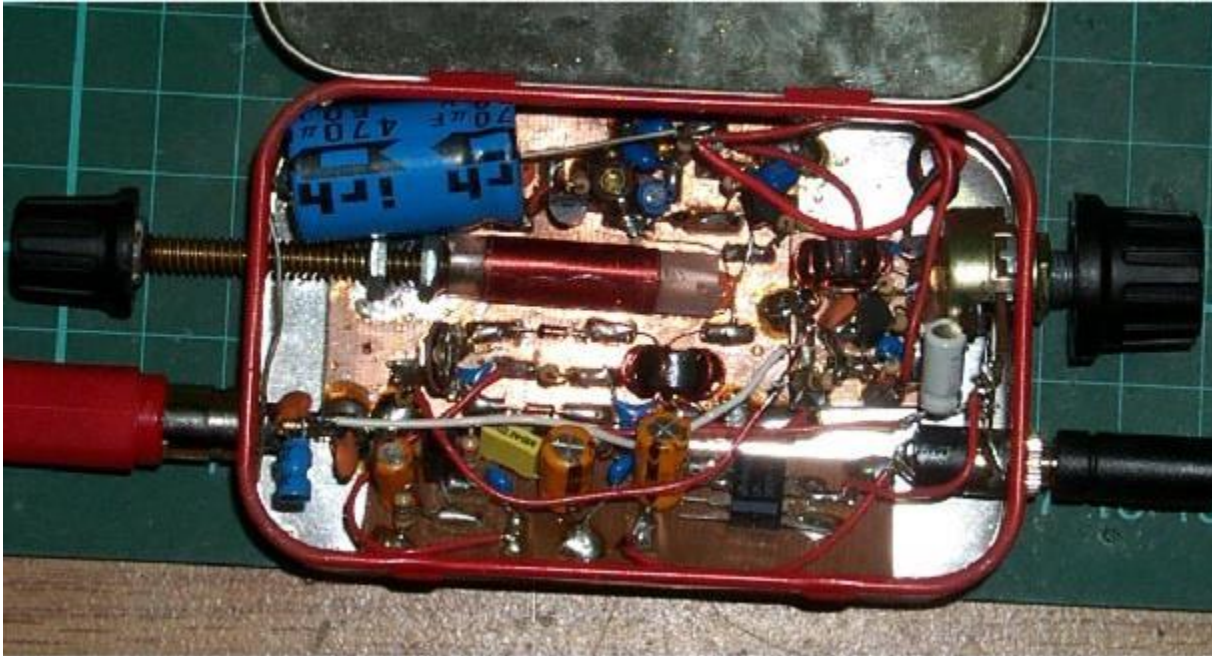


Complete PTO (Power Transmitter Output) VFO (Variable Frequency Oscillator) Receiver

Source:

<http://www.vk2zay.net/article/46>

RF Modules and Examples...

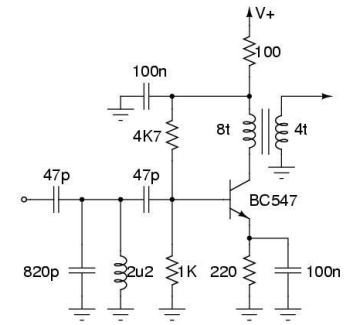


Simple RF T4 and L4 Receivers:

Simple RF Receivers provide the following features.

- There's no programming
- No configuring
- No addressing
- Receiver operates from 5-10VDC voltage supply

RF Modules and Examples...

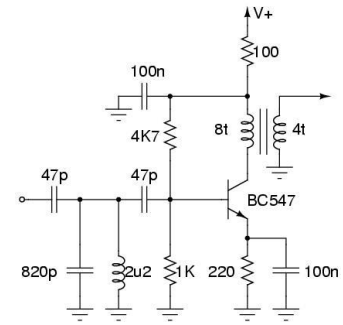

Simple RF T4 and L4 Receivers:


- The T4 Toggle Receiver – alternates output switching.

Example: Activate A output - goes High,
Activate A output again – goes Low.


- The L4 Latch Receiver – output sequencing

Example: Activate A output – goes High,
Activate A output again – goes Low, B output
goes High.

RF Modules and Examples...

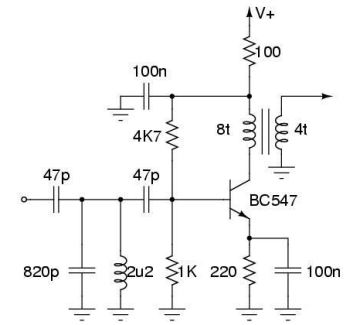



315 MHz Receiver Module

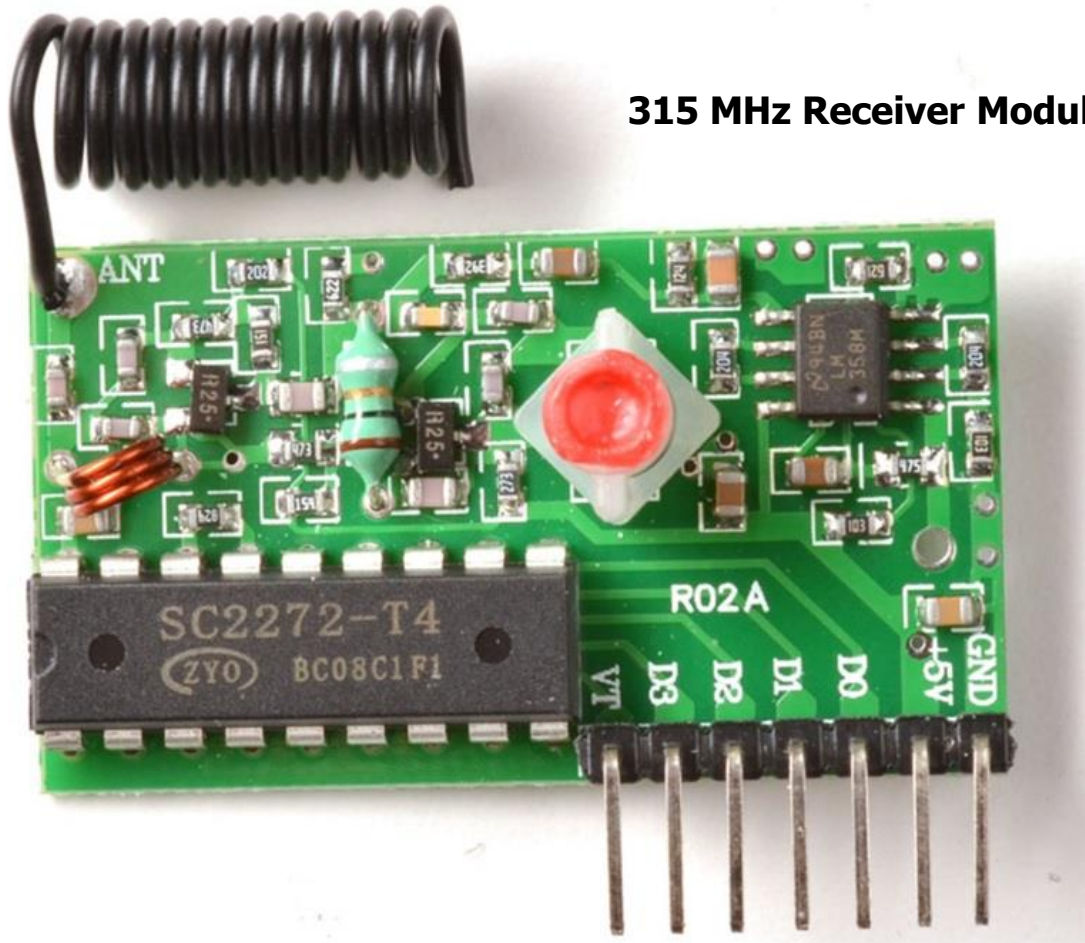

Source:

<https://www.adafruit.com/product/1097>

RF Modules and Examples...

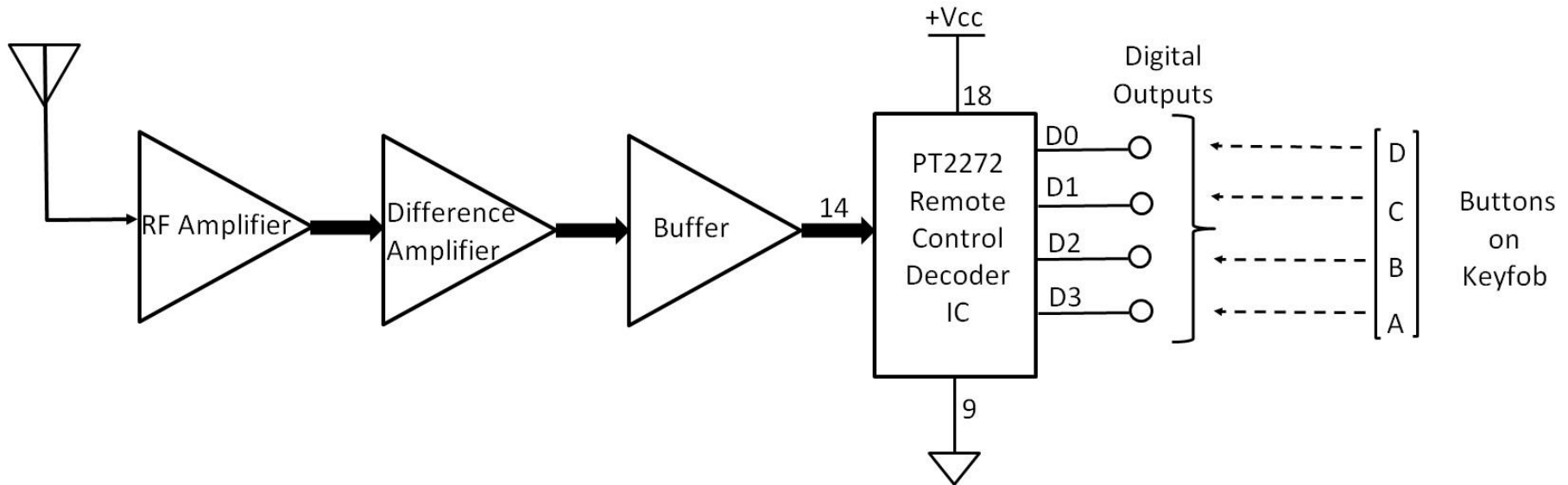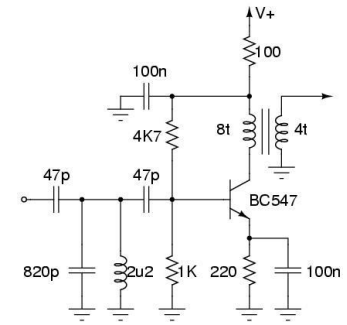


315 MHz Receiver Module: Block Diagram

Question 3

What 315 MHz receiver module latches its digital output pins?

RF Modules and Examples...

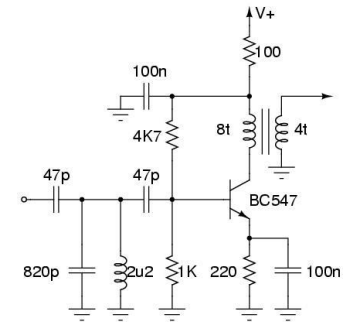

315 MHz Receiver Key Fob





Source:

<https://www.adafruit.com/product/1095>



RF Modules and Examples...

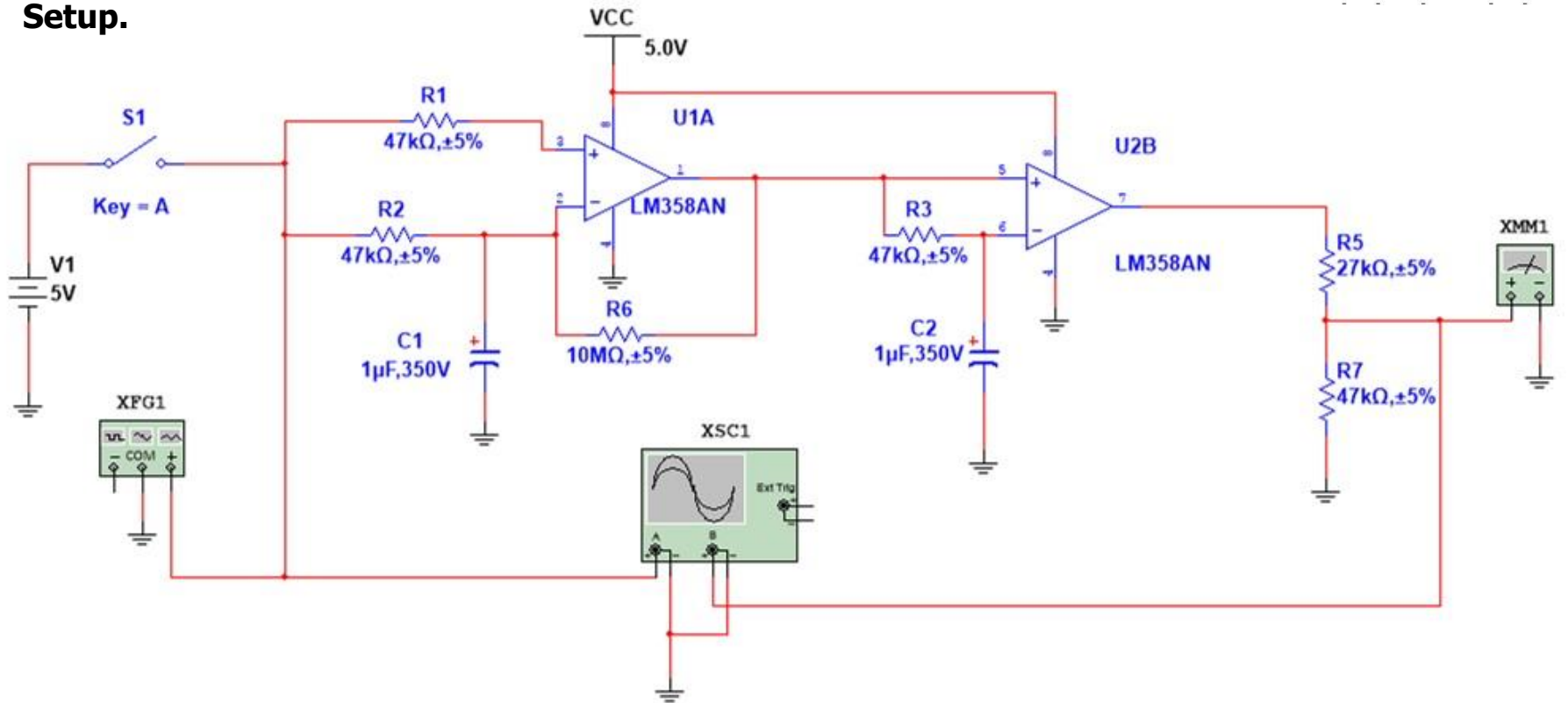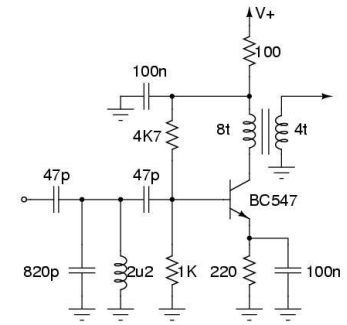**315 MHz Receiver Module:
Difference Amp and Buffer
Circuit Simulation Analysis
Setup.**



RF Modules and Examples...

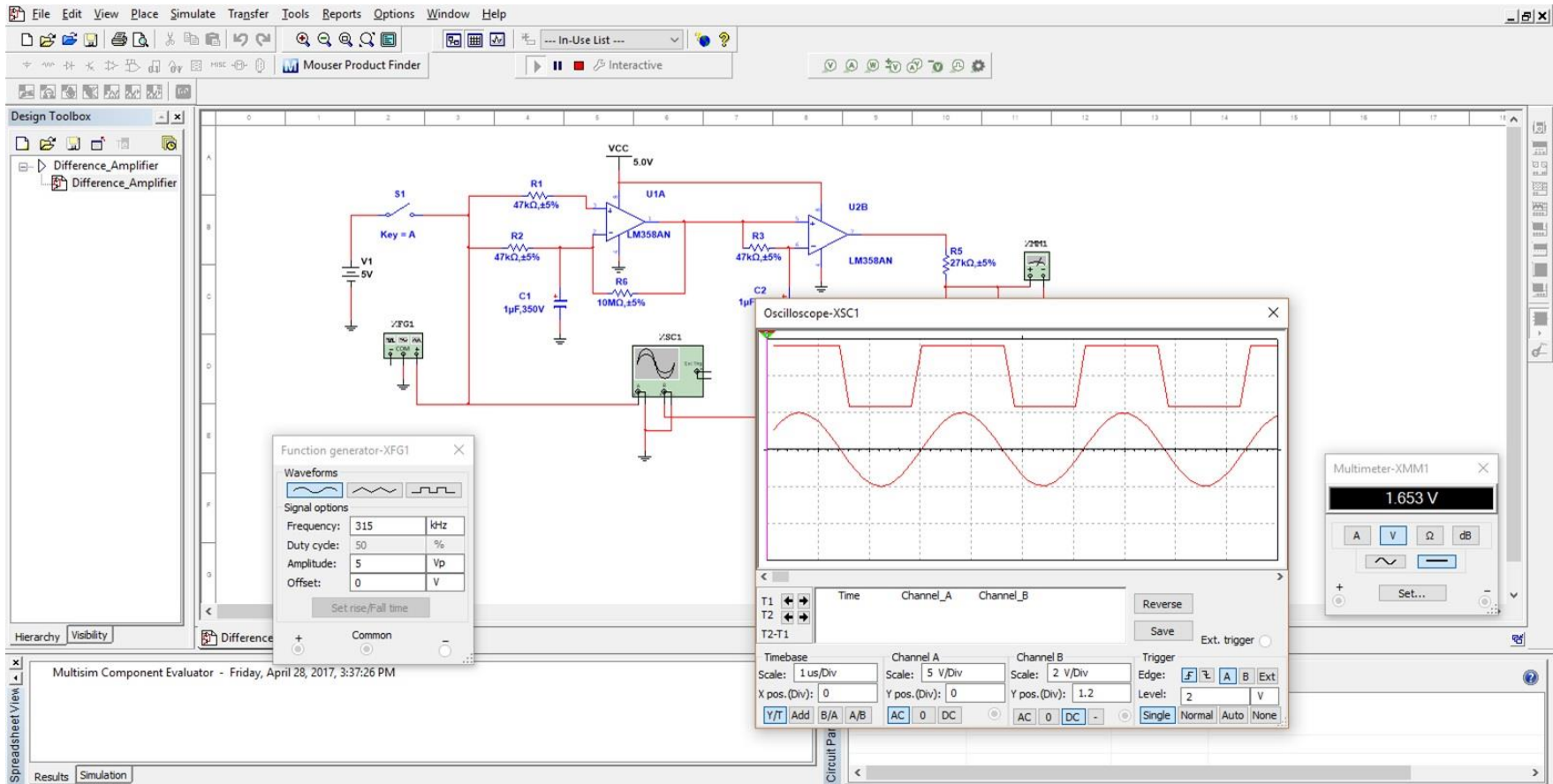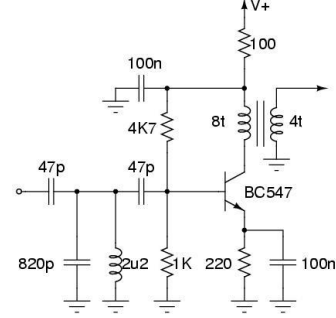315 MHz Receiver Module: Difference Amplifier and Buffer Circuit Simulation Analysis Solution.




Presented by:

Question 4

On the 315 MHz Receiver Module, what op-amp circuit is wired to the RF Amplifier's output signal?


RF Modules and Examples...

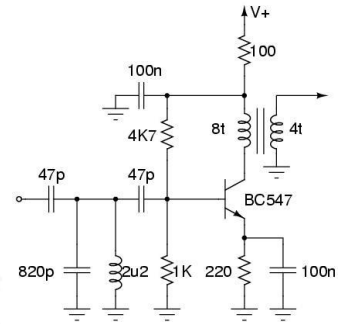**315 MHz Receiver Module:
Difference Amplifier and
Buffer Circuit Simulation
Analysis Solution...**





Digital
Data

Carrier
Frequency

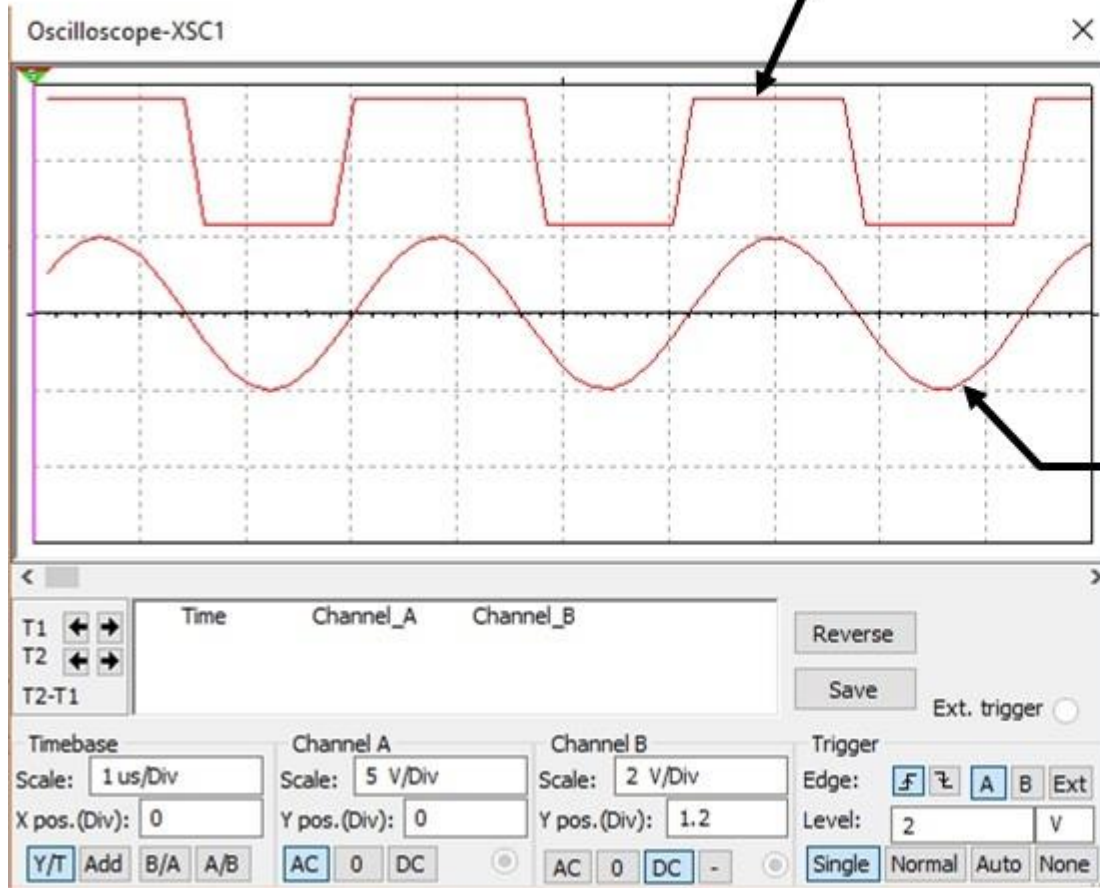

RF Modules and Examples...

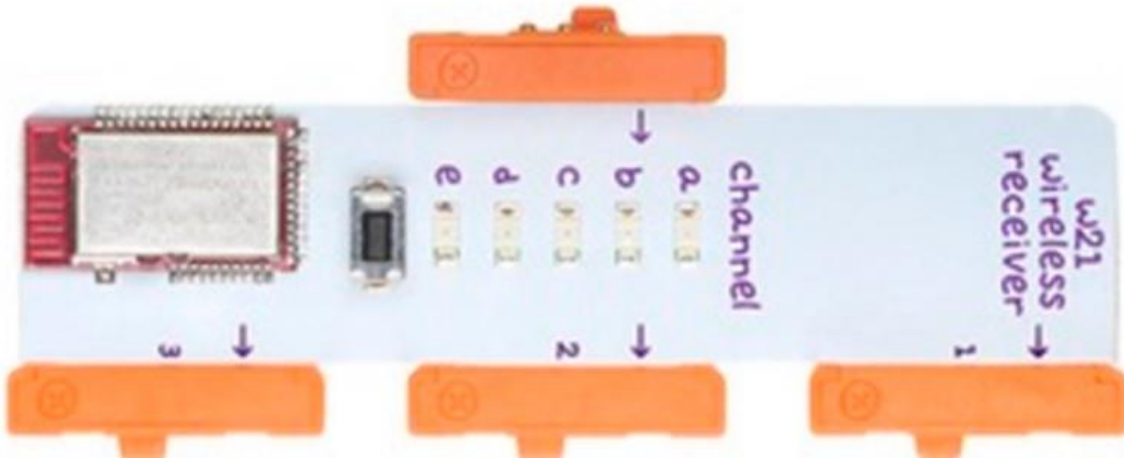
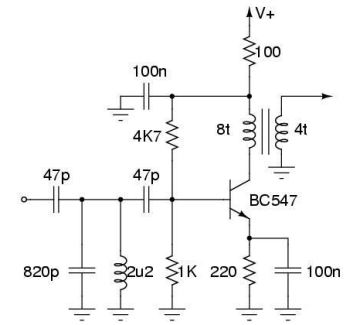


littleBits Wireless Receiver, 5 Channel

Source:


<http://littlebits.cc/bits/wireless-receiver-5-channels#specs>

RF Modules and Examples...

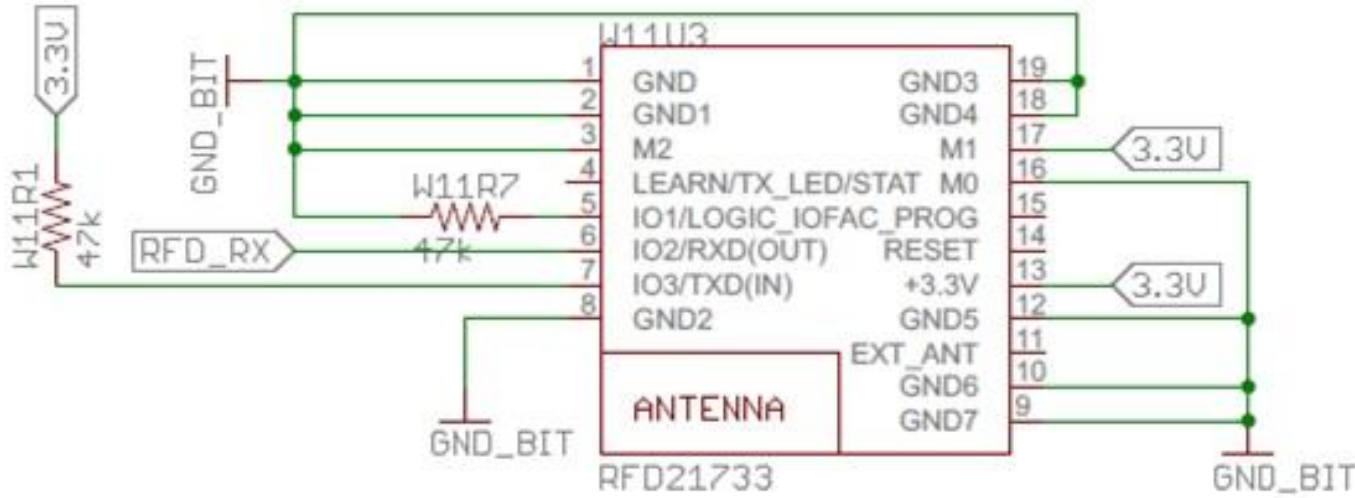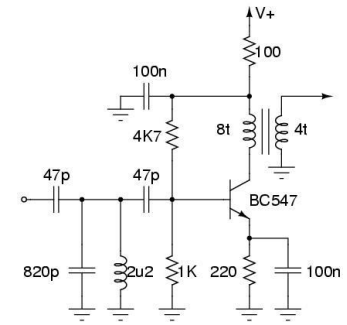

**RFD21733 2.5GHz RF Transceiver
Module with built in RFD8 Protocol**

RF Modules and Examples...

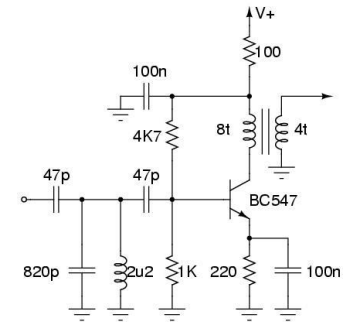



RFDP8 Application Protocol • Mode Selector Chart

RFDP8 Standard Mode Chart

© RF Digital Corp. 07.05.11 10:07 PM

Mode	Description	Mode Select Inputs			IN 3	IN 2	IN 1	Learn / Status	
		2	1	0				ESN LEARN	Network
0	Active RFID Transmitter	0	0	0	IN 3	IN 2	IN 1	TX LED	
1	3 Input Switch Logic Transmitter	0	0	1	IN 3	IN 2	IN 1	TX LED	
2	Serial UART Transceiver, 9600, N, 8, 1	0	1	0	TXD IN	RXD OUT	LOGIC I/O	X	
3	Serial UART Transceiver, 9600, N, 8, 1	0	1	1	TXD IN	RXD OUT	LOGIC I/O	ESN LEARN	Network
4	3 Output Switch Logic Receiver - 500ms	1	0	0	OUT 3	OUT 2	OUT 1	X	
5	3 Output Switch Logic Receiver - 500ms	1	0	1	OUT 3	OUT 2	OUT 1	ESN LEARN	Network
6	3 Output Switch Logic Receiver - 20ms	1	1	0	OUT 3	OUT 2	OUT 1	X	
7	3 Output Switch Logic Receiver - 20ms	1	1	1	OUT 3	OUT 2	OUT 1	ESN LEARN	Network
Module RFD21733 / RFD21735 Pin Number:		3	17	16	7	6	5	4	
RFDANT RFD21742 / RFD21743 Pin Number:		7	6	5	11	10	9	8	

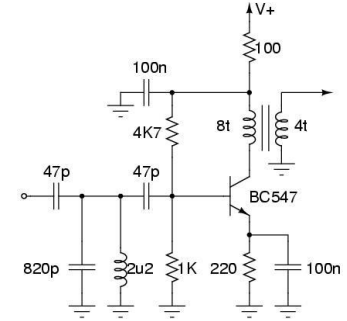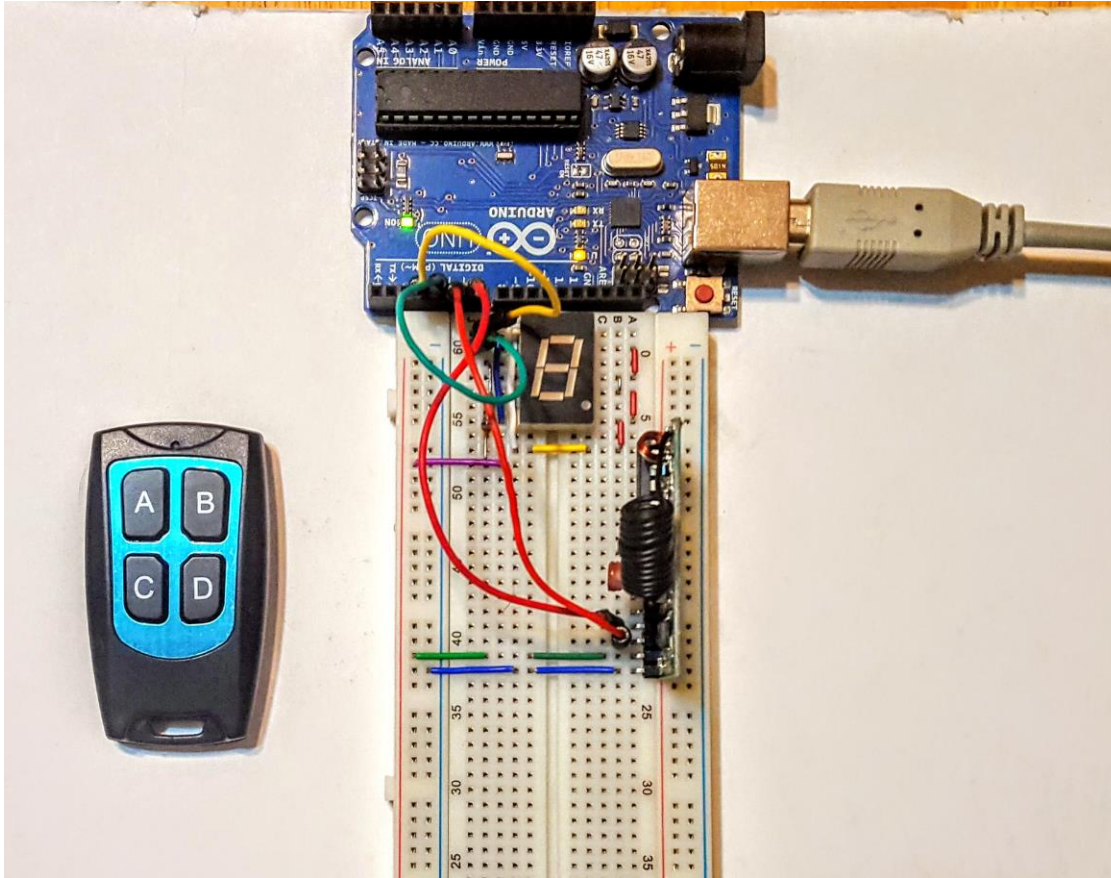Hands On Project: 7 Segment LED Display Controller




Hands On Project: 7 Segment LED Display Controller...



Project Objectives

Build a wireless Arduino controller that

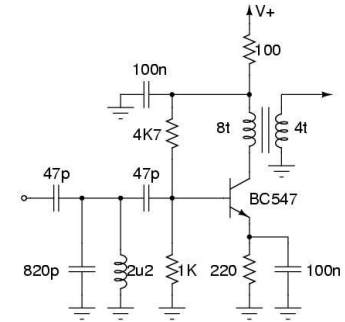
- allows the numbers "1" and "3" to be displayed on a 7 Segment LED Display.
- pressing the "C" key on the Fob will display the number "1"
- pressing the "D" key on the Fob will display the number "3"




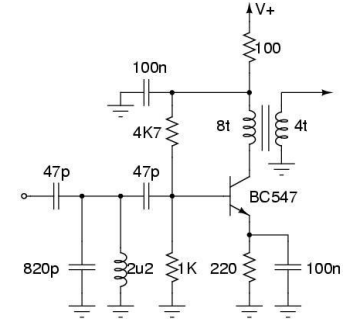
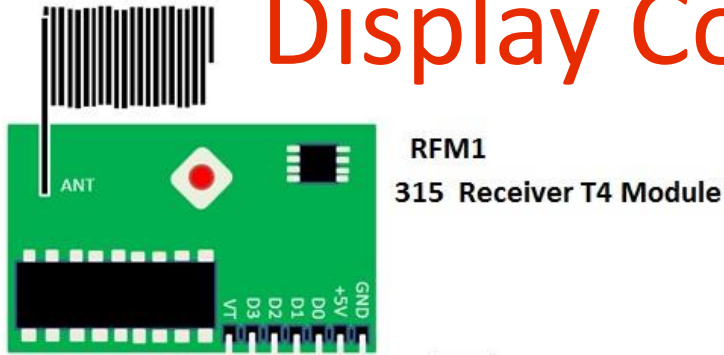
Hands On Project: 7 Segment LED Display Controller...



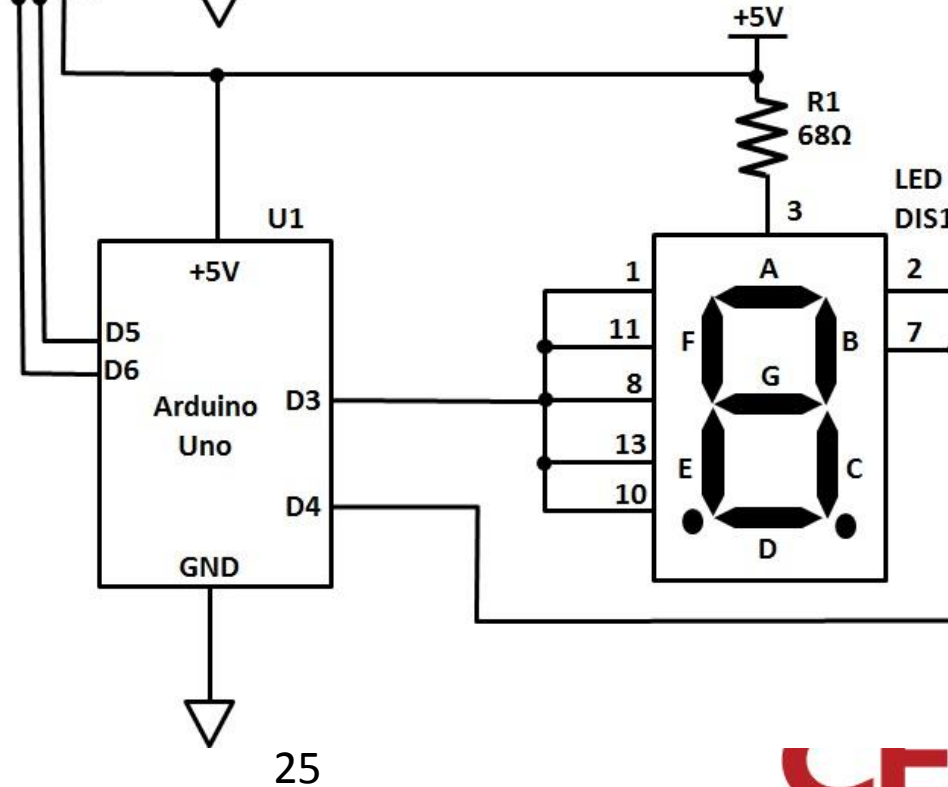7 Segment LED Display Controller Circuit Schematic Diagram



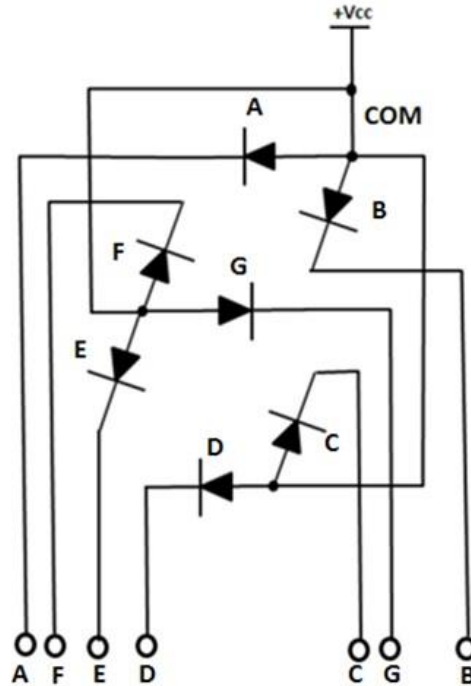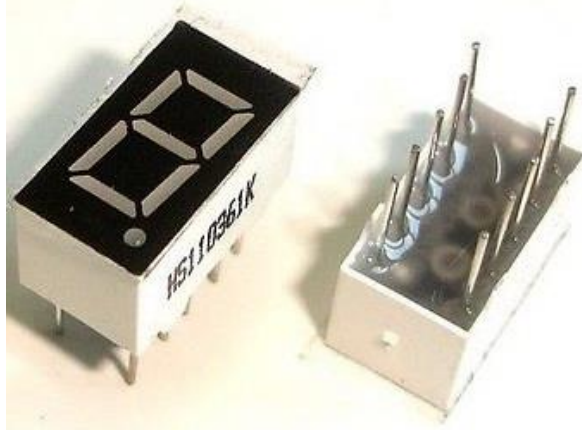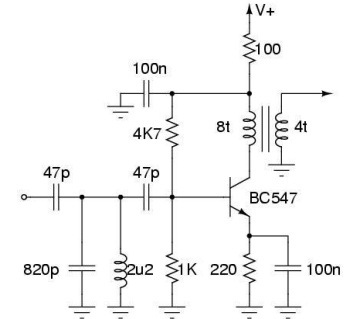Hands On Project: 7 Segment LED Display Controller...



Pin no.	Electrical connection
1	Cathode A
2	Cathode F
3	Common Anode
4	No Pin
5	No Pin
6	Cathode D. P.
7	Cathode E
8	Cathode D
9	No Connection
10	Cathode C
11	Cathode G
12	No Pin
13	Cathode B
14	Common Anode



Common Anode 7 Segment LED Display

Question 5

The common pin on a 7 segment LED Display refers to

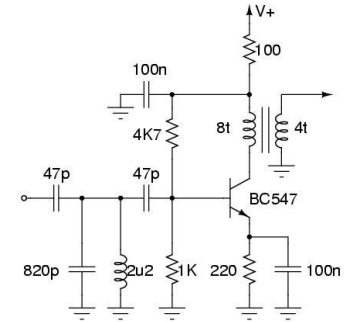
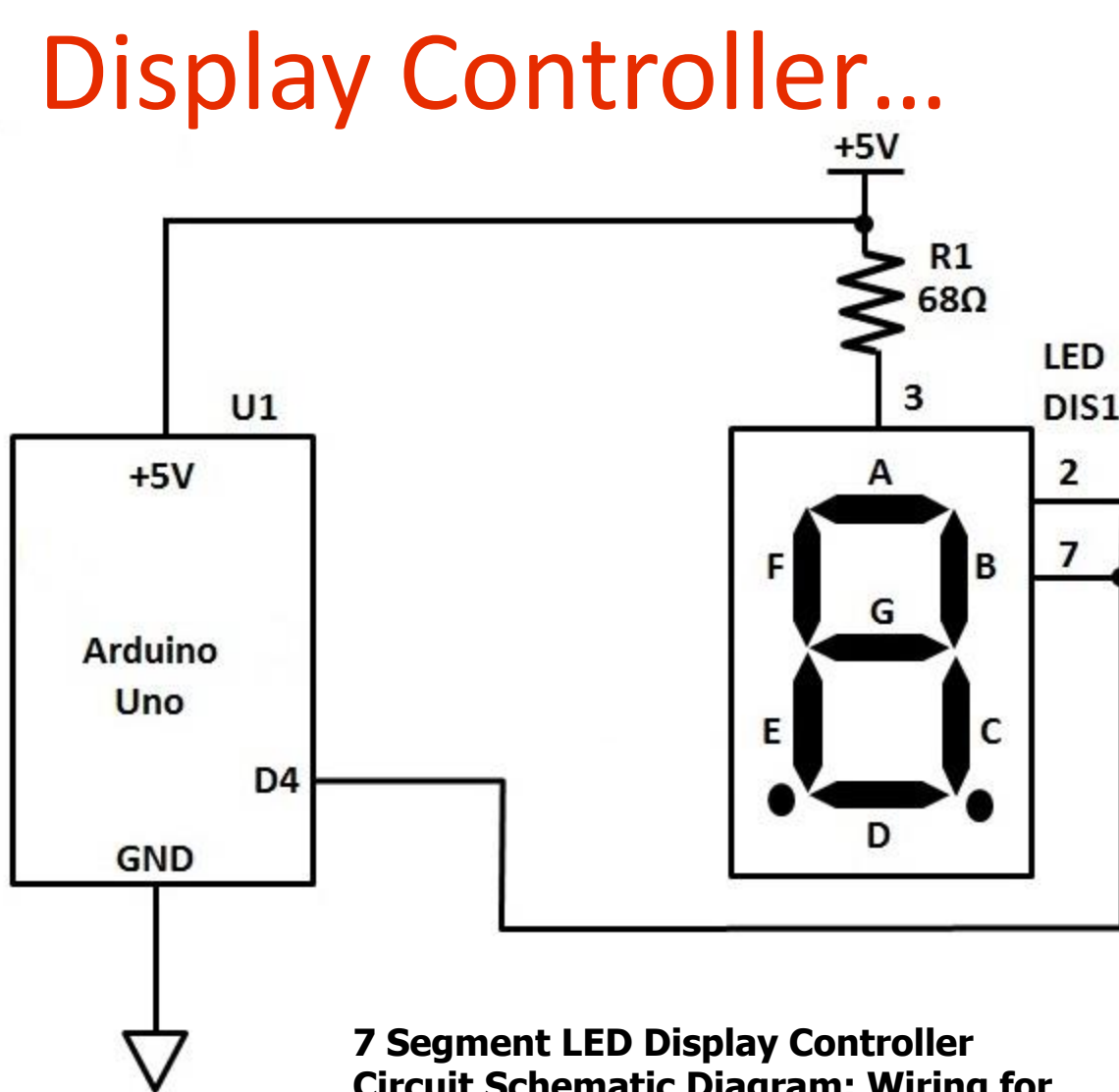
- a) all LED segment's cathodes or anodes wired together**
- b) the ground pin of the 7 segment LED Display**
- c) a reference for the 7 segment LED Display**
- d) none of the above**

Hands On Project: 7 Segment LED Display Controller...





**7 Segment LED Display Controller
Circuit Schematic Diagram: Wiring for
the number "1".**

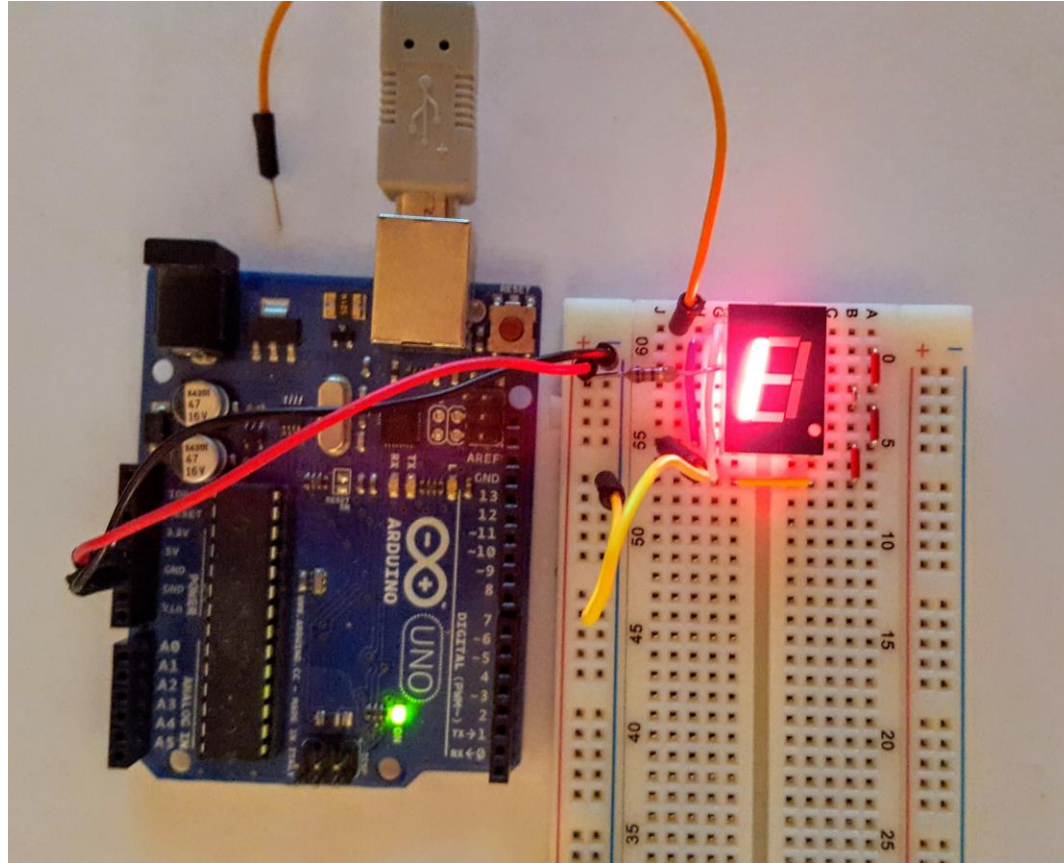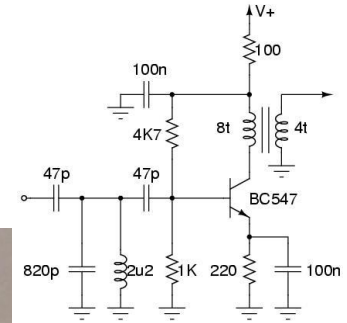Hands On Project: 7 Segment LED Display Controller...




7 Segment LED Display Controller Circuit Schematic Diagram: Testing display wiring for the number "1".

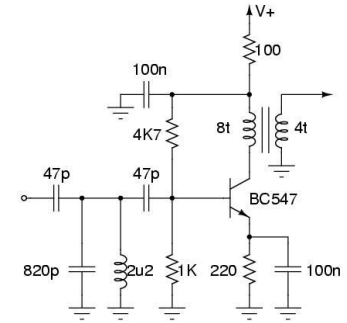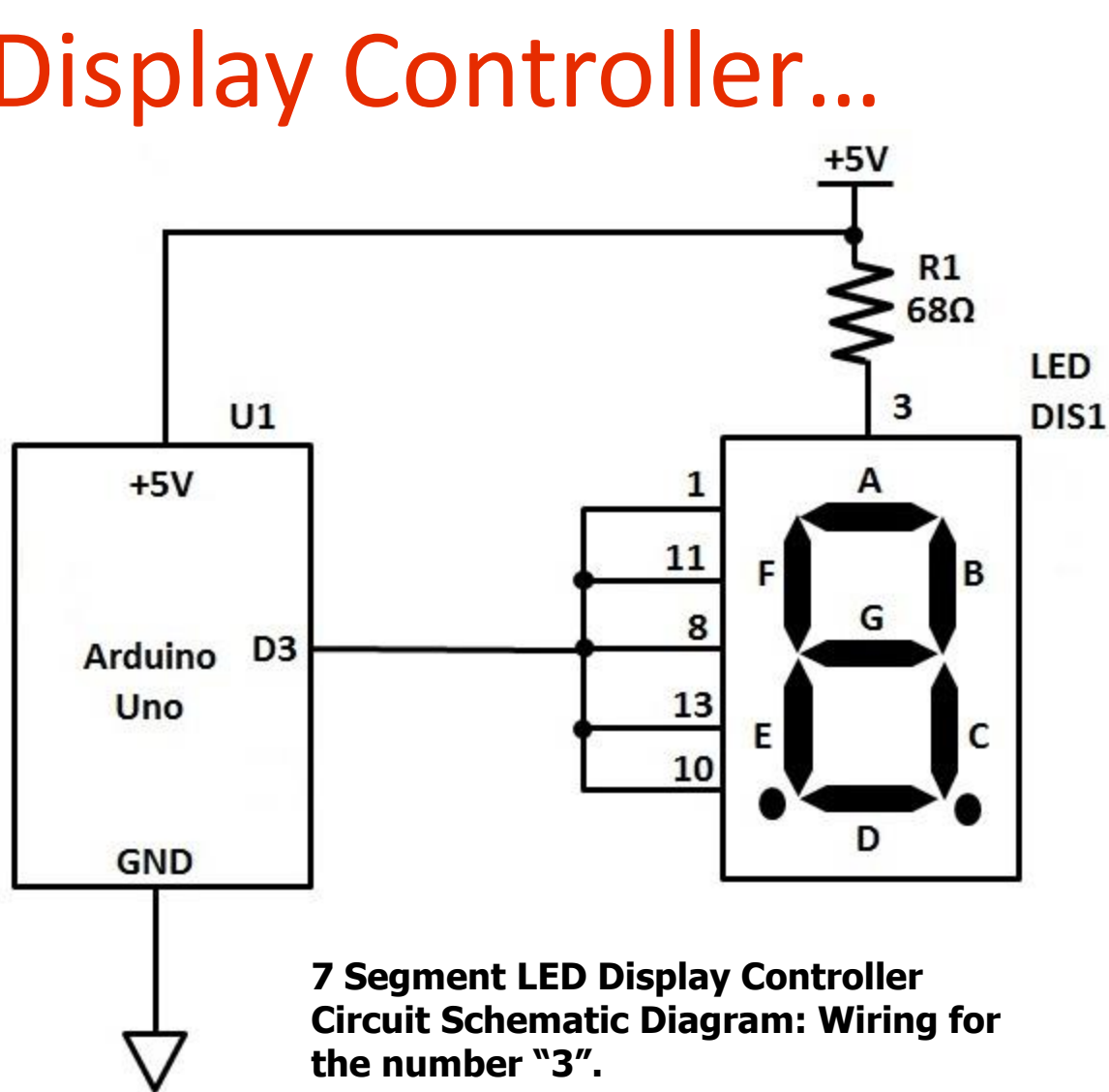
Hands On Project: 7 Segment LED Display Controller...



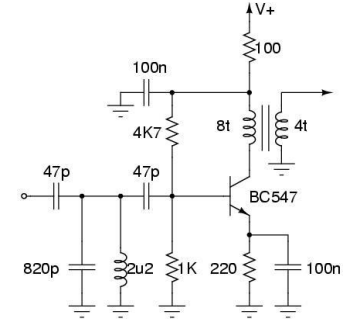Hands On Project: 7 Segment LED Display Controller...



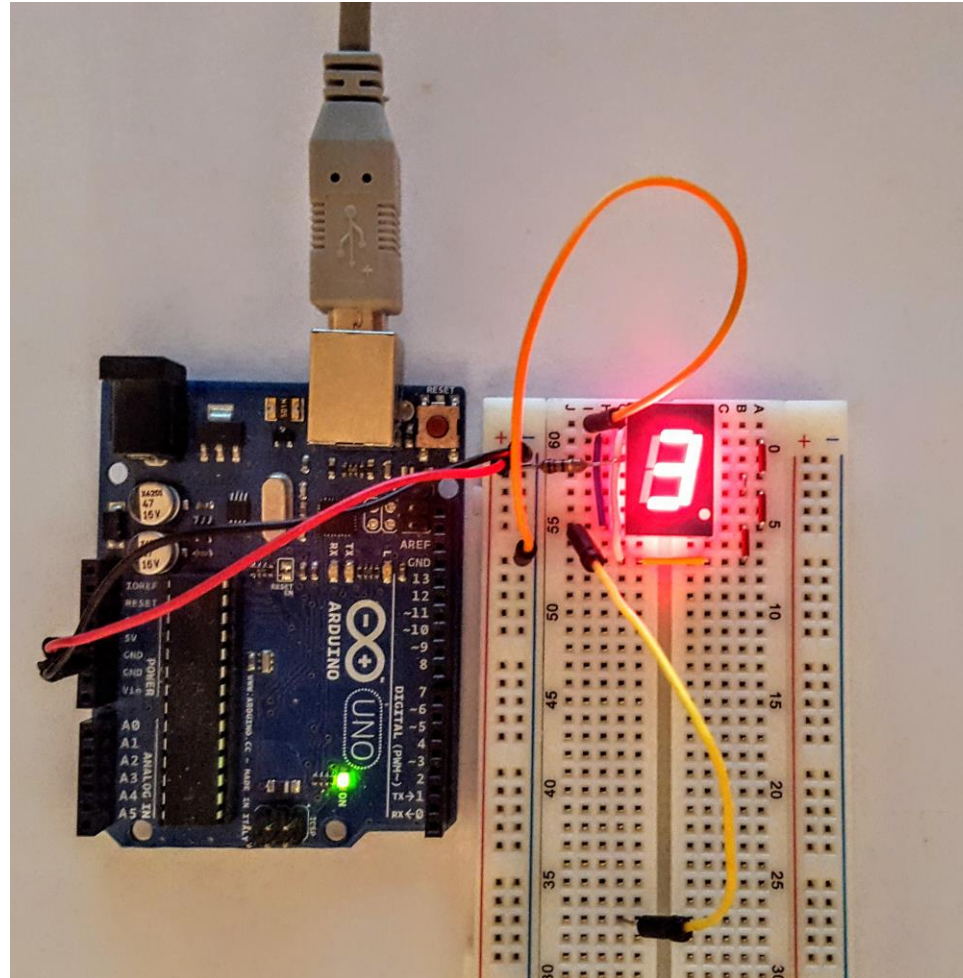7 Segment LED Display Controller Circuit Schematic Diagram: Testing display wiring for the number "3".



Presented by:

Hands On Project: 7 Segment LED Display Controller...

Modify the Button code (sketch) to control the 7 Segment LED Display.

```
Button
http://www.arduino.cc/en/Tutorial/Button
*/


// constants won't change. They're used here to
// set pin numbers:
const int buttonPin = 2;    // the number of the pushbutton pin
const int ledPin = 13;     // the number of the LED pin

// variables will change:
int buttonState = 0;       // variable for reading the pushbutton status

void setup() {
  // initialize the LED pin as an output:
  pinMode(ledPin, OUTPUT);
  // initialize the pushbutton pin as an input:
  pinMode(buttonPin, INPUT);
}

void loop() {
  // read the state of the pushbutton value:
  buttonState = digitalRead(buttonPin);


  // check if the pushbutton is pressed.
```

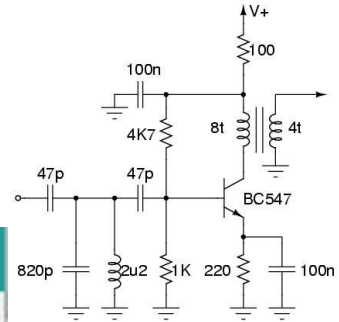

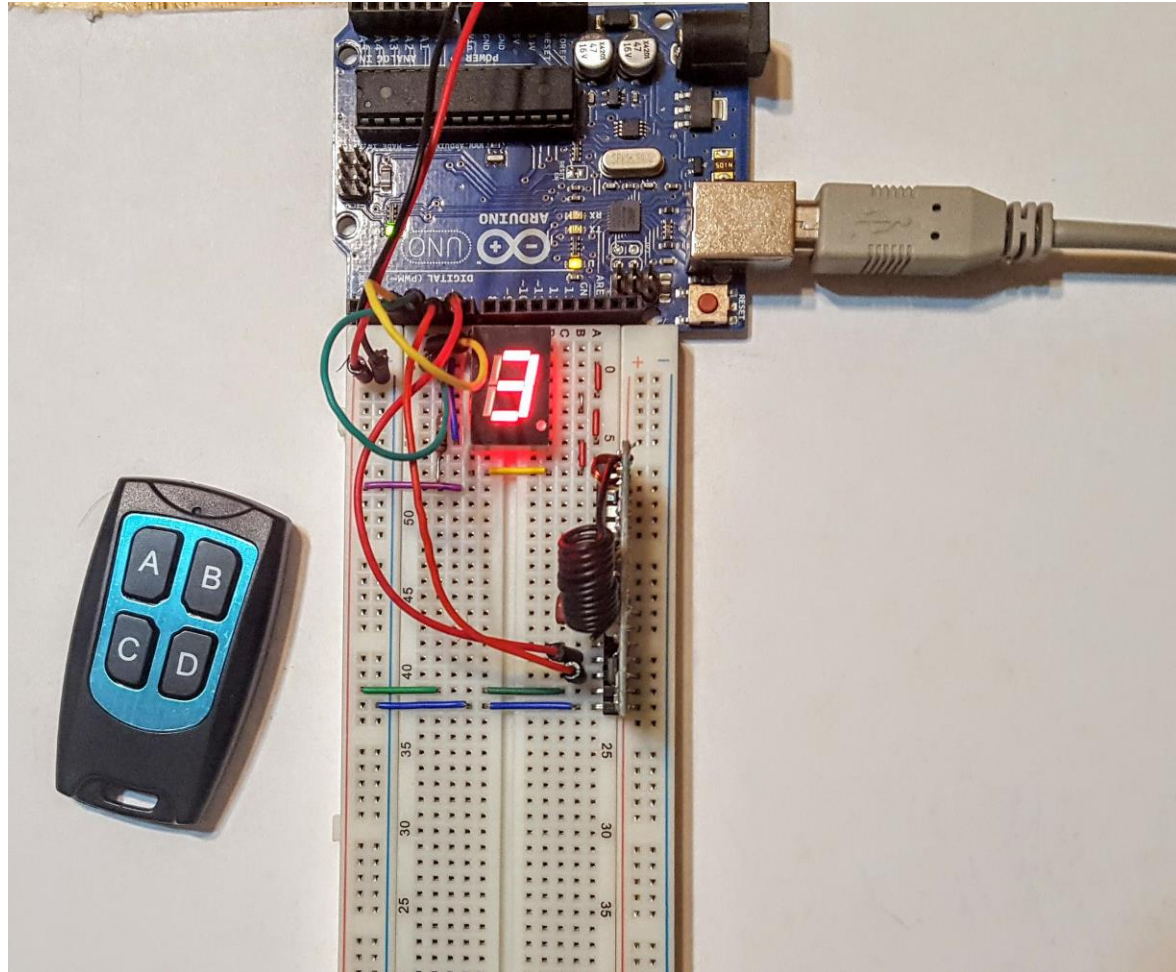
Question 6

What segment pins on the 7 segment LED Display are used to show a number 3?



Hands On Project: 7 Segment LED Display Controller...



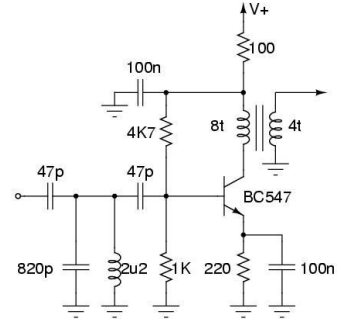Displaying the number "3" by pressing the "D" key on the Fob.



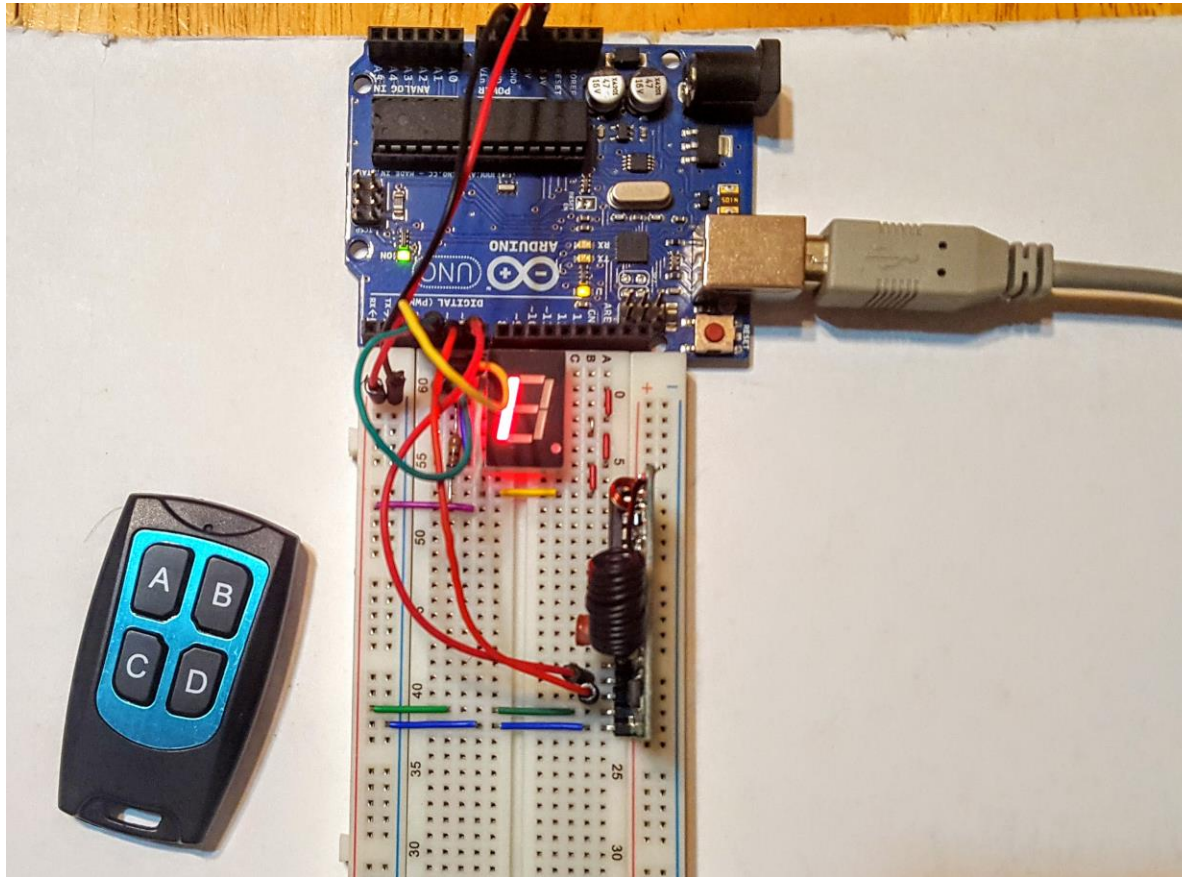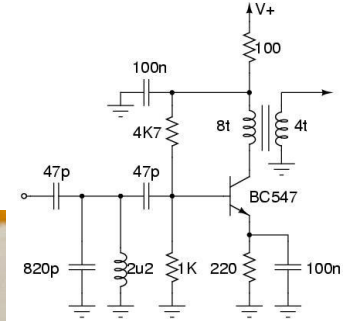Hands On Project: 7 Segment LED Display Controller...



Displaying the number "1" by pressing the "C" key on the Fob.