



**DesignNews**

Raspberry Pi 4 Automation

# DAY 4 : DC Motor Controls

Sponsored by



## Webinar Logistics

- Turn on your system sound to hear the streaming presentation.
- If you have technical problems, click “Help” or submit a question asking for assistance.
- Participate in ‘Group Chat’ by maximizing the chat widget in your dock.
- Submit questions for the lecturer using the Q&A widget. They will follow-up after the lecture portion concludes.



## Don Wilcher

Visit 'Lecturer Profile' in your console for more details.

## Agenda:

- Basic DC Motor Control Concept
- What is a H-Bridge Driver?
- The L293 H-Bridge IC
- Lab: A DC Motor Controller




## Basic DC Motor Control Concept



A Basic DC Motor Control consists of

- DC power supply.
- A controller
- A DC motor

### Basic DC Motor Control Block Diagram

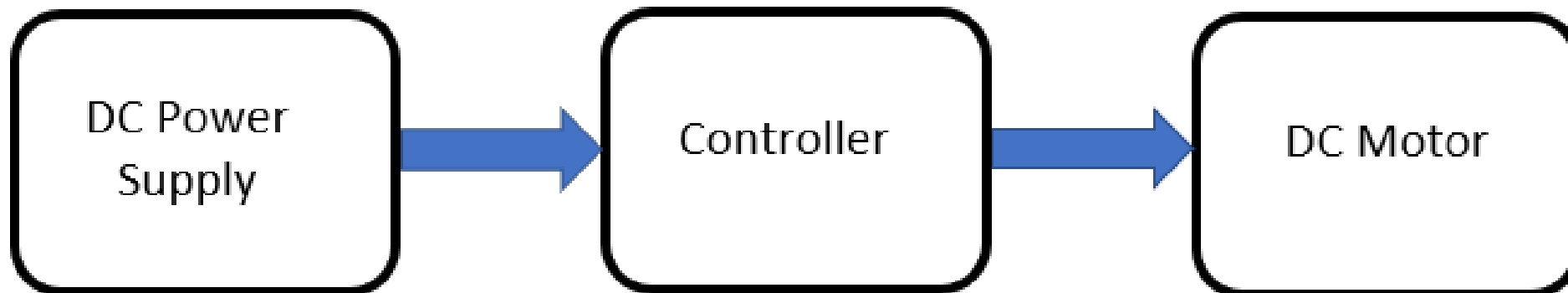

## Basic DC Motor Control Concept...


A simple controller for operating a typical dc motor is a Single Pole-Single Throw switch (SPST).



Rocker,  
Toggle or  
Slide SPST  
switch



Momentary  
Pushbutton  
SPST switch

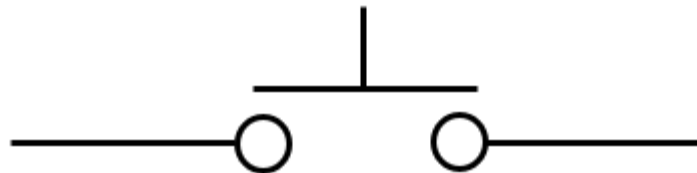

**Typical Switches which can be used as a simple controller**



## Basic DC Motor Control Concept...



Typical Switches which can be used as a simple controller



Slide SPST Switch



Rocker SPST Switch



Toggle SPST Switch

## Question 1



Identify the switch based on the electrical symbol shown in Figure 1.




Figure 1.



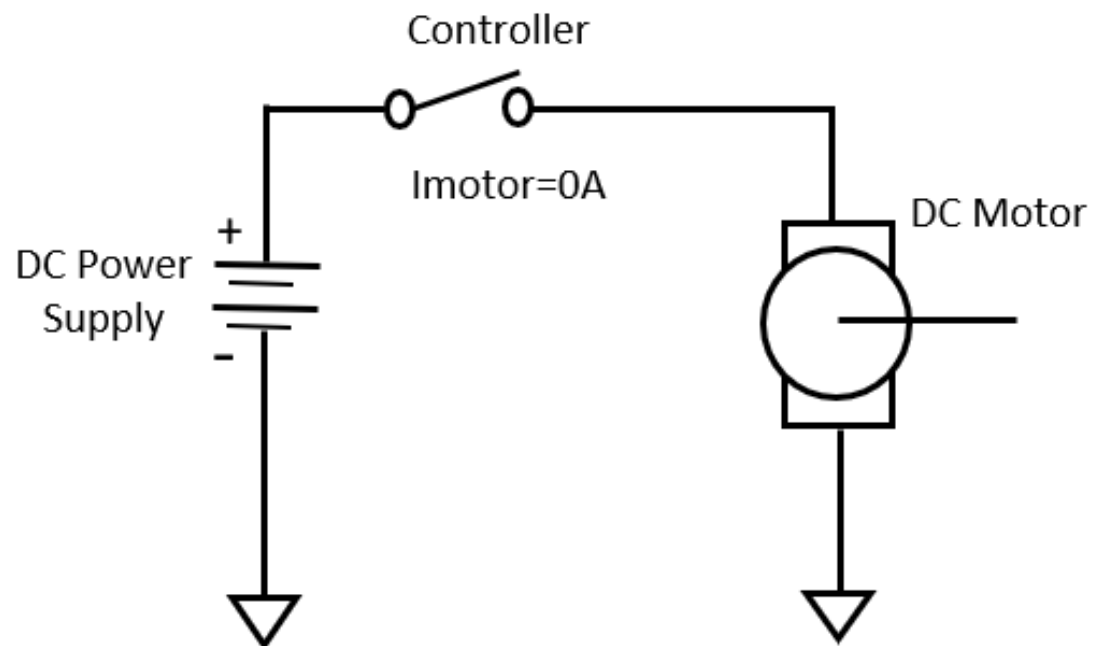
## Basic DC Motor Control Concept...



A typical circuit schematic diagram of Basic DC Motor Controller




**Motor OFF**

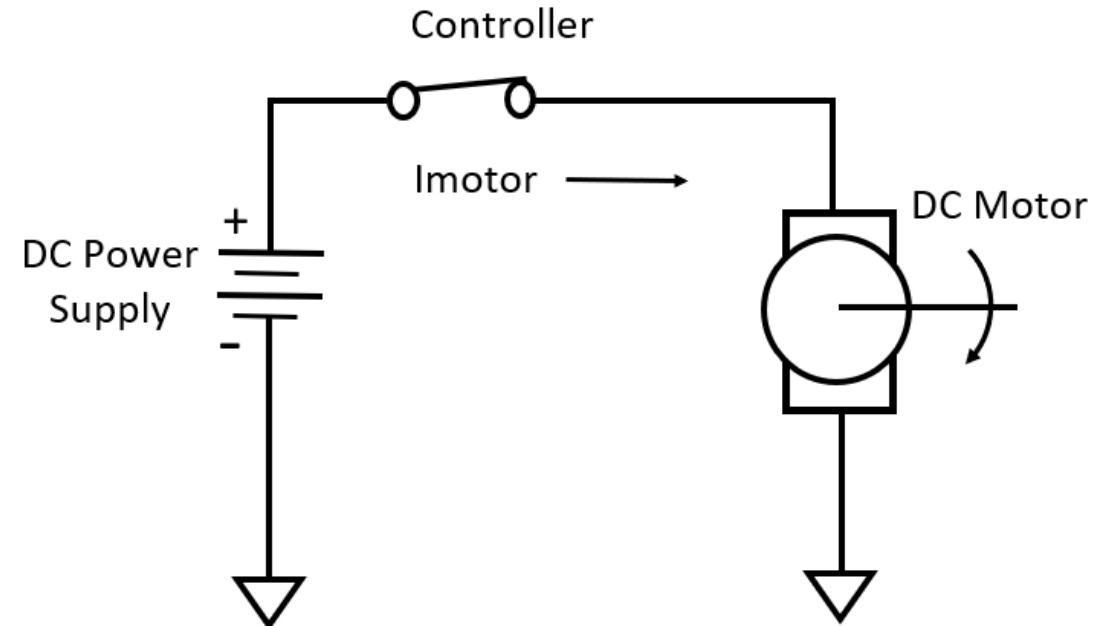

**Motor ON**

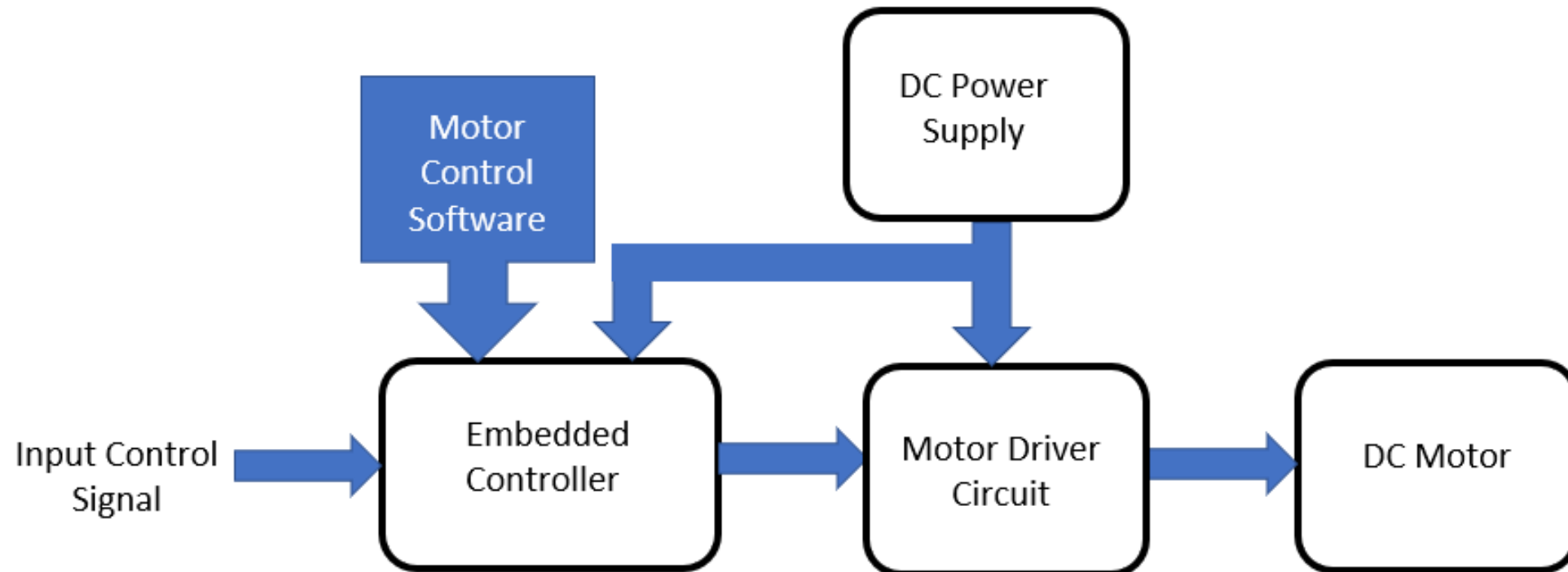
## Basic DC Motor Control Concept...

To make a controller that is less manual dependent, a desirable automation-based solution can be conceptualized.


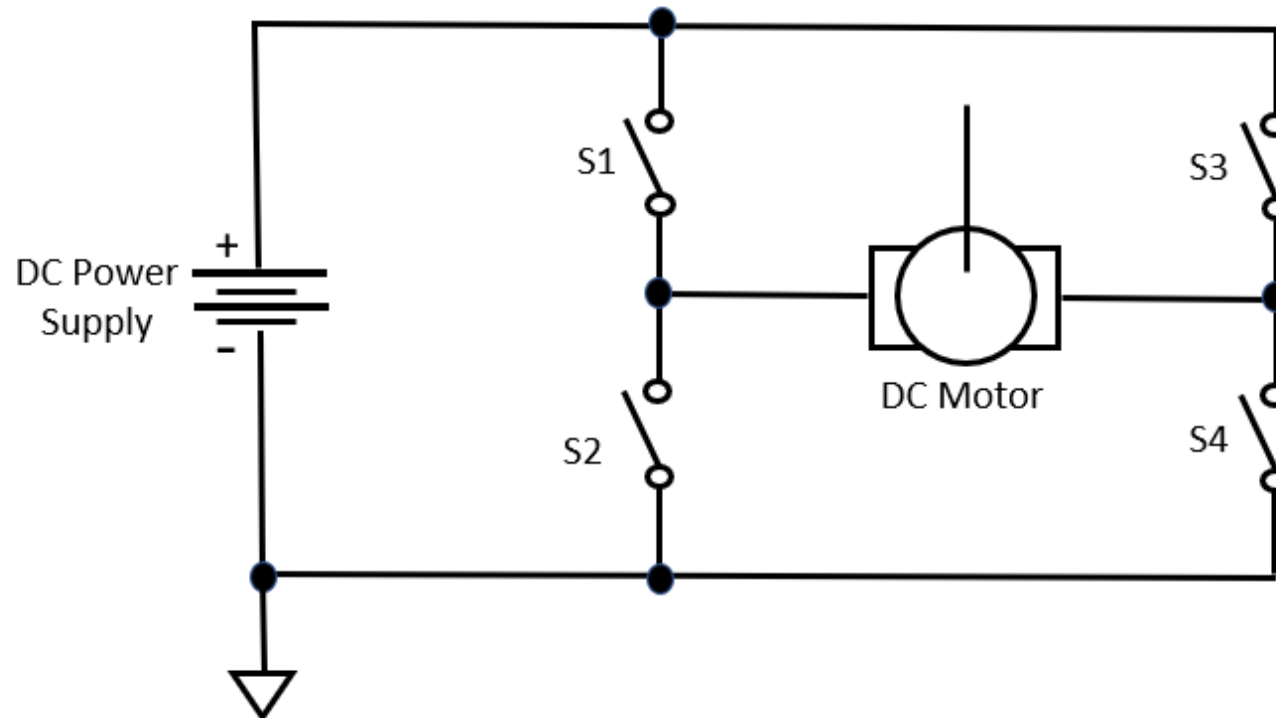
## What is a H-Bridge Driver?

An electronic circuit capable of switch polarity across electromechanical load. A basic method of illustrating the concept of a H-Bridge Driver circuit is using four SPST switches.




## What is a H-Bridge Driver?...


By closing the correct switch combinations, the H-Bridge Driver can control the direction of the DC motor.



S1S4 = Forward Direction

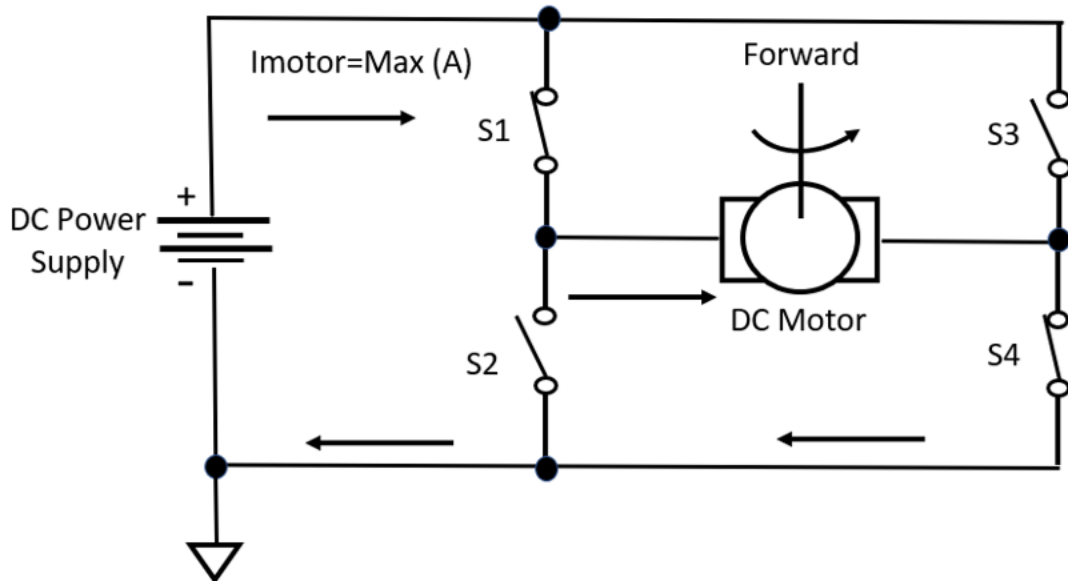


S2S3 = Reverse Direction

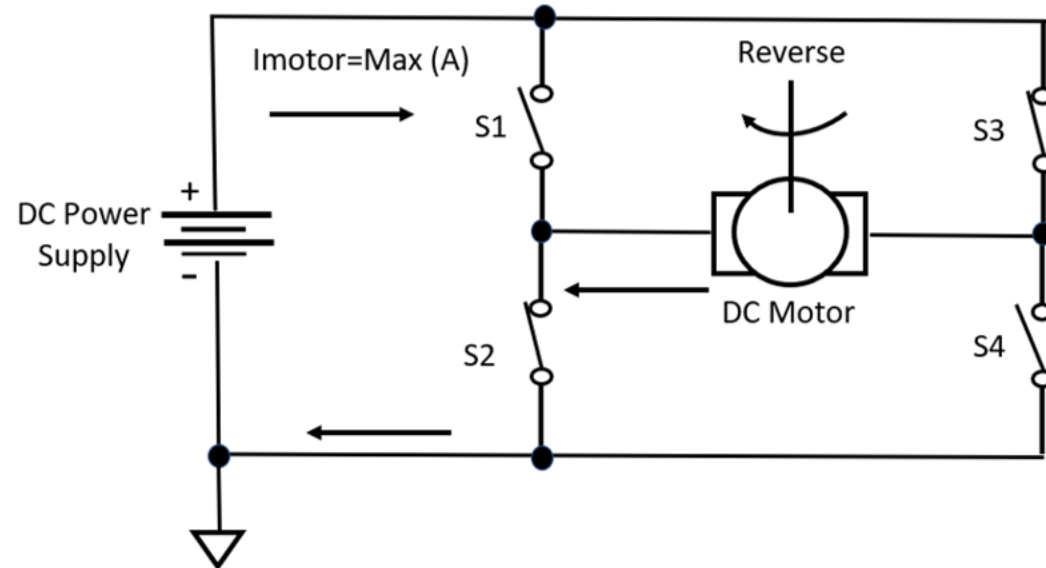
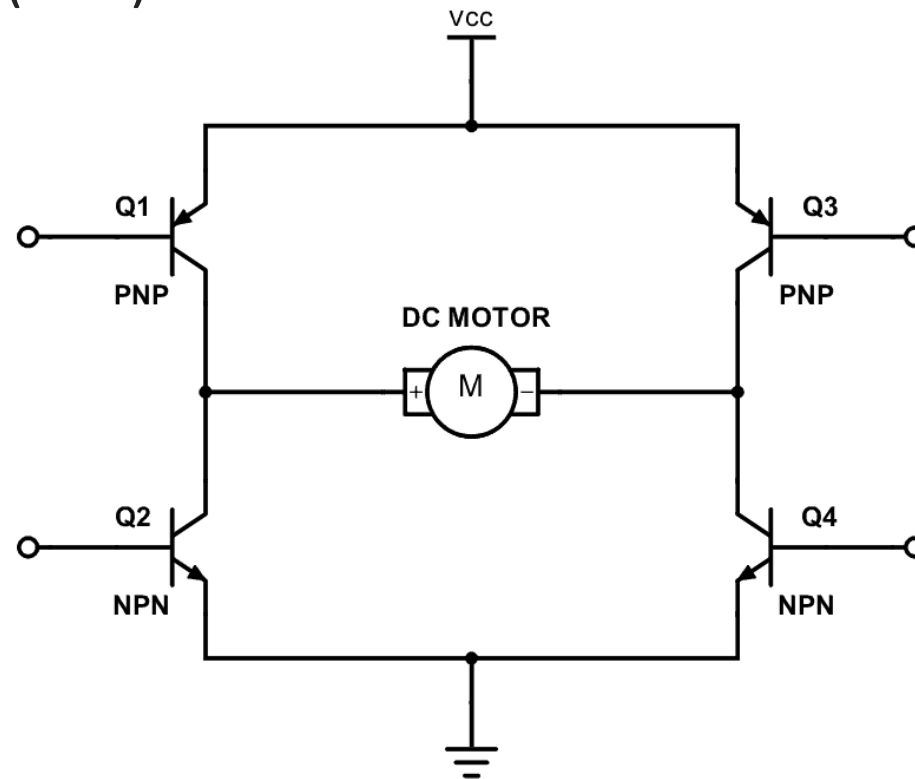
## What is a H-Bridge Driver?...

A solid-state (SS) version can be implemented using Complementary Pairs of PNP and NPN bipolar junction transistors (BJTs).



Source:

<https://www.build-electronic-circuits.com/h-bridge/>




## What is a H-Bridge Driver?...


The direction of the DC Motor is controlled by turning on the correct complementary pair of BJTs.



Q1Q4 = Forward Direction

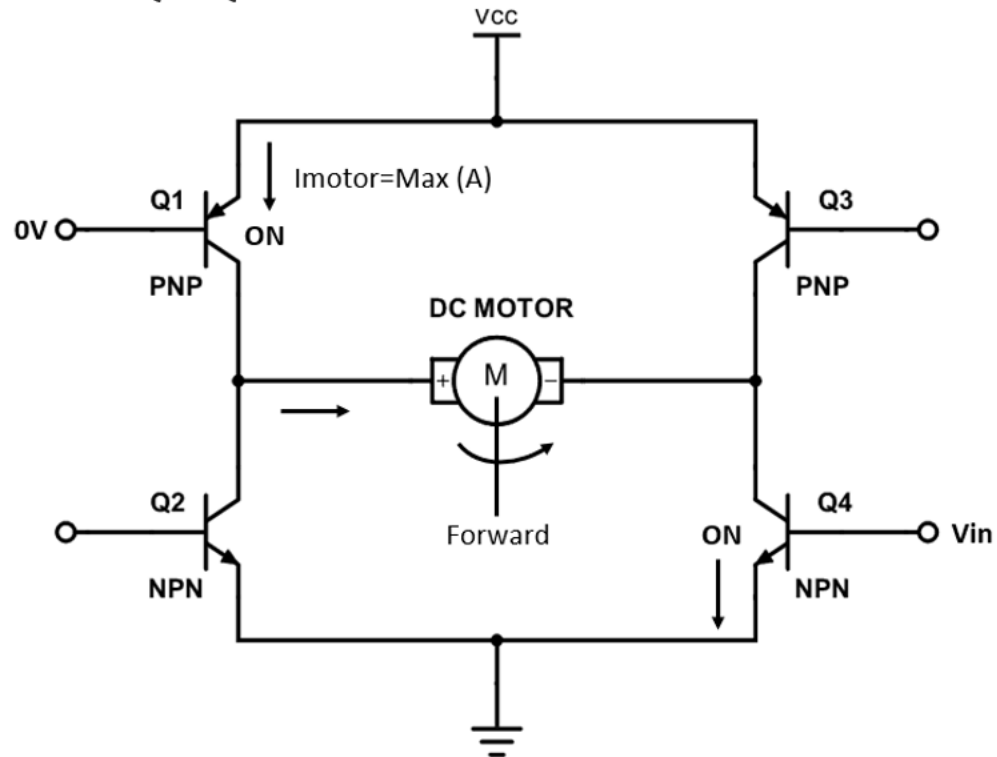

Q2Q3 = Reverse Direction

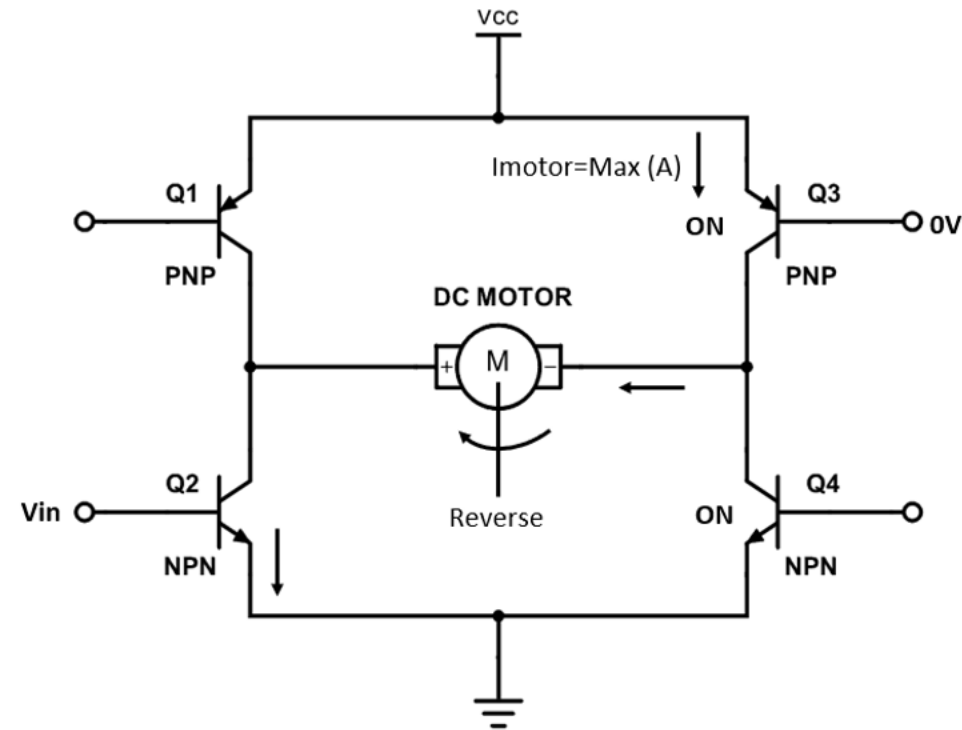



## What is a H-Bridge Driver?...

The advantage to using a SS H-Bridge Driver is the ability to control speed and direction of the DC Motor with a microcontroller.


### Concept Circuit Schematic Diagram

Pulse Width Modulating (PWM) the microcontroller's digital port pins (P1-P4) will provide speed control for the DC Motor.

P1P3 = Forward Direction

P2P4 = Reverse Direction

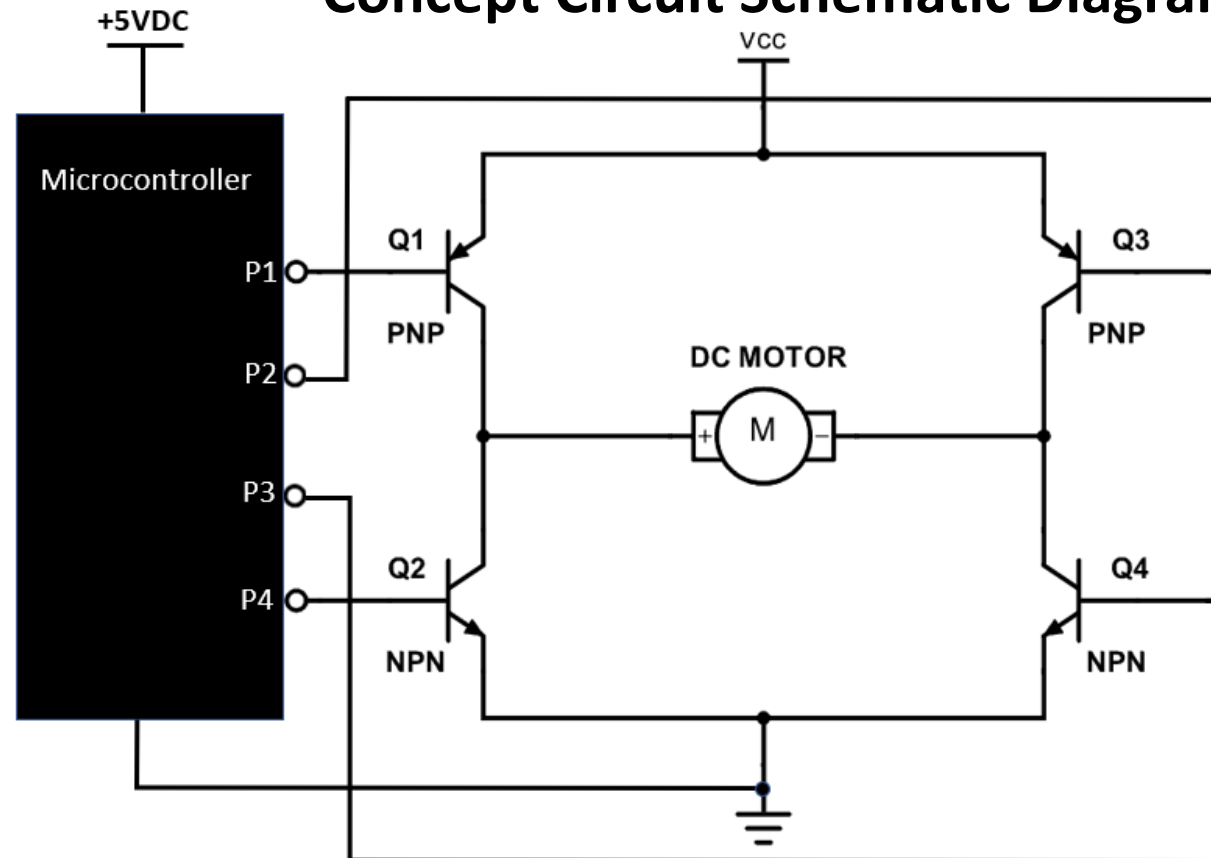**Note:** Each BJT transistor will have a base resistor ( $R_b$ ) to limit current flowing through the semiconductor component.




## The L293 H-Bridge IC


The L293 H-Bridge IC has four SS drivers integrated within its package.



BLOCK DIAGRAM

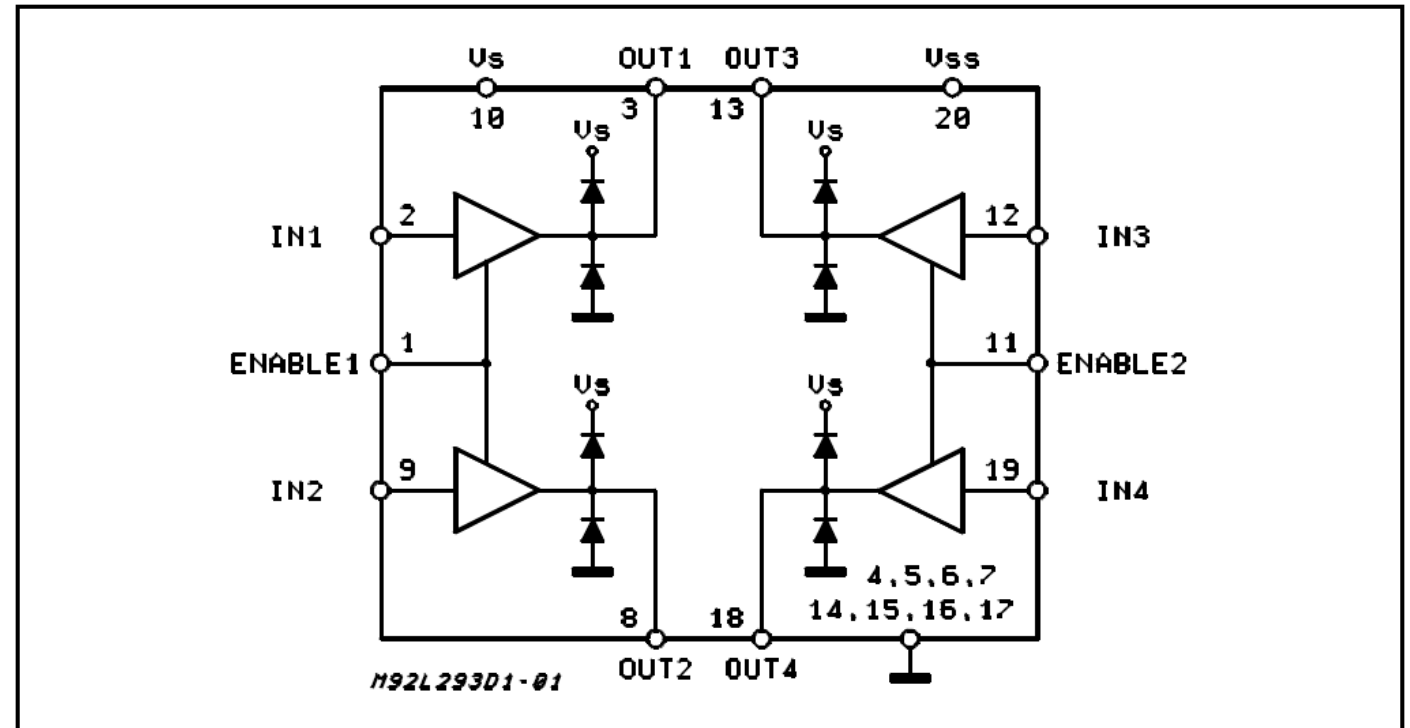

Small Outline (SO)

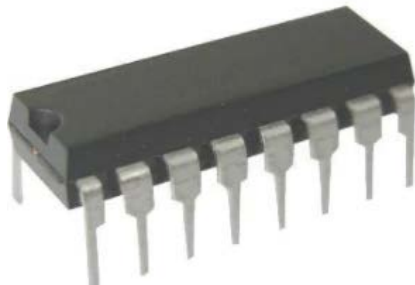

Power (DIP)

Source:


<https://www.mouser.com/datasheet/2/389/cd00000059-1795435.pdf>



## The L293 H-Bridge IC...

The L293 H-Bridge IC pinout for small outline (SO) and plastic Dual-Inline-Package (DIP) components

PIN CONNECTIONS (Top view)

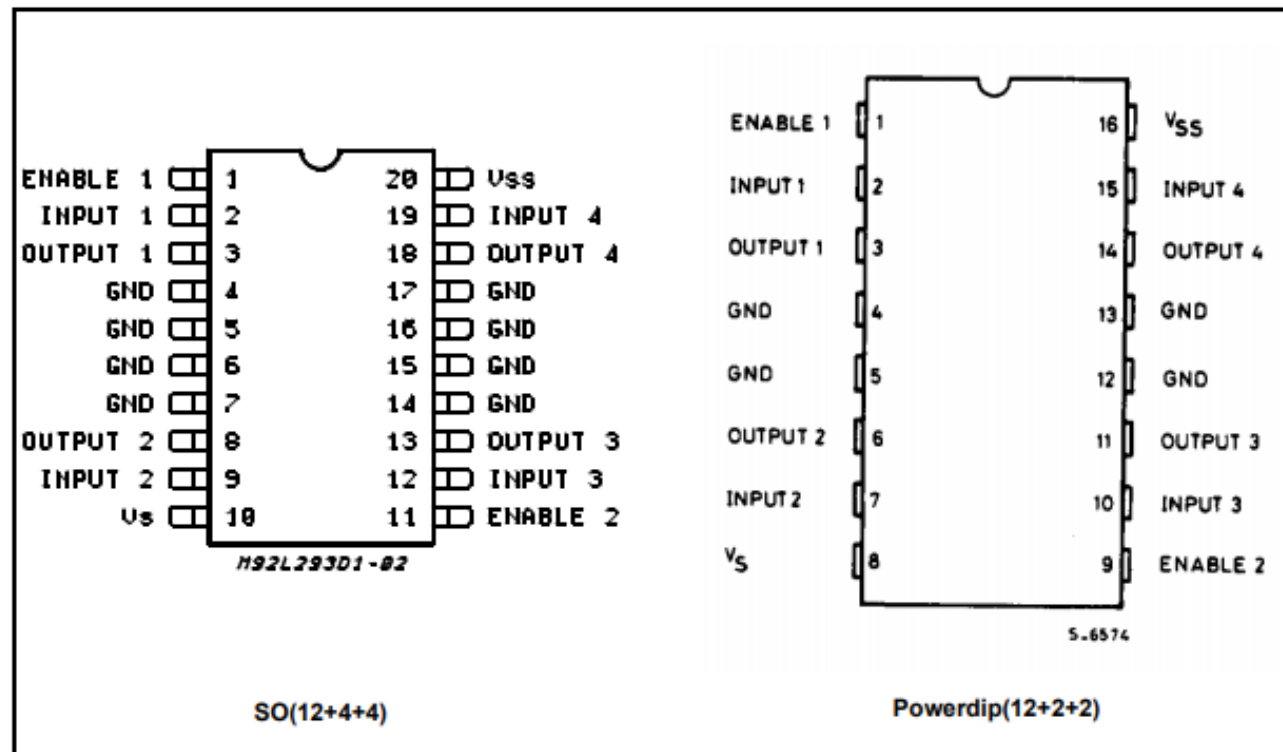

Source:

<https://www.mouser.com/datasheet/2/389/cd00000059-1795435.pdf>

## The L293 H-Bridge IC...



The L293 H-Bridge IC electrical specifications.

### ABSOLUTE MAXIMUM RATINGS

Symbol	Parameter	Value	Unit
$V_S$	Supply Voltage	36	V
$V_{SS}$	Logic Supply Voltage	36	V
$V_i$	Input Voltage	7	V
$V_{en}$	Enable Voltage	7	V
$I_o$	Peak Output Current (100 $\mu$ s non repetitive)	1.2	A
$P_{tot}$	Total Power Dissipation at $T_{pins} = 90\text{ }^\circ\text{C}$	4	W
$T_{stg}, T_j$	Storage and Junction Temperature	- 40 to 150	$^\circ\text{C}$


Source:

<https://www.mouser.com/datasheet/2/389/cd00000059-1795435.pdf>



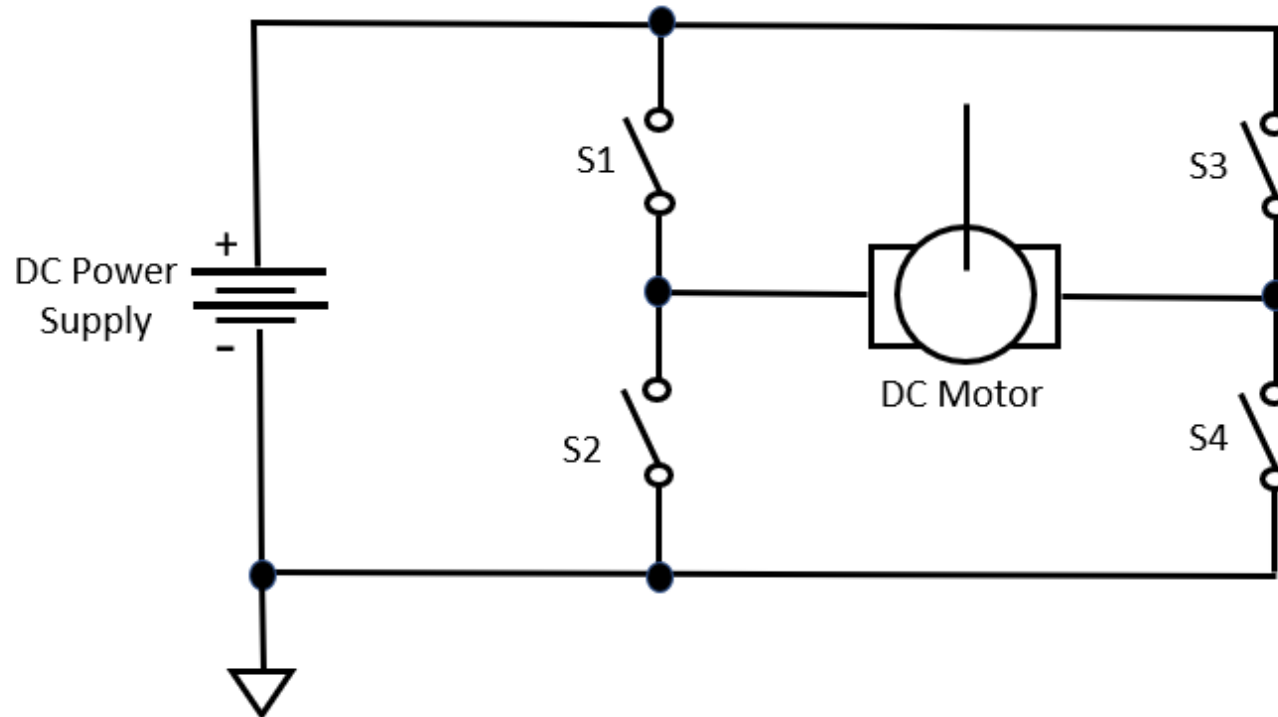
## Question 2

Identify the electronic circuit shown in Figure 2.



## Lab Project: A DC Motor Controller

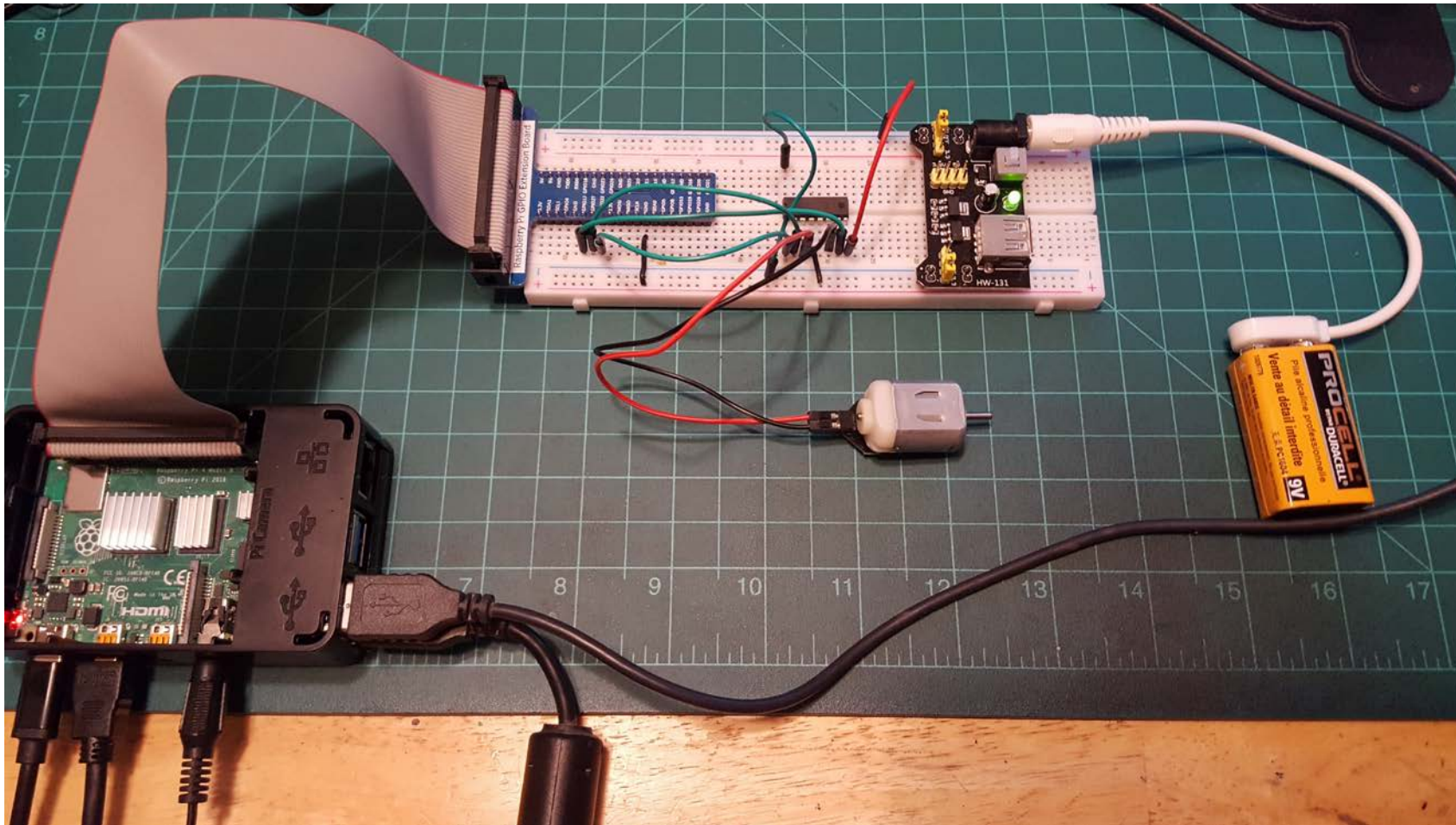

## Lab Project: A DC Motor Controller


### Big IDEAS:

1. Learners will be able to wire an electronic controller using a few off the shelf components .
2. Learners will be able to build a motor speed control device using Physical Computing concepts.
3. Learners will be able to make small changes to the code for personalization.



# Lab Project: A DC Motor Controller...

## A DC Motor Controller Block Diagram

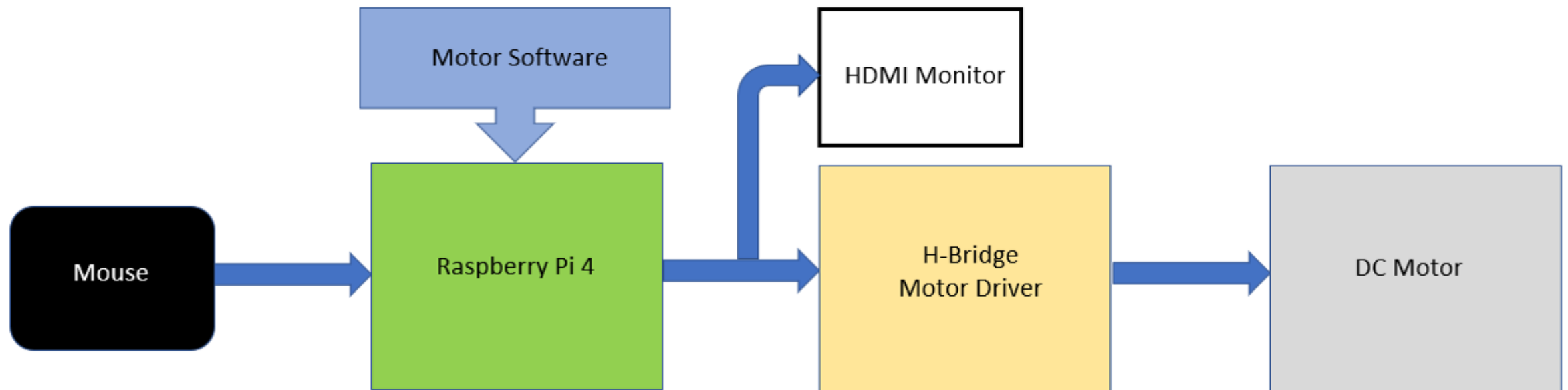



## Question 3




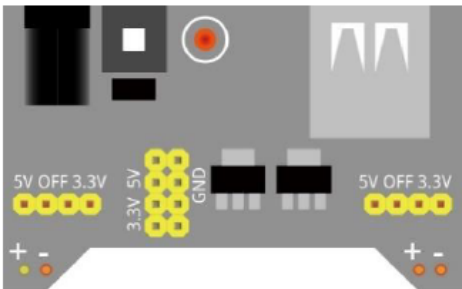

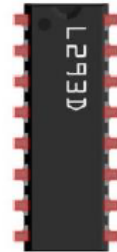

**In reviewing the DC Motor Controller Block Diagram, what is the name of the IC that performs the H-Bridge Motor Driver function?**



# Lab Project: A DC Motor Controller...


## Major Components



<p>Raspberry Pi x1 GPIO Extension Board &amp; Wire x1 BreadBoard x1</p>	<p>Jumper M/M x22</p> 	
<p>Breadboard power module x1</p> 	<p>Motor x1</p> 	<p>L293D</p> 
<p>9V Battery (provided by yourself) &amp; battery cable</p> 		

# Lab Project: A DC Motor Controller...


## Electrical Wiring Diagram

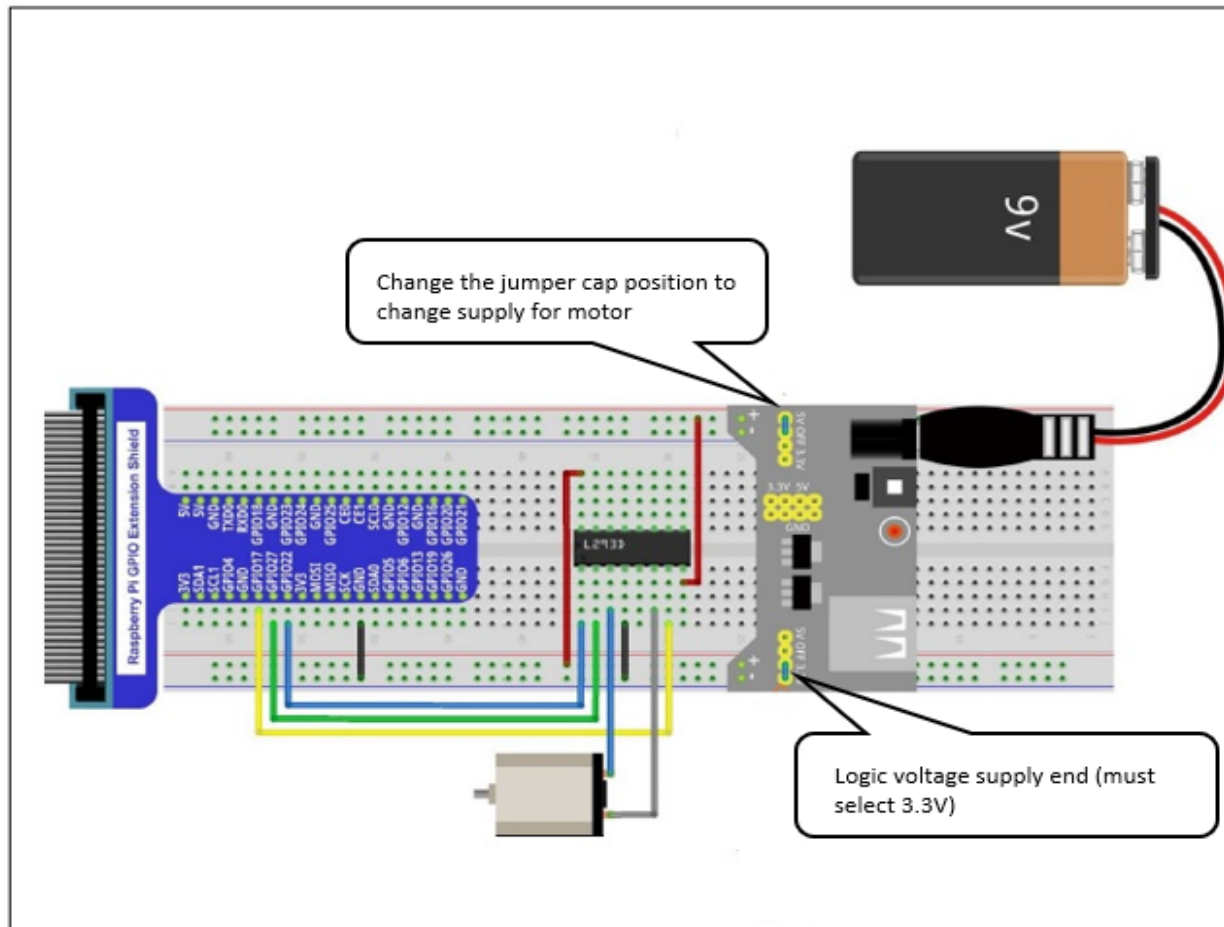

# Lab Project: A DC Motor Controller...



## Electronic Circuit Schematic Diagram

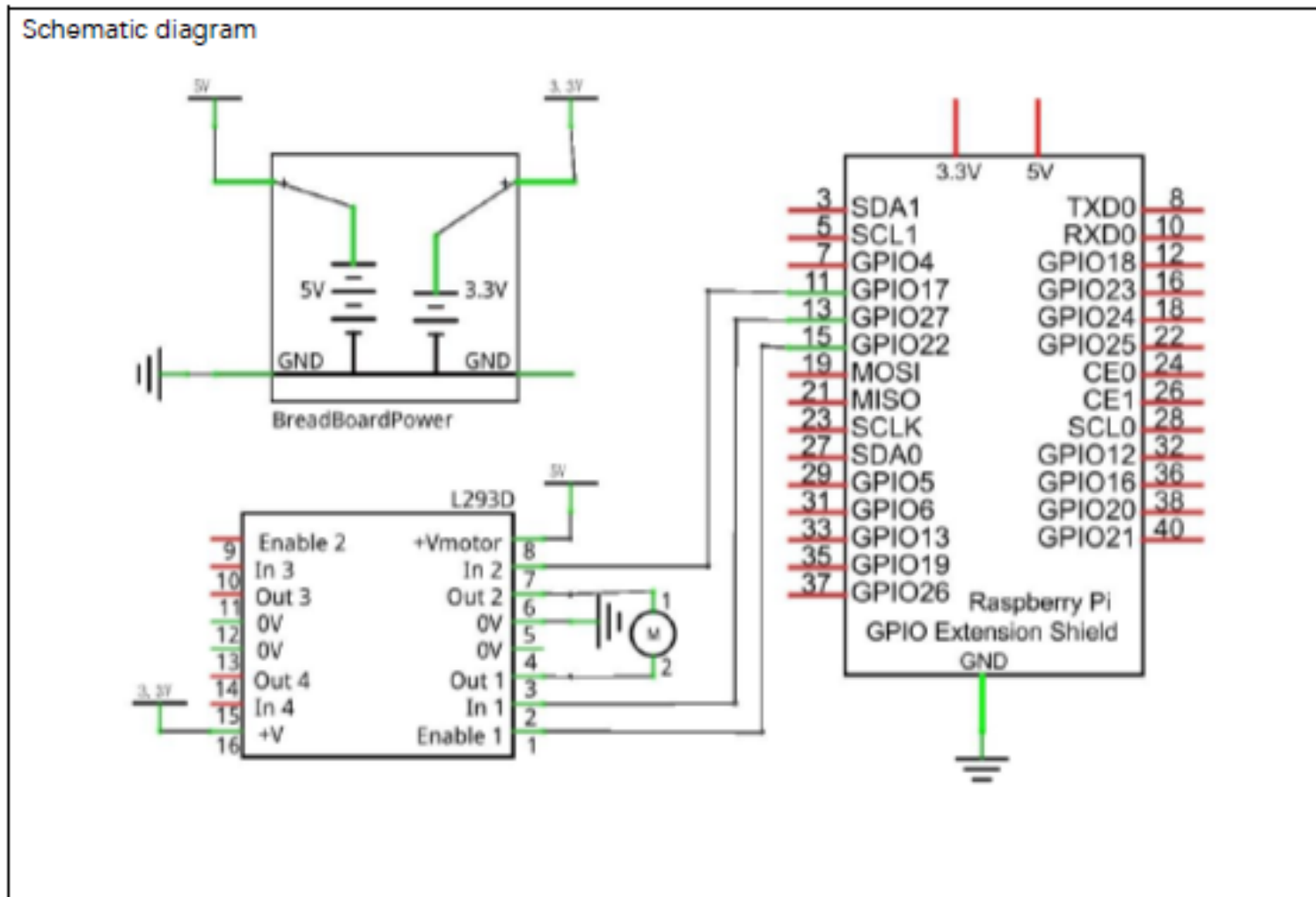

## Question 4




**In reviewing the electronic circuit schematic diagram shown on slide 26, which GPIO pin on the GPIO Expansion Shield is responsible for enabling the driver circuit wired to the DC motor?**





# Lab Project: A DC Motor Controller...

## Circuit Breadboard Complete

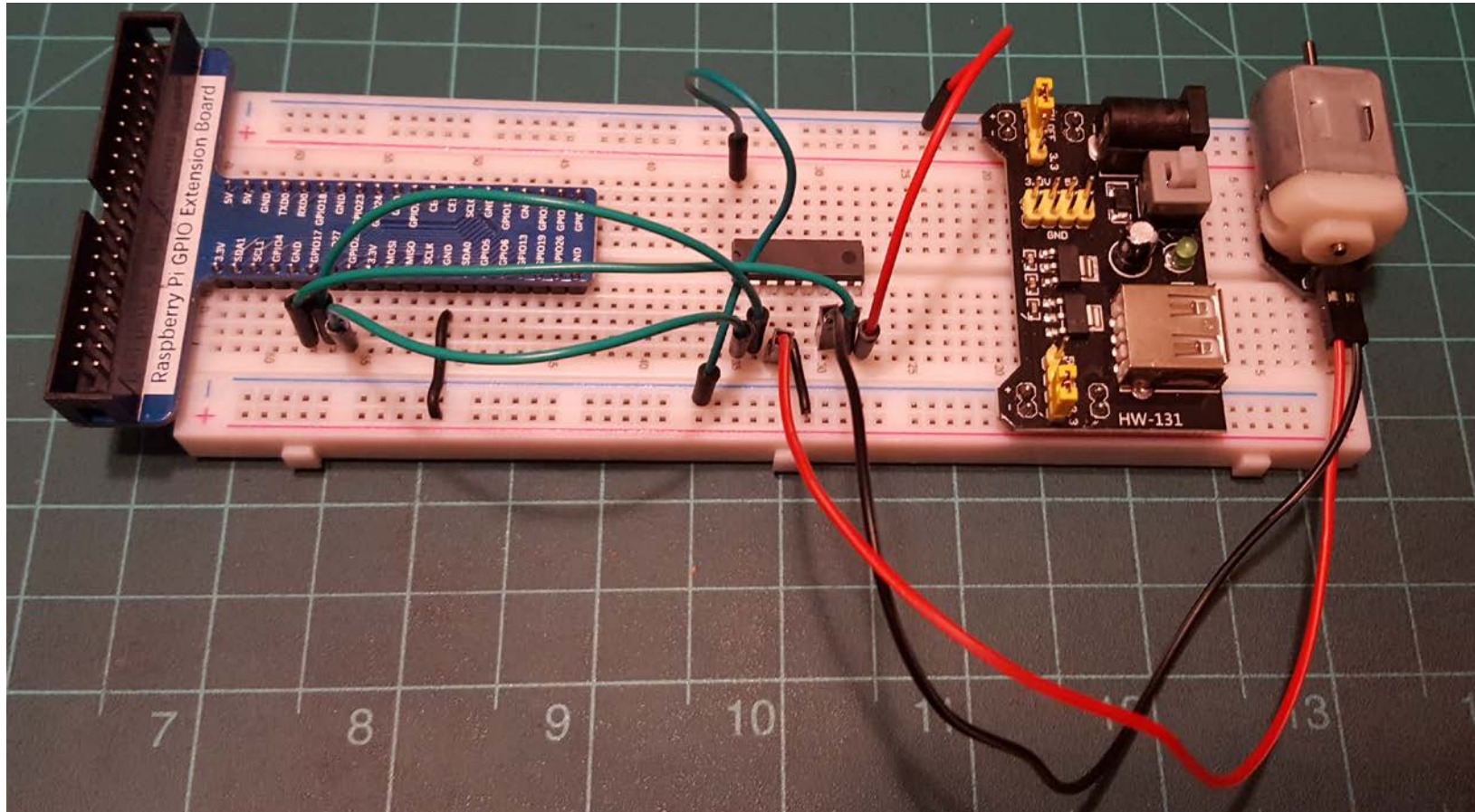




## Lab Project: A DC Motor Controller...




Demo

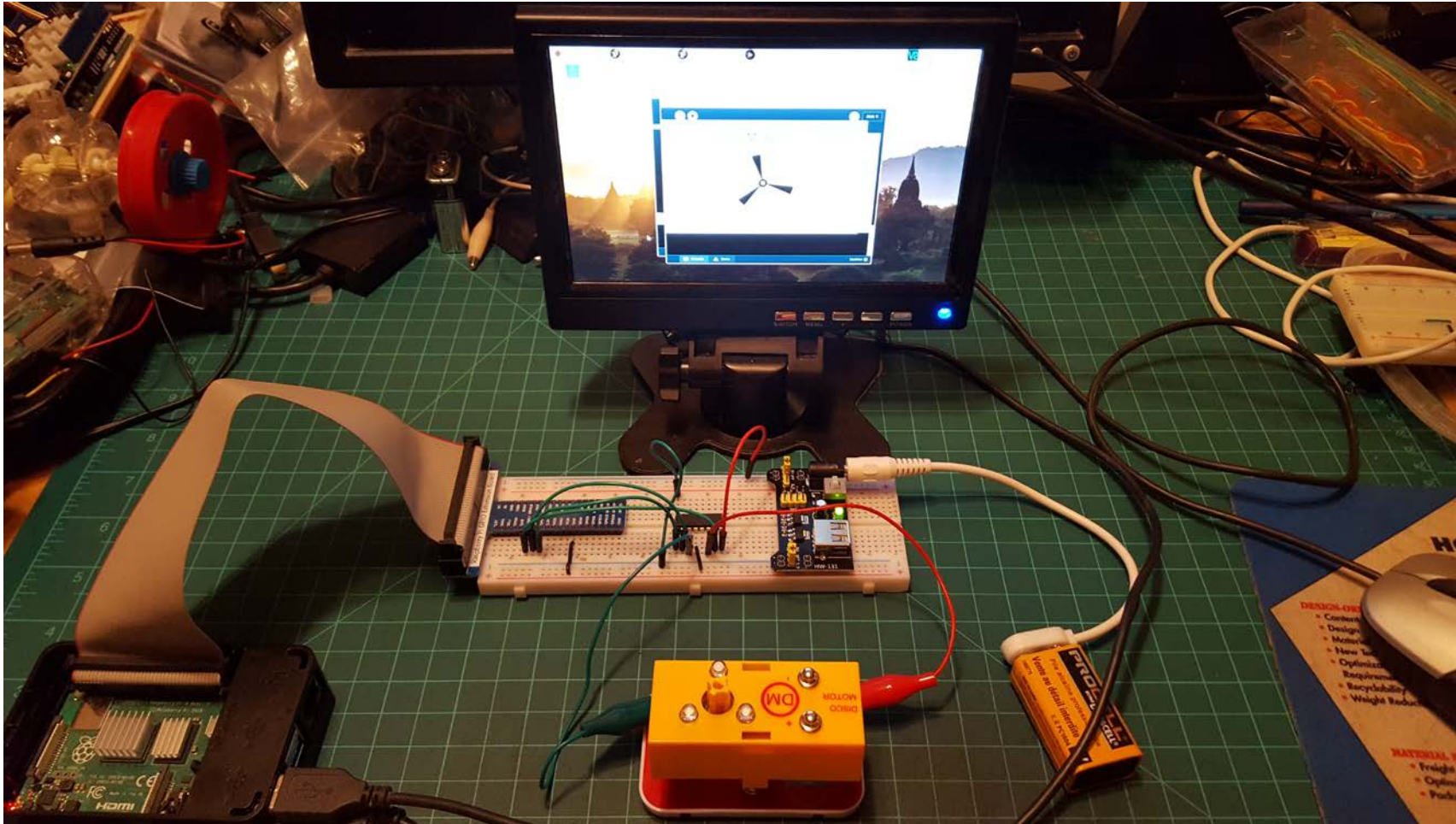

<https://youtu.be/9fopAQj8cP0>

# Lab Project: A DC Motor Controller...

## Processing Code

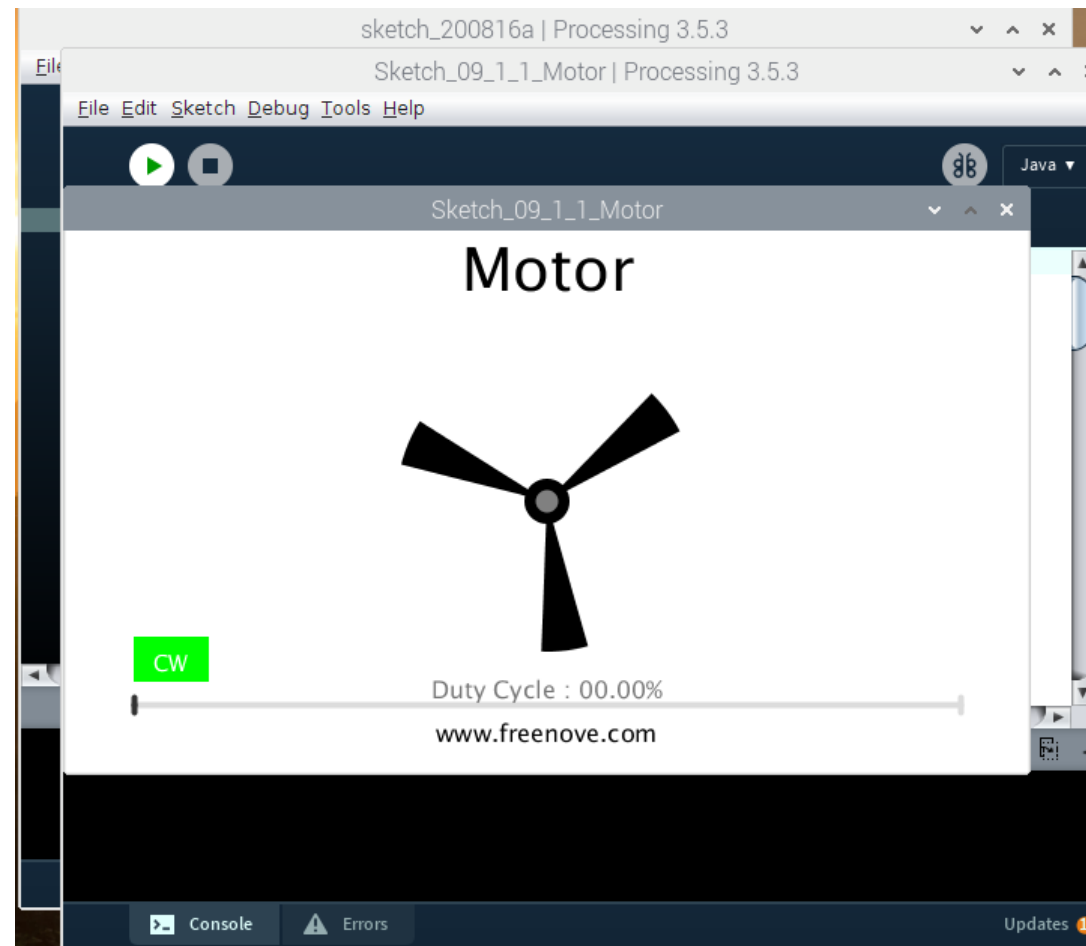

## Lab Project: A DC Motor Controller...



### Processing Code...

```
1 import processing.io.*;
2
3 int motorPin1 = 17; //connect to the L293D
4 int motorPin2 = 27;
5 int enablePin = 22;
6 final int borderSize = 45; //border size
7 //MOTOR Object
8 MOTOR motor = new MOTOR(motorPin1, motorPin2, enablePin);
9 ProgressBar mBar; //ProgressBar Object
10 boolean mMouse = false; //determined whether a mouse click the ProgressBar
11 BUTTON btn; //BUTTON Object, For controlling the direction of motor
12 int motorDir = motor.CW; //motor direction
13 float rotaSpeed = 0, rotaPosition = 0; //motor speed
14 void setup() {
15     size(640, 360);
16     mBar = new ProgressBar(borderSize, height-borderSize, width-borderSize*2);
17     mBar.setTitle("Duty Cycle"); //set the ProgressBar's title
18     btn = new BUTTON(45, height - 90, 50, 30); //define the button
19     btn.setBgColor(0, 255, 0); //set button color
20     btn.setText("CW"); //set button text
21 }
```



## Lab Project: A DC Motor Controller...



### Processing Code...

```
23 void draw() {
24     background(255);
25     titleAndSiteInfo(); //title and site information
26     strokeWeight(4); //border weight
27     mBar.create(); //create the ProgressBar
28     motor.start(motorDir, (int)(mBar.progress*100)); //control the motor starts to rotate
29     btn.create(); //create the button
30     rotaSpeed = mBar.progress * 0.02 * PI; //virtual fan's rotating speed
31     if (motorDir == motor.CW) {
32         rotaPosition += rotaSpeed;
33         if (rotaPosition >= 2*PI) {
34             rotaPosition = 0;
35         }
36     } else {
37         rotaPosition -= rotaSpeed;
38         if (rotaPosition <= -2*PI) {
39             rotaPosition = 0;
40         }
41     }
42     drawFan(rotaPosition); //show the virtual fan in Display window
43 }
```

## Lab Project: A DC Motor Controller...



```
44 //Draw a clover fan according to the stating angle
45 void drawFan(float angle) {
46     constrain(angle, 0, 2*PI);
47     fill(0);
48     for (int i=0; i<3; i++) {
49         arc(width/2, height/2, 200, 200, 2*i*PI/3+angle, (2*i+0.3)*PI/3+angle, PIE);
50     }
51     fill(0);
52     ellipse(width/2, height/2, 30, 30);
53     fill(128);
54     ellipse(width/2, height/2, 15, 15);
55 }
```

### Processing Code...



## Lab Project: A DC Motor Controller...



```
57 void mousePressed() {
58     if ( (mouseY < mBar.y+5) && (mouseY > mBar.y-5) ) {
59         mMouse = true;    //the mouse click the progressBar
60     } else if ((mouseY < btn.y+btn.h) && (mouseY > btn.y)
61         && (mouseX < btn.x+btn.w) && (mouseX > btn.x)) { // the mouse click the button
62         if (motorDir == motor.CW) {    //change the direction of rotation of motor
63             motorDir = motor.CCW;
64             btn.setBgColor(255, 0, 0);
65             btn.setText("CCW");
66         } else if (motorDir == motor.CCW) {
67             motorDir = motor.CW;
68             btn.setBgColor(0, 255, 0);
69             btn.setText("CW");
70         }
71     }
72 }
```

**Processing Code...**

## Lab Project: A DC Motor Controller...



### Processing Code...

```
73 void mouseReleased() {
74     mMouse = false;
75 }
76 void mouseDragged() {
77     int a = constrain(mouseX, borderSize, width - borderSize);
78     float t = map(a, borderSize, width - borderSize, 0.0, 1.0);
79     if (mMouse) {
80         mBar.setProgress(t);
81     }
82 }
83 void titleAndSiteInfo() {
84     fill(0);
85     textAlign(CENTER); //set the text centered
86     textSize(40); //set text size
87     text("Motor", width / 2, 40); //title
```

## Lab Project: A DC Motor Controller...



## Processing Code...

```
88     textSize(16);  
89     text("www.freenove.com", width / 2, height - 20);    //site  
90 }
```

---

## Question 5



**Identify the Processing Code line number that displays the developer's website on the virtual simulator control panel.**

## Thank you for attending

Please consider the resources below:

- The L239 H-Bridge Motor Driver IC Datasheet  
<https://www.mouser.com/datasheet/2/389/cd00000059-1795435.pdf>
- Physical Computing  
O'Sullivan, D., & Igoe, T. (2004). *Physical computing: Sensing and controlling the physical world with computers*. Boston, MA: Thompson.
- Freenove Ultimate Starter Kit for Raspberry Pi  
<http://www.freenove.com/tutorial.html>
- H-Bridge Driver Circuit  
<https://www.build-electronic-circuits.com/h-bridge/>





Thank You

Sponsored by

